

## ABET Check-Up

### Electrical and Computer Engineering Department University of New Mexico

Fall 2011

9  
/

#### Problem 1

Three voltage sources  $v_1(t)$ ,  $v_2(t)$  and  $v_3(t)$  are connected in series to a network, where (SCORE = 9)

$$v_1(t) = 1.0 \cos(100t + 45^\circ) \text{ V}$$

$$v_2(t) = 1.0 \cos(100t + 180^\circ) \text{ V}$$

$$v_3(t) = 1.0 \cos(130t - 135^\circ) \text{ V}$$

Note that  $v_3$  has a different frequency than  $v_1$  and  $v_2$ .

- Write down two forms of the phasors of  $v_1$ ,  $v_2$ , and  $v_3$
- Superpose these phasors as much as possible to find the simplest expression you can for the total series voltage  $v(t) = v_1 + v_2 + v_3$

$$\begin{aligned} a) \quad v_1 &= 1.0 \angle 45^\circ \text{ V} \quad \text{or} \quad -1.0 \angle -135^\circ \text{ V} \\ v_2 &= 1.0 \angle 180^\circ \text{ V} \quad \text{or} \quad -1.0 \angle 0^\circ \text{ V} \\ v_3 &= 1.0 \angle -135^\circ \text{ V} \quad \text{or} \quad -1.0 \angle 45^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} b) \quad v_1 + v_2 &= 1.0 \left( \frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}} - 1 \right) = 1.0 (1.707 + j \cdot 0.707) \\ &= 1.848 \angle 22.5^\circ \text{ V} \end{aligned}$$

$$v = 1.848 \cos(100t + 22.5^\circ) \text{ V} + 1.0 \cos(130t - 135^\circ)$$

24/24

### Problem 2

For each circuit element, R, L, and C, in the table, write down the expression for the impedance, Z, admittance, Y, resistance, R, conductance, G, reactance, X, and susceptance, B at an angular frequency  $\omega$ . Also, below Z, Y, R, G, B, and X give its SI units. (Score 24)


	Resistor, R	Capacitor, C	Inductor, L
Impedance, Z Units: <u>ohms</u>	R	$\frac{1}{j\omega C}$	$j\omega L$
Admittance, Y Units: <u>siemens</u>	$\frac{1}{R}$	$j\omega C$	$\frac{1}{j\omega L}$
Resistance, R Units: <u>ohms</u>	R	0	0
Conductance, G Units: <u>siemens</u>	$\frac{1}{R}$	0	0
Reactance, X Units: <u>ohm</u>	0	$\frac{1}{j\omega C}$	$j\omega L$
Susceptance, B Units: <u>siemen</u>	0	$j\omega C$	$\frac{1}{j\omega L}$

18  
-----  
14

**Problem 3** (score = 18)

The periodic current,  $i(t)$ , shown below flows through a  $10 \Omega$  resistor, a  $10 \text{ H}$  inductor, and a  $10 \text{ F}$  capacitor. Find (or write down an expression for)

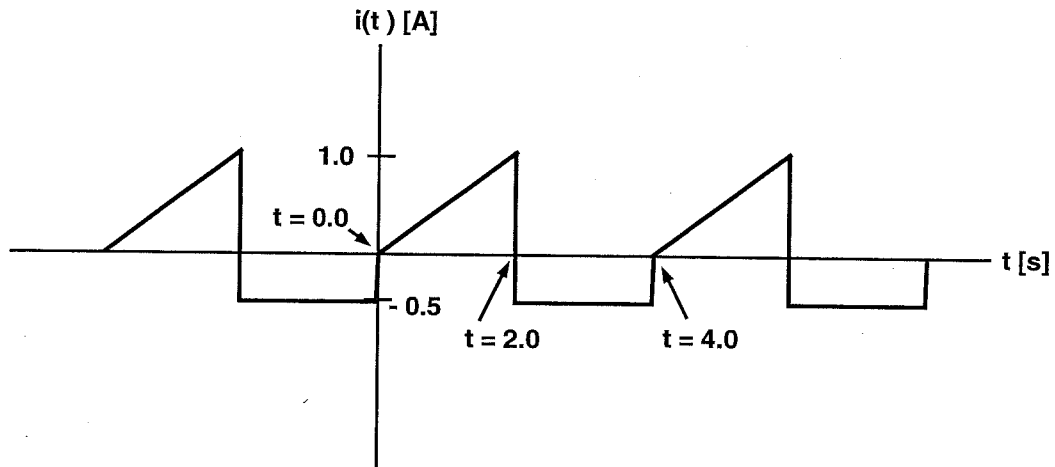- a) the real instantaneous power dissipated in the resistor, the inductor, and the capacitor
- b) the (time) average real power dissipated in the resistor, the inductor, and the capacitor



$$Z = 10 \Omega + j\omega 10 \text{ H} + \frac{1}{j\omega 10 \text{ F}}$$

a)  $P_R(t) = \dot{i}(t)^2 R$     $P_L(t) = 10 \text{ H } j\omega \dot{i}^2(t)$     $P_C(t) = \frac{\dot{i}^2(t)}{j\omega 10 \text{ F}}$

b)  $P_R = \frac{1}{\sqrt{2}} I^2 R$     $P_L = 0$     $P_C = 0$

## ABET Check-Up

### Electrical and Computer Engineering Department University of New Mexico

Fall 2011

8  
—  
4

#### Problem 1

Three voltage sources  $v_1(t)$ ,  $v_2(t)$  and  $v_3(t)$  are connected in series to a network, where (SCORE = 9)

$$v_1(t) = 1.0 \cos(100t + 45^\circ) \text{ V}$$

$$v_2(t) = 1.0 \cos(100t + 180^\circ) \text{ V}$$

$$v_3(t) = 1.0 \cos(130t - 135^\circ) \text{ V}$$

change freq?

Note that  $v_3$  has a different frequency than  $v_1$  and  $v_2$ .

- Write down two forms of the phasors of  $v_1$ ,  $v_2$ , and  $v_3$
- Superpose these phasors as much as possible to find the simplest expression you can for the total series voltage  $v(t) = v_1 + v_2 + v_3$

a)

$$V_1 = 1 + j100 = 1 \angle 45^\circ$$

$$V_2 = 1 + j100 = 1 \angle 180^\circ$$

$$V_3 = 1 + j130 = 1 \angle -135^\circ$$

$$V = 3 + j330 \quad X$$

3/24

$V = IR$

**Problem 2**

For each circuit element, R, L, and C, in the table, write down the expression for the impedance, Z, admittance, Y, resistance, R, conductance, G, reactance, X, and susceptance, B at an angular frequency  $\omega$ . Also, below Z, Y, R, G, B, and X give its SI units. (Score 24)

	Resistor, R	Capacitor, C	Inductor, L
Impedance, Z Units: $\checkmark$ <u><math>\Omega</math></u>	$\frac{V}{I}$		
Admittance, Y Units: $\checkmark$ <u><math>\frac{1}{\Omega}</math></u>	$\frac{I}{V}$		
Resistance, R Units: $\checkmark$ <u><math>\Omega</math></u>	$\frac{V}{I}$		
Conductance, G Units: $\times$ <u>Farad.</u>			
Reactance, X Units: $\times$ <u>Henry.</u>			
Susceptance, B Units: $\times$			


**Problem 3** (score = 18)

10 Ω 10 H 10 F  
~~10 Ω 10 H 10 F~~

The periodic current,  $i(t)$ , shown below flows through a  $10 \Omega$  resistor, a  $10 \text{ H}$  inductor, and a  $10 \text{ F}$  capacitor. Find (or write down an expression for)

- a) the real instantaneous power dissipated in the resistor, the inductor, and the capacitor  
 b) the (time) average real power dissipated in the resistor, the inductor, and the capacitor

$\frac{6}{18}$

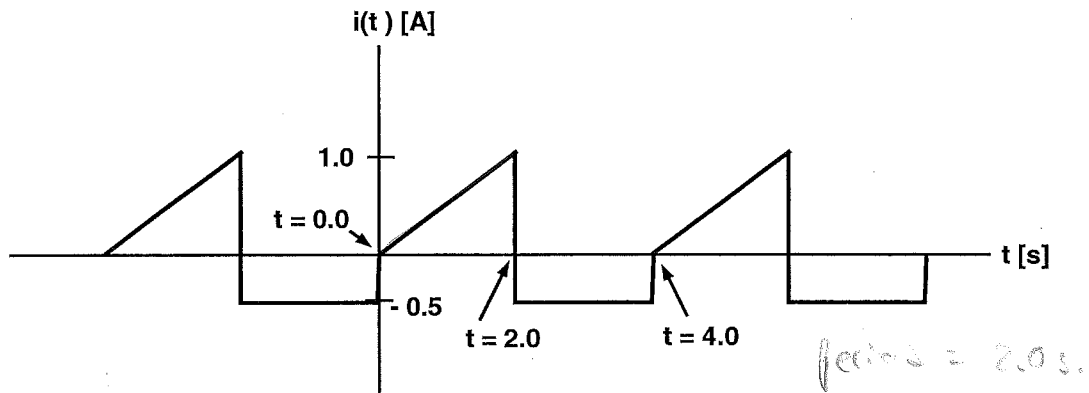

a)  $P(t) = VI = I^2 R = \int_0^T i(t)^2 dt$  X

b) Resistor  $P = I^2 R = 10$

Inductor  $P = I^2 (10) = 10 \leftarrow 0$

Capacitor  $P = I^2 (10) = 10 \leftarrow 0$

## ABET Check-Up

Electrical and Computer Engineering Department  
University of New Mexico

Fall 2011

3  
9

### Problem 1

Three voltage sources  $v_1(t)$ ,  $v_2(t)$  and  $v_3(t)$  are connected in series to a network, where (SCORE = 9)

$$v_1(t) = 1.0 \cos(100t + 45^\circ) \text{ V}$$

$$v_2(t) = 1.0 \cos(100t + 180^\circ) \text{ V}$$

$$v_3(t) = 1.0 \cos(130t - 135^\circ) \text{ V}$$

Note that  $v_3$  has a different frequency than  $v_1$  and  $v_2$ .

- Write down two forms of the phasors of  $v_1$ ,  $v_2$ , and  $v_3$
- Superpose these phasors as much as possible to find the simplest expression you can for the total series voltage  $v(t) = v_1 + v_2 + v_3$

$$a) \quad v_1(t) = 1 \angle 100t + 45^\circ = \cos(100t + 45^\circ) + j \sin(100t + 45^\circ)$$

$$v_2(t) = 1 \angle 100t + 180^\circ = \cos(100t + 180^\circ) + j \sin(100t + 180^\circ)$$

$$v_3 = 1 \angle 130t - 135^\circ = \cos(130t - 135^\circ) + j \sin(130t - 135^\circ)$$

4  
—  
24

**Problem 2**

For each circuit element, R, L, and C, in the table, write down the expression for the impedance, Z, admittance, Y, resistance, R, conductance, G, reactance, X, and susceptance, B at an angular frequency  $\omega$ . Also, below Z, Y, R, G, B, and X give its SI units. (Score 24)


	Resistor, R	Capacitor, C	Inductor, L
Impedance, Z  Units: _____			
Admittance, Y  Units: _____			
Resistance, R  Units: ✓ _____ <u>ohms</u>	$R = \frac{V}{I}$		
Conductance, G  Units: ✓ _____ <u>mho's</u>	$\frac{1}{R}$ or $\frac{I}{V}$		
Reactance, X  Units: _____			
Susceptance, B  Units: _____			

**Problem 3** (score = 18)

The periodic current,  $i(t)$ , shown below flows through a  $10 \Omega$  resistor, a  $10 \text{ H}$  inductor, and a  $10 \text{ F}$  capacitor. Find (or write down an expression for)

- the real instantaneous power dissipated in the resistor, the inductor, and the capacitor
- the (time) average real power dissipated in the resistor, the inductor, and the capacitor

2  
/ 18

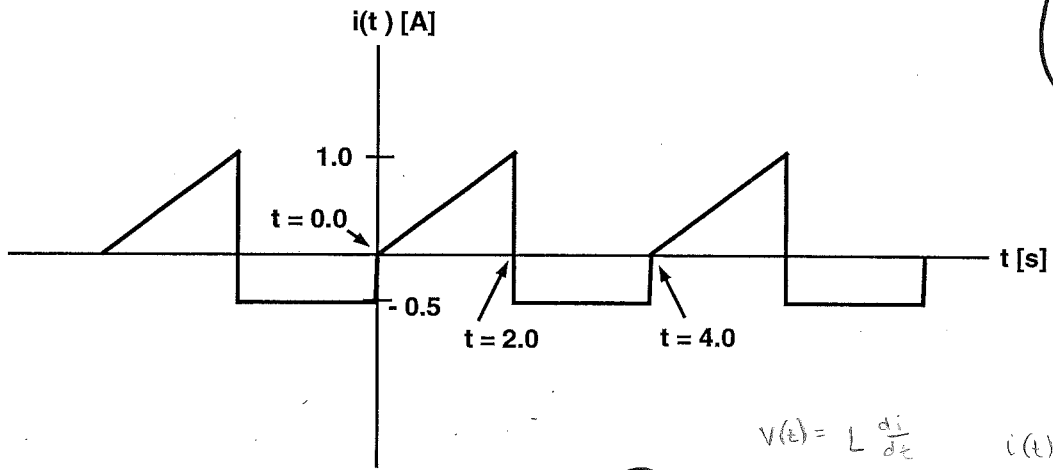

(a)  $P = vI(t)$

$v = IR$

$P = 10 i(t)^2 + vI + vI$

$P = RI^2$

$v(t) = L \frac{di}{dt}$

$i(t) = C \frac{dv}{dt}$

$P = 10 i(t)^2 + LI \frac{di}{dt} + CV \frac{dv}{dt}$