

Hardware Modeling

Verilog is a descriptive language that describes the *relationship between signals* in a circuit, and is *not* a computational program.

Verilog also has a semantic of *time* associated with signals, because it needs to model their temporal relationships and evolution.

Module Declaration:

```
module_declaration ::= module_keyword module_id [list_of_ports]
                    {module_item}
endmodule
module_keyword ::= module | macromodule
module_item ::=
    module_item_declaration |
    parameter_override |
    continuous_assign |
    gate_instantiation |
    upd_instantiation |
    module_instantiation |
    specify_block |
    initial_construct |
    always_construct |
```



Verilog Module Instantiation


Module ports can be scalar (single-value) or vector objects (one dimensional).

Keywords to classify ports include **input**, **output** and **inout**

Modules can be instantiated in parents.

```

 module half_adder(sum, c_out, a, b);
input a, b;
output sum, c_out;
wire c_out_bar;
xor(sum, a, b);
nand(c_out_bar, a, b);
not(c_out, c_out_bar);
endmodule
    
```



```

module full_adder(sum, c_out, a, b, c_in);
input a, b, c_in;
output sum, c_out;
wire w1, w2, w3;
    half_adder M1(w1, w2, a, b);
    half_adder M2(sum, w3, w1, c_in);
or (c_out, w2, w3);
endmodule
    
```

Module instance name

Verilog Primitives

The predefined primitives implement the behavior of a combinational logic function or transistor level switch.

- Combinational Logic

`and, nand, or, nor, xor, xnor, buf, not`

- Three state

`bufif0, bufif1, notif0, notif1`

- MOS gates

`nmos, pmos, rnmos, rpmos`

- CMOS gates

`cmos, rcmos`

- Bi-directional gates

`tran, tranif0, tranif1, rtran, rtranif0, rtranif1`

- Pull Gates

`pulldown, pullup`

Note that the first port in any primitive is the *output* port.

Verilog Primitives

The primitives allow for *gate level* and *switch level* modeling.

They are idealized models because they ignore the time delays exhibited in real gates by default.

However, delays can be assigned when they are instantiated.

```
module AOI_4_unit(y_out, x_in1, x_in2, x_in3, x_in4);  
  input x_in1, x_in2, x_in3, x_in4;  
  output y_out;  
  wire y1, y2;  
  
  and #1 (y1, x_in1, x_in2);  
  and #1 (y2, x_in3, x_in4);  
  nor #1 (y_out, y1, y2);  
endmodule
```

Note that these delays are ONLY used during simulation, i.e., they have no effect during synthesis.

A *module instance name* is optional with verilog primitives.

Verilog Primitives

Timing is a very important property of a circuit and Verilog allows **accurate** timing information to be incorporated (if it is available).

For example, propagation delay may be different for rising and falling edges and the designer may want to simulate *worst, typical* and *best* case corners.

Process variations make each chip a little bit different.

```

module nanf201(O, A1, B1);
  input A1, B1;
  output O;
  nand(O, A1, B1);
  specify
    specparam
      Tpd_0_1 = 1.13:3.09:7.75
      Tpd_1_0 = 0.93:2.50:7.34
      (A1 => O) = (Tpd_0_1, Tpd_1_0);
      (B1 => O) = (Tpd_0_1, Tpd_1_0);
  endspecify
endmodule
    
```

The individual path delays are given for each input-to-output path.



Verilog Primitives

Verilog primitives are "smart" because the same primitive, e.g., **nand**, can be used for a gate with any number of inputs.

For example, **nand**(O, A1, A2, A3) instantiates a *3-input* version of the Verilog **nand** gate primitive.

Explicit and Implicit Structural Description

As indicated, *explicit* structural descriptions are analogous to placing and wiring components on a schematic diagram.

We've seen examples of this style previously.

Implicit structural descriptions make use of Verilog built-in operators within the **continuous assignment statement**.

```
module nand2_RTL(y, x1, x2);  
  input x1, x2;  
  output y;  
  
  assign y = x1 ~& x2;    Bitwise-nand  
  
endmodule
```



Explicit and Implicit Structural Description

Here, the operators are not bound directly to physical gates.

The keyword **assign** declares a Verilog *continuous assignment*.

Continuous assignment corresponds to combinational logic, without requiring explicit instantiation of gates.

Think of these as "event scheduling rules".

In this example, the continuous assignment defines how output, y , depends on events that occur for signals $x1$ and $x2$.

This style is also called a **data flow** or **RTL** description.

Continuous assignment can be made in 2 ways.

The first, as we have seen, uses the keyword **assign**:

```
cont_assign ::= assign [drive_strength][delay3] list_of_net_assignments;
```

Explicit and Implicit Structural Description

The second method creates a *continuous assignment* **implicitly** within the declaration.

```
module bit_or8_gate1(y, a, b);  
  input [7:0] a, b;  
  output [7:0] y;  
  wire [7:0] y = a|b;  
  
endmodule
```

Port Connection Syntax

A connection to a port of a Verilog module can be made in 2 ways.

The first is by position, as we have seen, and the second is by naming.

```
module parent_mod;  
  wire [3:0] g;  
  child_mod(.c(g[3]),  
            .d(g[2]), .b(g[0]),  
            .a(g[1]));  
endmodule
```

```
module child_mod(a, b, c, d);  
  input a, b;  
  output c, d;  
  // Other stuff  
endmodule
```



Behavioral Descriptions

Consist of procedural statements that define input-output signal relationships *without* reference to hardware or structure.

There are two basic styles of *behavioral description*.

- Register transfer level (RTL), defines input-output relationships in terms of dataflow operations on signals and register values.
- Abstract, algorithmic description of operations, that need not conform to a dataflow and which may *not* be synthesizable.

RTL/Data Flow Descriptions

Verilog language operators are used to define the flow of data.

For combinational logic, the *continuous assignment* statement is used (for *implicit structural model*).

```
module and4_rtl(y_out, x1, x2, x3, x4);  
  input x1, x2, x3, x4;  
  output y_out;  
  assign y_out = x1 & x2 & x3 & x4;  
endmodule
```



RTL/Data Flow Descriptions

A sequential example:

```
module FF(q, dat_in, clk, set, rst);
  input data_in, clk, set, rst;
  output q;
  reg q;
  always @(posedge clk)
  begin
    if (rst == 0)    q = 0;
    else
      if (set == 0)  q = 1;
      else
        q = data_in;
    end
  endmodule
```

Here, the FF output, q , is updated **synchronously**, and retains its value between clk edges.

reg types retain an assigned value until another assignment is made to them (similar to variables in C).

They can be assigned a value **ONLY** by a procedural statement.



Algorithm-Based Descriptions

An algorithmic description of behavior assigns value to a register storage (**reg**) by executing *procedural statements*.

The procedural statements are those common in high-level languages.

```
module and4_algo(y_out, x_in);
```

```
  input [3:0] x_in;
```

```
  output y_out;
```

```
  reg y_out;
```

```
  integer k;
```

```
  always @(x_in)
```

```
    begin: and_loop
```

```
      y_out = 1;
```

```
      for (k = 0; k <= 3; k = k + 1)
```

```
        if (x_in[k] == 0)
```

```
          begin
```

```
            y_out = 0;
```

```
            disable and_loop;
```

```
          end
```

```
        end
```

```
    endmodule
```

Sensitivity list consists of 4 bits. A change in one or more causes block to execute during a simulation

Behavior implemented may be *combinational* or *sequential* -- it depends on the data dependencies and computations performed

Data objects of type **reg** and **integer** can only be changed by a procedural stmt.



Algorithm-Based Descriptions

The **always** statement waits for an event on its event expression, i.e. for x_in to change value.

The @ operator informs the simulator to monitor changes on the event expression (in this case, if any of the bits with x_in change).

Verilog's **initial** statement is very similar to the **always** statement, except it only executes exactly once (does not wait and repeat like **always**).

Verilog for Synthesis

HDLs play a significant role in design flows that synthesize behavioral descriptions to gate level netlists.

A given functionality can be synthesized from a variety of descriptions.



Verilog for Synthesis


The functionality of the comparator can be represented by the following boolean expressions.

$$A_lt_B = \overline{A1} B1 + \overline{A1} \overline{A0} B0 + \overline{A0} B1 B0$$

$$A_gt_B = A1 \overline{B1} + A0 \overline{B1} \overline{B0} + A1 A0 \overline{B0}$$

$$A_eq_B = \overline{A1} \overline{A0} \overline{B1} \overline{B0} + \overline{A1} A0 \overline{B1} B0 + A1 A0 B1 B0 + A1 \overline{A0} B1 \overline{B0}$$

 Using Karnaugh maps to eliminate redundant logic yields



Verilog for Synthesis

The **explicit** structural Verilog description can be derived directly from the schematic.

```
module compare_2_str(A_lt_B, A_gt_B, A_eq_B, A0, A1,
                    B0, B1);
input A0, A1, B0, B1;
output A_lt_B, A_gt_B, A_eq_B;
wire w1, w2, w3, w4, w5, w6, w7;

or(A_lt_B, w1, w2, w3);
nor(A_gt_B, A_lt_B, A_eq_B);
and(A_eq_B, w4, w5);
and(w1, w6, B1);
and(w2, w6, w7, B0);
and(w3, w7, B0, B1);
not(w6, A1);
not(w7, A0);
xnor(w4, A1, B1);
xnor(w5, A0, B0);

endmodule
```



Verilog for Synthesis

Alternatively, the comparator can be described by a Verilog RTL model using *continuous assignment*.

```
module compare_2a(A_lt_B, A_gt_B, A_eq_B, A0, A1,
                  B0, B1);
input A0, A1, B0, B1;
output A_lt_B, A_gt_B, A_eq_B;

assign A_lt_B = (~A1) & B1 | (~A1) & (~A0) & B0 |
               (~A0) & B1 & B0;
assign A_gt_B = A1 & (~B1) | A0 & (~B1) & (~B0) |
               A1 & A0 & (~B0);
assign A_eq_B = (~A1) & (~A0) & (~B1) & (~B0) |
               (~A1) & A0 & (~B1) & B0 |
               A1 & (~A0) & B1 & (~B0) |
               A1 & A0 & B1 & B0;

endmodule
```

Focus here is not on the detail but rather only on the input-output relationship.

Verilog for Synthesis

A simpler implementation that exploits Verilog operators.

```
module compare_2b(A_lt_B, A_gt_B, A_eq_B, A0, A1,
                 B0, B1);
  input A0, A1, B0, B1;
  output A_lt_B, A_gt_B, A_eq_B;

  assign A_lt_B = ({A1,A0} < {B1,B0});
  assign A_gt_B = ({A1,A0} > {B1,B0});
  assign A_eq_B = ({A1,A0} == {B1,B0});
endmodule
```

A second version using continuous assign:

```
module compare_2_ca(A_lt_B, A_gt_B, A_eq_B, A, B);
  input [1:0] A, B;
  output A_lt_B, A_gt_B, A_eq_B;

  assign A_lt_B = (A < B);
  assign A_gt_B = (A > B);
  assign A_eq_B = (A == B);
endmodule
```



Verilog for Synthesis

The algorithmic model

```
module compare_2_algo(A_lt_B, A_gt_B, A_eq_B, A, B);  
  input [1:0] A,B;  
  output A_lt_B, A_gt_B, A_eq_B;  
  reg A_lt_B, A_gt_B, A_eq_B;  
  
  always @ (A or B)  
  begin  
    A_lt_B = 0; A_gt_B = 0; A_eq_B = 0;  
    if (A == B) A_eq_B = 1;  
    else if (A > B) A_gt_B = 1;  
    else A_lt_B = 1;  
  end  
endmodule
```



Language Conventions

Verilog is case sensitive - all verilog keywords are lower case.

Identifiers can use upper and lower case alphabetical chars, the decimal digits and the underscore.

Single line comments use `//` while multiple line comments use `/* ... */`

All names that begin with `$` denote a built-in system task or function.

Numbers can be represented in decimal (d or D), hex (h or H), octal (o or O) and binary (b or B) formats.

Format is `<size><base_format><number>`, and `<size>` is optional, e.g.,

- `8'b1010` (stored as `0000_1010`)
- `4'hA` (stored as `1010`)
- `12'bx0001` (stored as `xxxx_xxxx_0001` with x indicating undefined)
- `3'b5` (illegal)