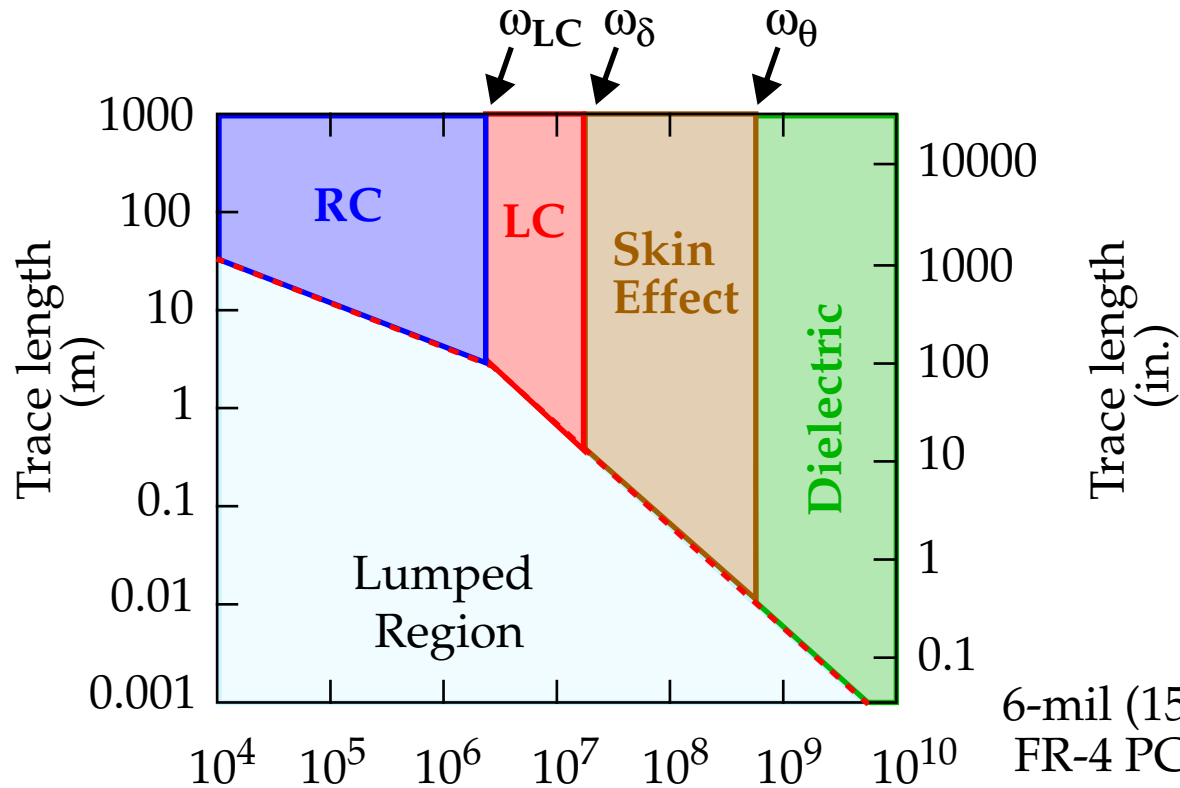


### Skin-Effect Region

In the skin-effect region, the *internal inductance* of the conductors becomes significant compared to the DC resistance.



6-mil (150  $\mu\text{m}$ ), 50- $\Omega$ , FR-4 PCB stripline

$\omega_{\delta}$  delineates the start of the region where the real part of the skin-effect resistance,  $R_{AC}$ , equals the DC resistance,  $R_{DC}$ .

## Skin-Effect Region

Recalling from previous discussions

$$R_{DC} = \frac{k_a \rho}{a}$$

$$Re[R_{AC}] = \frac{k_p k_r \sqrt{\omega \mu}}{p \sqrt{2\sigma}}$$

$\omega_\delta$  is given by

$$\omega_\delta = \omega_0 \left( \frac{R_{DC}}{R_0} \right)^2$$

Here,  $\omega_0$  is a frequency well into the skin-effect region and  $R_0$  is the value of  $R_{AC}$  at that frequency.

In skin-effect mode, the **characteristic impedance** remains fairly flat but the **line attenuation** in dB varies in proportion to the *square root of frequency*.

Characteristic impedance is given by

$$Z_C = \sqrt{\frac{j\omega L_0 + R(\omega)}{j\omega C}}$$



### Skin-Effect Characteristic Impedance

The term  $L_0$  refers to the *external inductance* of the line, since *internal inductance* is accounted for in  $R(\omega)$ .

External inductance is the value of series inductance assuming that current rides on the surface without penetrating the wire.

As you proceed to higher frequencies above  $\omega_\delta$ , the contribution of  $R(\omega)$  becomes negligible, leaving


$$Z_0 \triangleq \lim_{\omega \rightarrow \infty} \sqrt{\frac{j\omega L_0 + R(\omega)}{j\omega C}} = \sqrt{\frac{L_0}{C}}$$

This indicates that although  $R(\omega)$  grows in proportion to the square root of frequency,  $j\omega L_0$  grows more quickly.

Therefore, once past the cross-over  $\omega_{LC}$  (remember, this is where the inductance impedance equals the DC resistance),  $R(\omega)$  diminishes in importance.
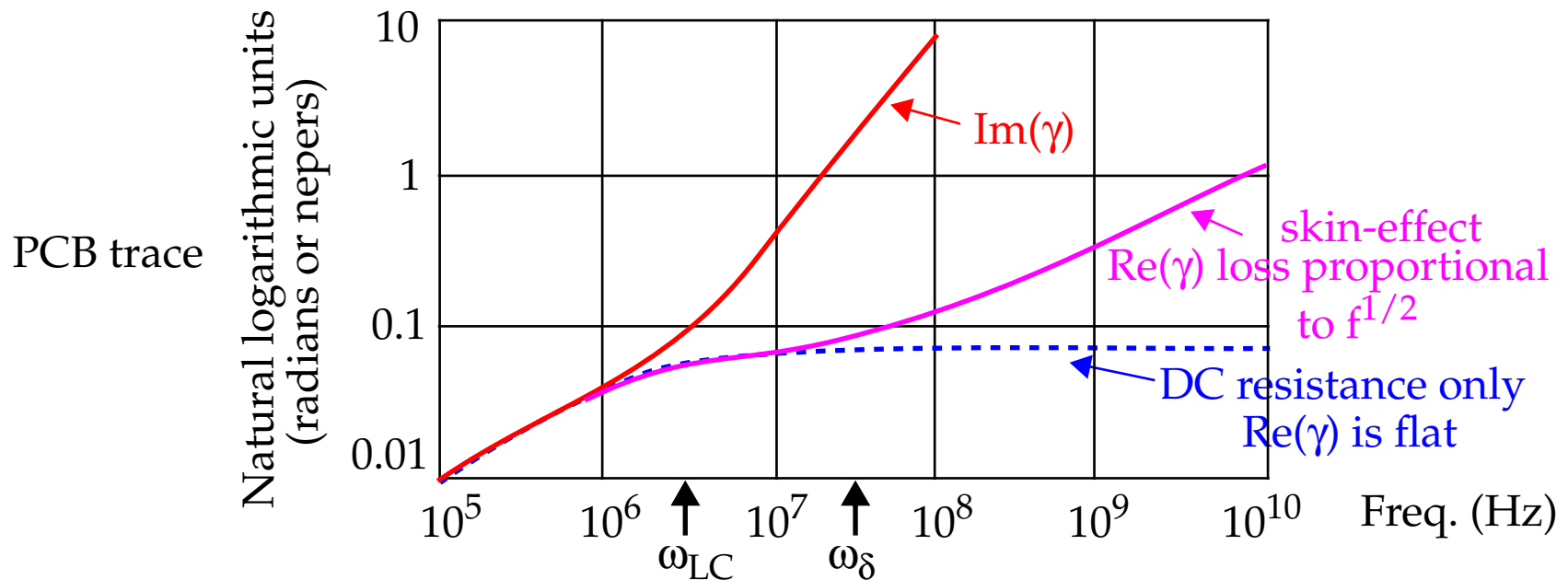
### Skin-Effect Propagation Coefficient

Because the skin-effect onset is so close to the LC-mode onset, the flat region for the real part is very small.



As indicated, after  $\omega_{\delta}$ , attenuation (in dB) increases proportional to the square root of frequency.

The *decoupling* of phase and attenuation enable the construction of a line with an enormous phase delay and yet very low attenuation.



### Skin-Effect Propagation Coefficient

Propagation function assuming operation at a frequency well in excess of  $\omega_s$

so that  $R_{AC} \gg R_{DC}$

$$\gamma(\omega) = \sqrt{(j\omega L_0 + R_{AC})(j\omega C)}$$

Factoring out common  $j\omega L_0$  and  $j\omega C$  terms

$$\gamma(\omega) = \sqrt{(j\omega L_0)(j\omega C)} \sqrt{1 + \frac{R_{AC}}{j\omega L_0}}$$

Assuming  $\omega \gg \omega_{LC}$  so that  $|j\omega L_0| \gg |R_{AC}|$

$$\gamma(\omega) = \sqrt{(j\omega L_0)(j\omega C)} \left( 1 + \frac{1}{2} \frac{R_{AC}}{j\omega L_0} \right)$$

Distributing

$$\gamma(\omega) = \sqrt{(j\omega L_0)(j\omega C)} + \sqrt{(j\omega L_0)(j\omega C)} \frac{1}{2} \frac{R_{AC}}{j\omega L_0}$$

### Skin-Effect Propagation Coefficient

Combining and substituting for characteristic impedance

$$\gamma(\omega) = \sqrt{(j\omega L_0)(j\omega C)} + \frac{1}{2} \frac{R_{AC}}{Z_0}$$

Factoring out  $j\omega$  on the left and substituting expression for  $R_{AC}$  described earlier

$$\gamma(\omega) = j\omega \sqrt{L_0 C} + \frac{(1+j)R_0}{2} \frac{1}{Z_0} \sqrt{\frac{\omega}{\omega_0}}$$

Like the LC region, the first term indicates linear phase and represent the bulk transport delay.

$$t_p \triangleq \frac{1}{v_0} = \sqrt{L_0 C} \text{ s/m}$$

The second term is a **low-pass filter** whose attenuation in dB grows proportional to the *sqrt*( $f$ ).

### Skin-Effect Propagation Coefficient

Similar to the LC region, the **skin-effect loss coefficient** can be defined

$$\alpha_r \triangleq \operatorname{Re}[\gamma(\omega)] = \frac{1}{2} \frac{R_0}{Z_0} \sqrt{\frac{\omega}{\omega_0}} \text{ neper/m} = 4.34 \frac{R_0}{Z_0} \sqrt{\frac{\omega}{\omega_0}} \text{ dB/m}$$

The low-pass filtering action will *slur* the rising edge of the step response, adding slew.

$$|H(\omega, l)| = e^{-l \frac{1}{2} \frac{R_0}{Z_0} \sqrt{\frac{\omega}{\omega_0}}}$$

Here again, doubling length, doubles the signal loss.


However, here signal loss is also **frequency dependent**, doubling the frequency multiplies the loss by the *sqrt(2)*.

The termination approaches discussed with reference to the LC region work here as well (and in the dielectric-loss-limited region).

This is true because all three regions share the same asymptotic high-frequency value of characteristic impedance  $Z_0$ .

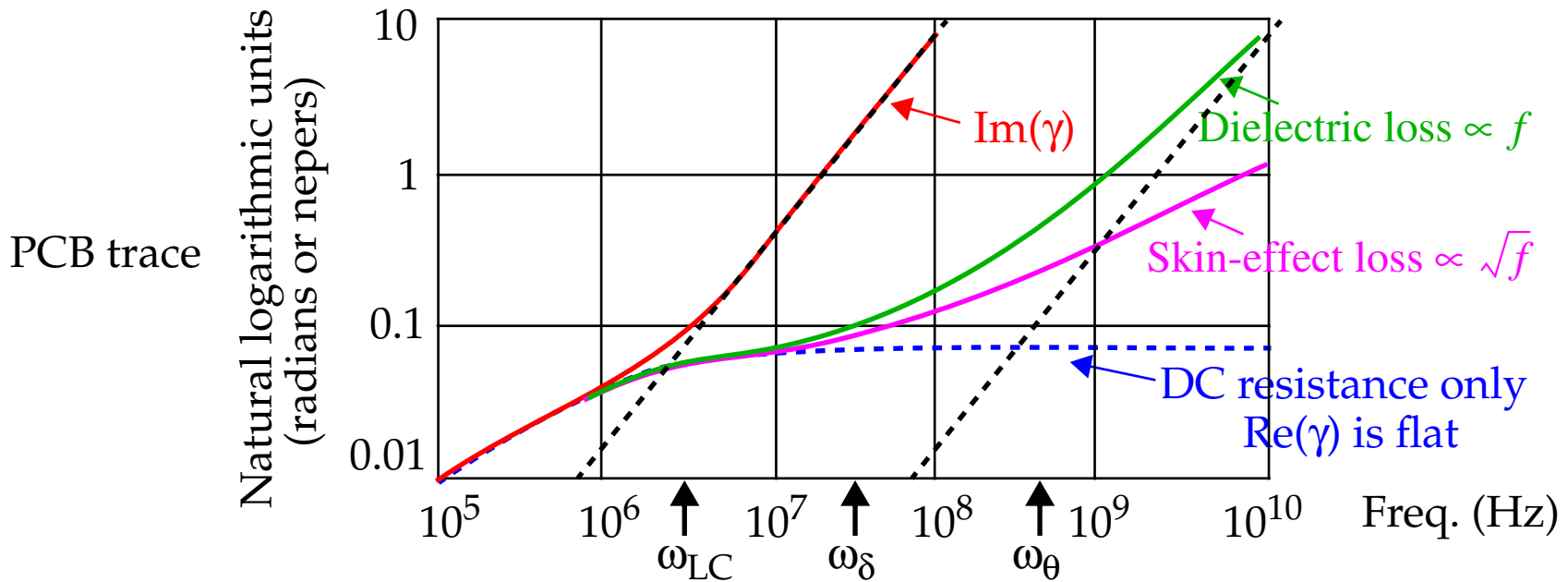**Dielectric-Loss-Limited Region**

Dielectric-loss increases the slope of the  $\text{Re}(\gamma)$



It is common in PCB problems to see skin-effect losses AND dielectric losses.

Waveguide-dispersion region begins when the frequency of the signal approaches the dimensions of your conductor.

For a stripline, the critical dimension is the spacing between the planes.

Strange modes appear, severe ringing occurs under perfect termination.



**Example**

## Specs

- Length  $l = 0.6$  m (23.6 in.) (backplane application)
- Conductor parameters:  $w = 152$   $\mu\text{m}$  (6 mil),  $t = 17.4$   $\mu\text{m}$  (1/2 oz. Cu), perimeter  $p = 2(w + t) = 339$   $\mu\text{m}$  (13.35 mil)
- Conductivity of signal conductor  $\sigma = 5.98 \times 10^7$  S/m
- Specification frequency for AC parameters:  $\omega_0 = 2\pi \times 10^9$
- Characteristic impedance at  $\omega_0$ :  $Z_0 = 100$   $\Omega$
- Effective dielectric constant  $\epsilon_R = 4.3$
- Effective loss tangent for FR-4 dielectric:  $\tan \theta_0 = 0.025$
- Proximity factor  $k_p = 3.2$

## Computed values

- Propagation velocity above RC region

$$v_0 = \frac{c}{\sqrt{\epsilon_R}} = 1.4457 \times 10^8 \text{ m/s} \quad t_p = 175.7 \text{ ps/in.}$$

**Example**

- Differential inductance per meter

$$L = \frac{Z_0}{v_0} = 691 \text{ nH/m}$$

- Differential capacitance per meter

$$C = \frac{1}{Z_0 v_0} = 69.1 \text{ pF/m}$$

- DC resistance

$$R_{DC} = \frac{2}{(\sigma w t)} = 12.64 \text{ } \Omega/\text{m}$$

- AC resistance

$$R_0 = \frac{k_p}{p} \sqrt{\frac{\omega_0 \mu}{2\sigma}} = 76.74 \text{ } \Omega/\text{m}$$

**Example**

Lumped-element region

$$\text{critical length} = \left( \frac{0.25}{R_{DC}} \right) \sqrt{\frac{L}{C}} = 1.97 \text{ m}$$

The trace length of  $l = 0.6 \text{ m}$  falls short of the critical length, so we move from lumped-element directly to LC, skipping the RC region.

Other region transitions

Note:  $\omega$  values multiplied by  $1/(2\pi)$ 

$\omega_{LC} = \left( \frac{\Delta}{l} \right) \sqrt{LC} = 9.58 \text{ MHz}$	LC Region
$\omega_{\delta} = \omega_0 \left( \frac{R_{DC}}{R_0} \right)^2 = 27.1 \text{ MHz}$	Skin-effect
$\omega_{\theta} = \frac{1}{\omega_0} \left[ \frac{(v_0 R_0)}{Z_0 \tan \theta_0} \right]^2 = 498 \text{ MHz}$	Dielectric (haven't covered)