

Register Transfer Methodology: Principle

We typically use **algorithms** to accomplish complex tasks

Although it is common to execute algorithms on a GPU, a hardware implementation is sometimes needed because of performance constraints

RT methodology is a design process that describes system operation by a sequence of data transfers and manipulations among **registers**

This methodology supports the sequential execution, e.g., data and control dependencies, required to carry out an algorithm

Consider an algorithm that computes the sum of 4 numbers, divides by 8 and rounds the result to the nearest integer

```
size = 4;  
sum = 0;  
for i in (0 to size-1) do  
    { sum = sum + a(i); }  
end
```

Register Transfer Methodology: Principle

```
q = sum/8;  
r = sum rem 8;  
if (r > 3)  
    { q = q + 1; }  
outp = q;
```

Algorithm characteristics:

- Algorithms use **variables**, memory locations with a symbolic addresses
Variables can be used to store *intermediate* results
- Algorithms are executed sequentially and the order of the steps is important

As we know, variables and sequential execution are supported as a special case and are **encapsulated** inside a process

However, variables are NOT treated as symbolic names for memory locations!

We also note that the sequential semantics of an algorithm are very different from the concurrent model of hardware

Register Transfer Methodology: Principle

What we have learned so far is how to transfer **sequential execution** into a **structural data flow**, where the sequence is embedded in the 'flow of data'

This is accomplished by mapping an algorithm into a system of *cascading hardware blocks*, where each block represents a statement in the algorithm


The previous algorithm can be **unrolled** into a data flow diagram

```
sum <= 0;
sum0 <= a(0);
sum1 <= sum0 + a(1);
sum2 <= sum1 + a(2);
sum3 <= sum2 + a(3);
q <= "000" & sum3(8 downto 3);
r <= "00000" & sum3(2 downto 0);
outp <= q + 1 when (r > 3) else
    q;
```

Note that this is very different from the algorithm -- the circuit is a pure combinational (and parallel) logic circuit with NO memory elements

Register Transfer Methodology: Principle

Block diagram

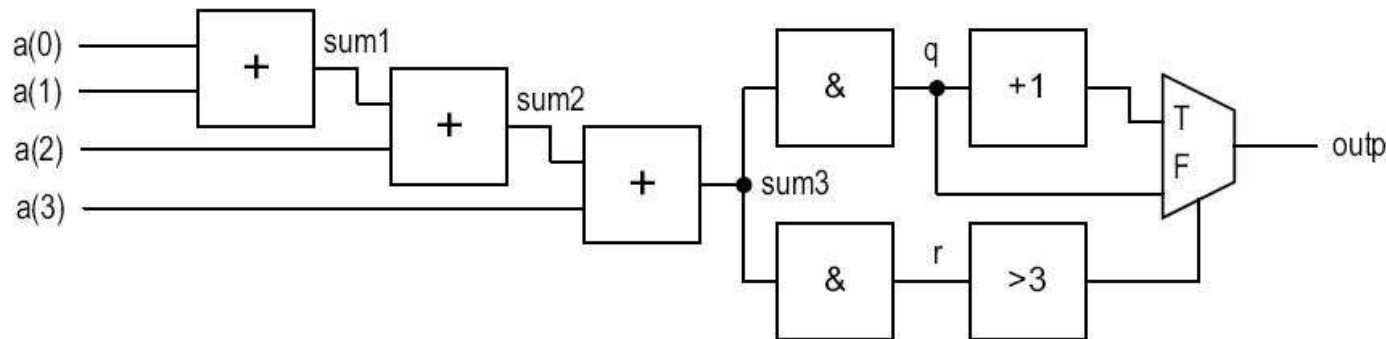

The problem is the *structural data flow* implementation is that it can only be applied to trivial problems and is not flexible (is specific to an array of 4 values)

A better implementation is to *share* one adder in a time-multiplexed manner (as is done on a GPU)

Register Transfer Methodology introduces hardware that *matches* the variable and sequential execution model

- Registers are used to store intermediate data (model symbolic variables)
- A datapath is used to implement the operations
- A control path (FSM) is used to specify the order of register operations

FSMD

The control, data path and registers are implemented as an **FSMD** (FSM with a data-path)

FSMDs are key to realizing RT methodology

The basic action in RT methodology is the *register transfer operation*:

$$r_{\text{dest}} \leftarrow f(r_{\text{src1}}, r_{\text{src2}}, \dots, r_{\text{src3}})$$

The **destination** register is shown on the left while the **source** registers are listed on the right

The function f uses the contents of the source registers, plus external outputs in some cases

Difference between an algorithm and an RT register is the implicit embedding of clk

- At the rising edge of the clock, the output of registers $r_{\text{src1}}, r_{\text{src2}}$ become available
- The output are passed to a combinational circuit that represents $f()$
- At the **next rising edge** of the clock, the result is stored into r_{dest}

FSMD

The function $f()$ can be any expression that is representable by a combinational circuit

$$r \leftarrow 1$$

$$r \leftarrow r$$

$$r0 \leftarrow r1$$

$$n \leftarrow n - 1$$

$$y \leftarrow a \oplus b \oplus c \oplus d$$

$$s \leftarrow a^2 + b^2$$

Note that we will continue to use the notation $_reg$ and $_next$ for the current output and next input of a register

The notation

$$r_1 \leftarrow r_1 + r_2$$

is translated as

```
r1_next <= r1_reg + r2_reg;
```



```
r1_reg <= r1_next; -- on the next rising edge of clk
```

Block diagram and timing diagram are shown below

FSMD

Be sure to study this carefully because it is heavily used in digital systems

$$r \leftarrow r1 + r2$$

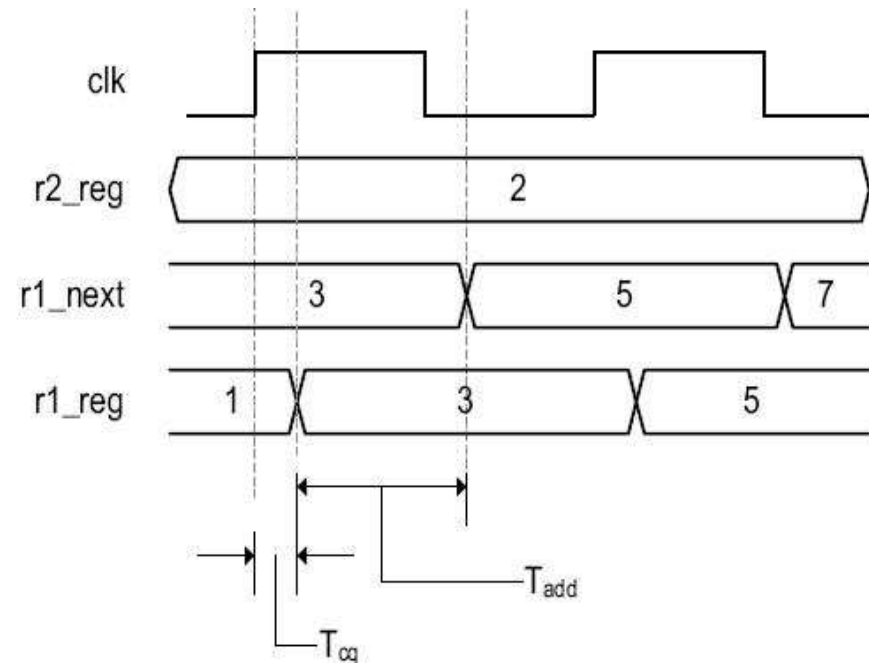 **Multiple RT operations**

An algorithm consists of many steps and a *destination* register may be loaded with different values over time, e.g., initialized to 0, stores result of addition, etc.


FSMD

Consider the following sequence of operations

$$r_1 \leftarrow 1$$

$$r_1 \leftarrow r_1 + r_2$$

$$r_1 \leftarrow r_1 + 1$$
 
$$r_1 \leftarrow r_1$$


Since r_1 is the destination of multiple operations, we need a MUX to route the proper value to its input

An FSM is used to drive the *control signals* so that the sequence of operations are carried out in the order given


The FSM can also implement *conditional* execution based, e.g., on external signals

FSMD

Note that the state transitions take place on the rising edge of *clk* -- the same instant that the RT registers are updated

So we can embed the RT operations within the state boxes/arcs of the FSM

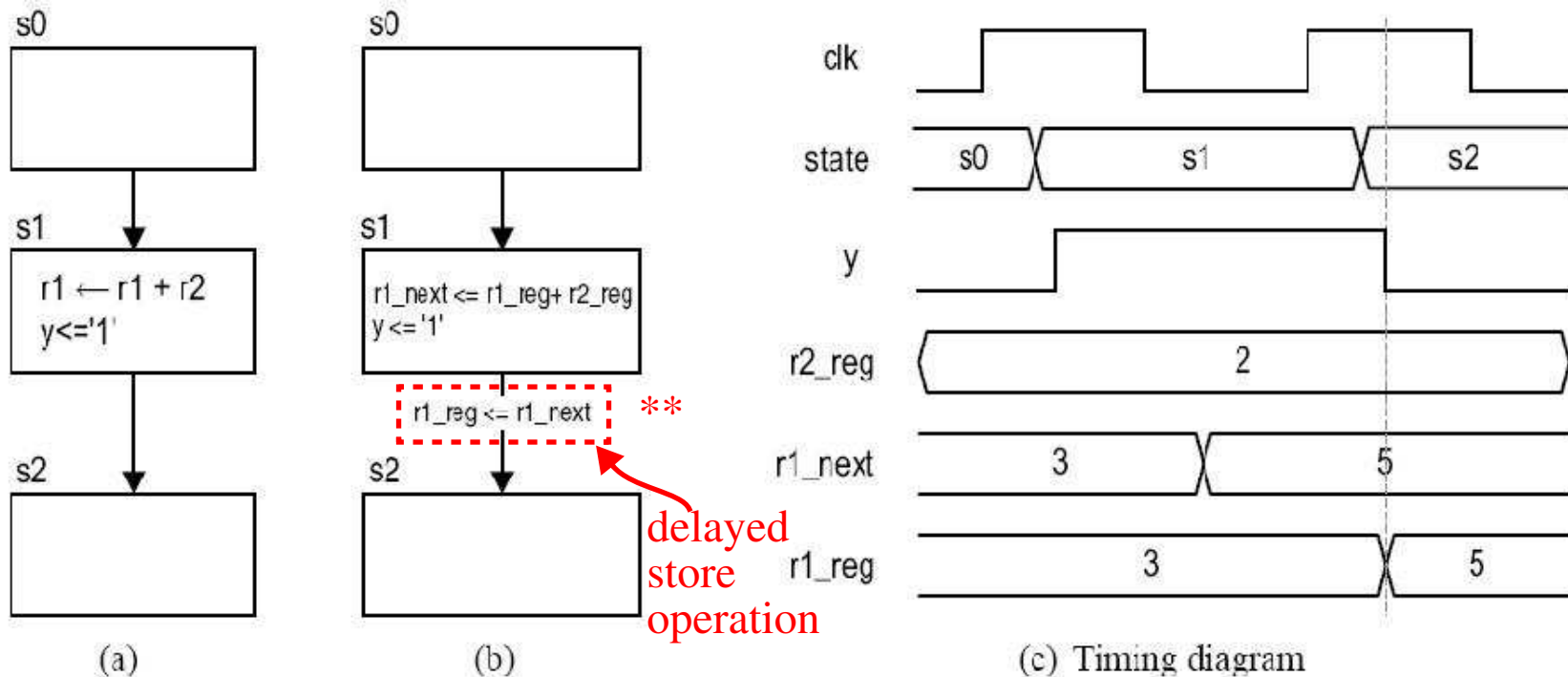An extended ASM chart known as **ASMD** (ASM with datapath) chart can be used to represent the FSMD




**** IMPORTANT:** the new value of r_1 is only available when the FSM exits the s_1 state

FSMD

NOTE: When a register is NOT being updated with a new value, it is assumed that it maintains its current value, i.e.,

$$r_1 \leftarrow r_1 \quad \text{These actions are NOT shown in the ASMD/state chart}$$

Conceptual block diagram of an FSMD

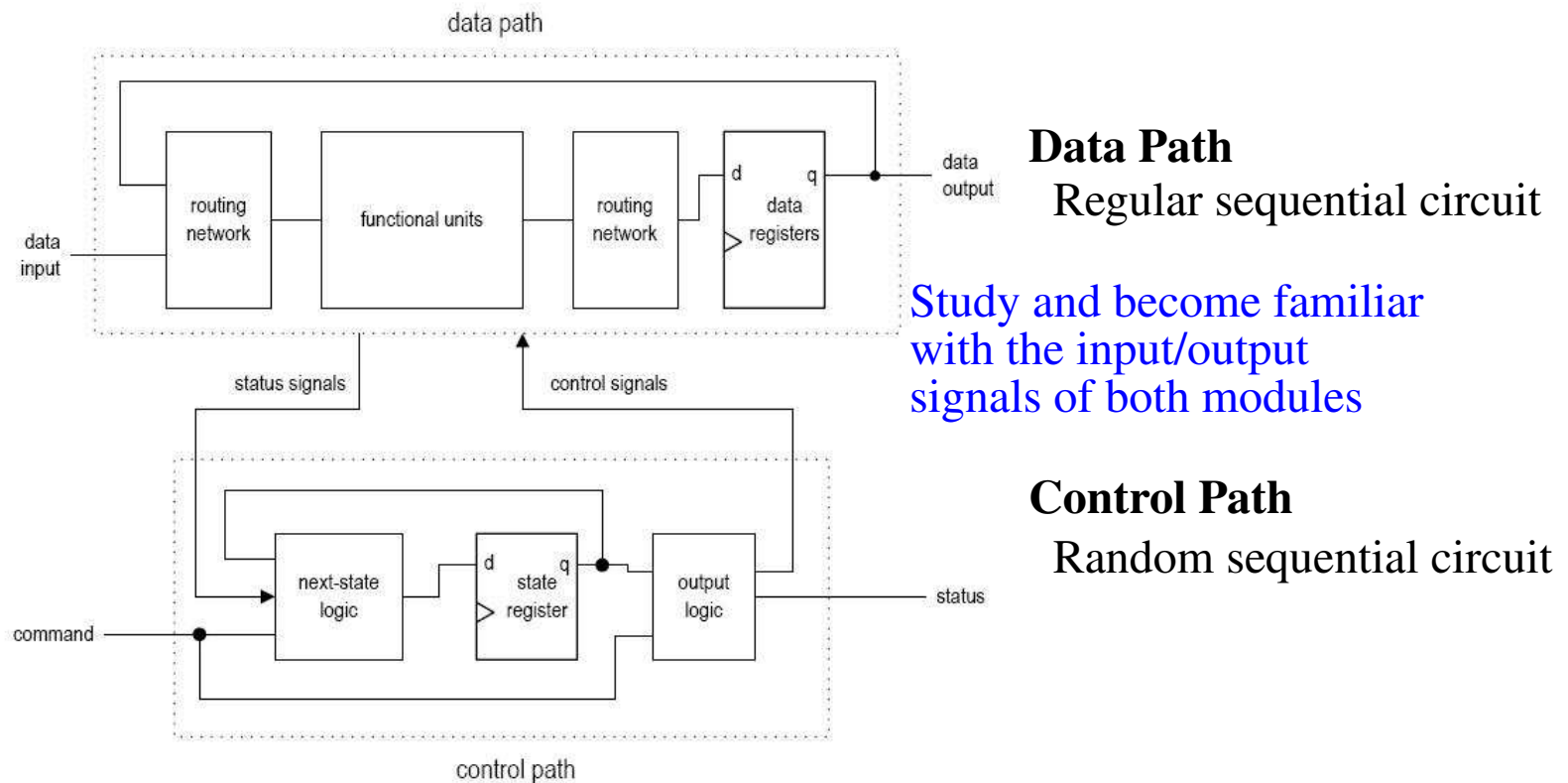

FSMD Design Examples

Repetitive addition multiplier

We built a combinational multiplier earlier which used multiple adders in a data-flow configuration

It's also possible to build it using one adder and a sequential algorithm

Basic algorithm: $7*5 = 7+7+7+7+7$

```
if (a_in=0 or b_in=0) then
    { r = 0; }
else
    {
    a = a_in;
    n = b_in;
    r = 0;
    while (n != 0)
        {
        r = r + a;
```

FSMD Design Examples

```
        n = n - 1;
    }
}
return(r);
```

This code is a better match to an ASMD because ASMD does not have a **loop** construct

```
if (a_in = 0 or b_in = 0) then
    { r = 0; }
else
    {
        a = a_in;
        n = b_in;
        r = 0;
op:   r = r + a;
        n = n - 1;
        if (n = 0) then
            { goto stop; }
```

FSMD Design Examples

```
        else
            { goto op; }
        }
stop: return(r);
```

To implement this in hardware, we must first define the I/O signals

- *a_in*, *b_in*: 8-bit unsigned input
- *clk*, *reset*: 1-bit input
- *start*: 1-bit command input
- *r*: 16-bit unsigned output
- *ready*: 1-bit status output -- asserted when unit has completed and is ready again


The *start* and *ready* signals are added to support sequential operation

When this unit is embedded in a larger design, and the main system wants to perform multiplication

- It checks *ready*
- If '1', it places inputs on *a_in* and *b_in* and asserts the *start* signal

FSMD Design Examples

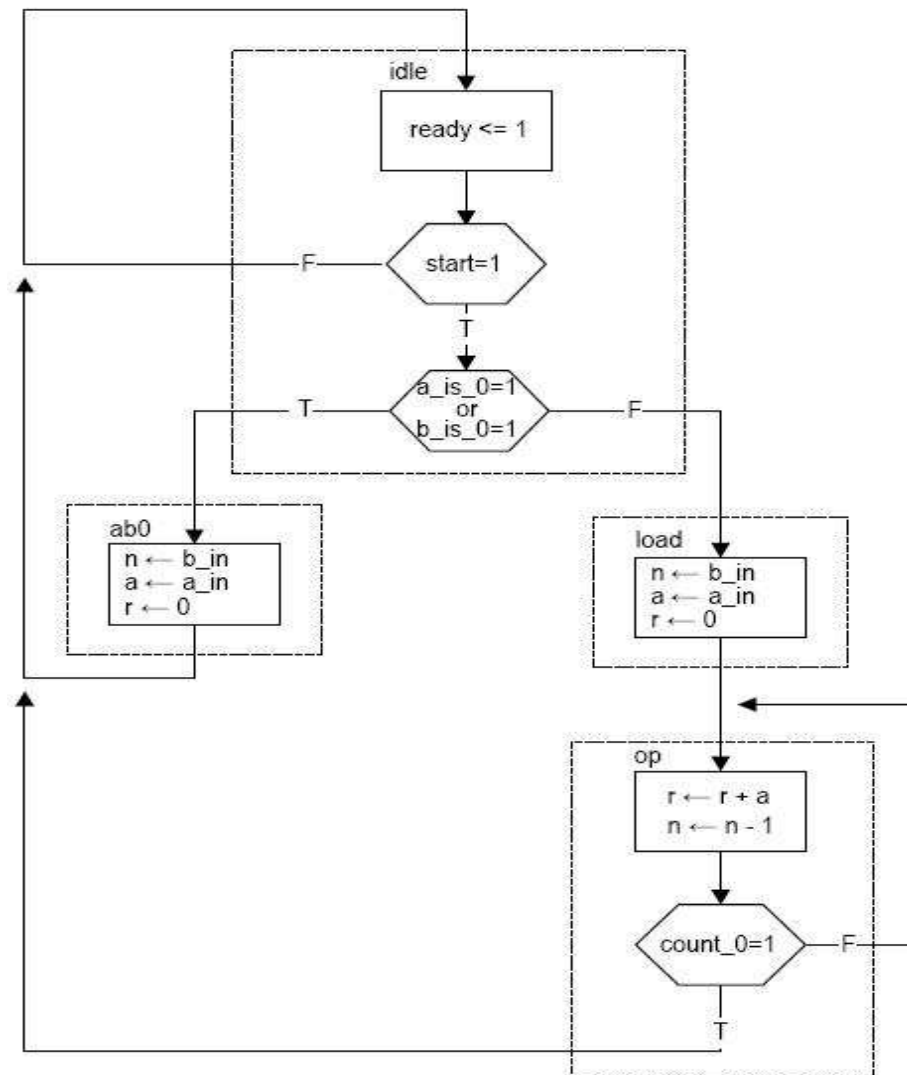The ASMD uses n , a and r data registers to emulate the three variables



Decision boxes are used to implement the *if stmts*

One difference between the pseudo code and the ASMD is the **parallelism** available in the latter

When RT operations are scheduled in the same state they execute in parallel in that clock cycle, e.g., *op state*

Multiple operations can be scheduled in the same state if enough hardware resources are available and there are **no** data dependencies

FSMD Design Examples

With the ASMD chart available, we can refine the original block diagram

We first divide the system into a *data path* and a *control path*

For the control path, the input signals are *start*, *a_is_0*, *b_is_0* and *count_0* -- the first is an external signal, the latter three are status signals from the data path

These signals constitute the inputs to the FSM and are used in the *decision boxes*

The output of the control path are *ready* and control signals that specify the RT operations of the data path

In this example, we use the state register as the output control signals

Construction of the data path is easier if it is handled as follows:

- List all RT operations
- Group RT operation according to the destination register
- Add combinational circuit/mux
- Add status circuits

FSMD Design Examples

For example

- RT operation with the r register

$r \leftarrow r$ (in the idle state)

$r \leftarrow 0$ (in the load and op states)

$r \leftarrow r + a$ (in the op state)

- RT operations with the n register

$n \leftarrow n$ (in the idle state)

$n \leftarrow b_in$ (in the load and ab0 state)

$n \leftarrow n - 1$ (in the op state)

- RT operations with the a register


$a \leftarrow a$ (in the idle and op states)

$a \leftarrow a_in$ (in the load and ab0 states)

Note that the **default** operations **MUST** be included to build the proper data path

FSMD Design Examples

 Let's consider the circuit associated with the r register



The three possible sources, 0 , r and $r+a$ are selected using a MUX

The select signals are labeled symbolically with the state names


The routing specified matches that given on the previous slide

We can repeat this process for the other two registers and combine them

The status signals are implemented using three comparators

FSMD Design Examples

The entire control and data path

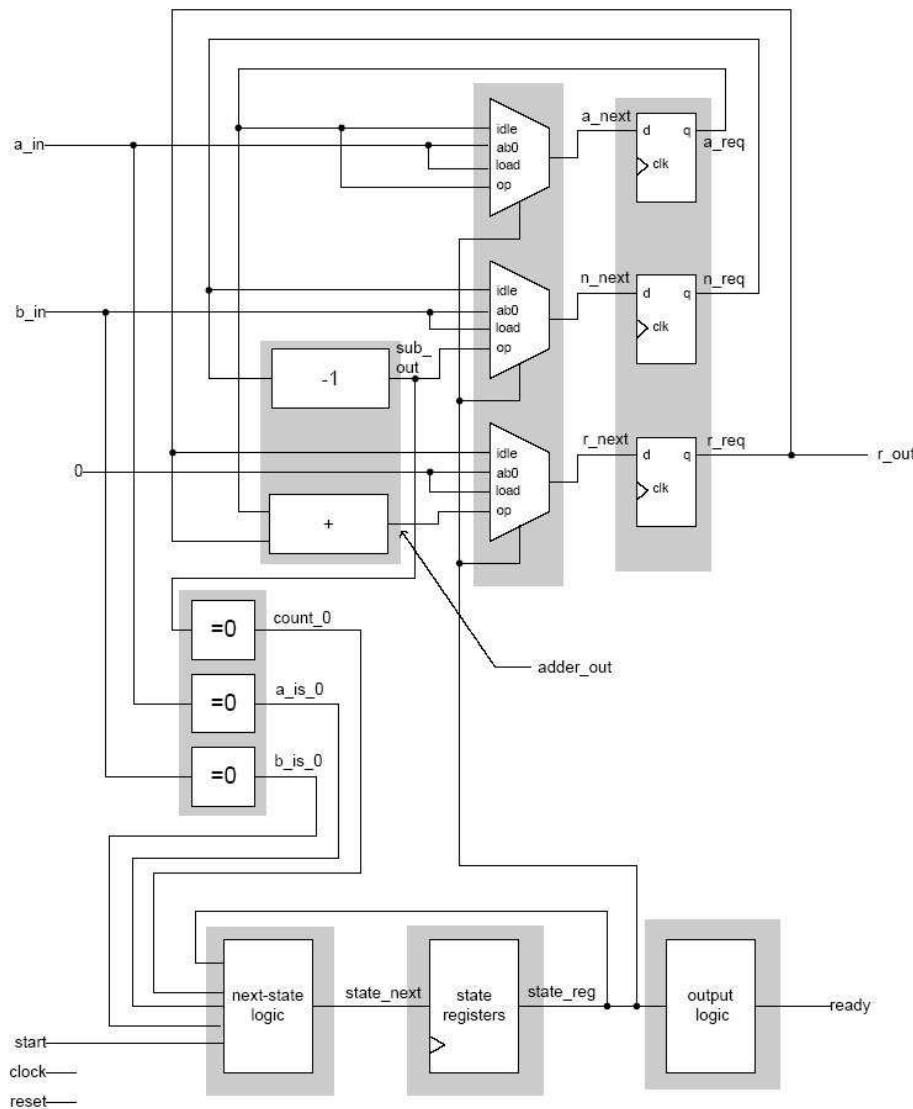

Note that some elements are more complicated than necessary

For example, the a_next signal can be replaced with a register with an *enable* signal

Don't worry, the synthesis tool will optimize this design

FSMD Design Examples

The VHDL code follows the block diagram and is divided into **seven** blocks

- Control path state registers
- Control path next-state logic
- Control path output logic
- Data path data registers
- Data path functional units
- Data path routing network
- Data path status circuit

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity seq_mult is  
  port (  
    clk, reset: in std_logic;  
    start: in std_logic;  
    a_in, b_in: in std_logic_vector(7 downto 0);
```

FSMD Design Examples

```
        ready: out std_logic;  
        r: out std_logic_vector(15 downto 0)  
    );  
end seq_mult;
```

```
architecture mult_seg_arch of seq_mult is  
    constant WIDTH: integer:=8;  
    type state_type is (idle, ab0, load, op);  
    signal state_reg, state_next: state_type;  
    signal a_is_0, b_is_0, count_0: std_logic;  
    signal a_reg, a_next: unsigned(WIDTH-1 downto 0);  
    signal n_reg, n_next: unsigned(WIDTH-1 downto 0);  
    signal r_reg, r_next: unsigned(2*WIDTH-1 downto 0);  
    signal adder_out: unsigned(2*WIDTH-1 downto 0);  
    signal sub_out: unsigned(WIDTH-1 downto 0);  
begin
```

FSMD Design Examples

```
-- control path: state register
process(clk, reset)
  begin
    if (reset = '1') then
      state_reg <= idle;
    elsif (clk'event and clk = '1') then
      state_reg <= state_next;
    end if;
  end process;

-- control path: next-state/output logic
process(state_reg, start, a_is_0, b_is_0, count_0)
  begin
    case state_reg is
      when idle =>
        if (start = '1') then
          if (a_is_0 = '1' or b_is_0 = '1') then
            state_next <= ab0;
```

FSMD Design Examples

```
        else
            state_next <= load;
        end if;
    else
        state_next <= idle;
    end if;
when ab0 =>
    state_next <= idle;
when load =>
    state_next <= op;
when op =>
    if (count_0 = '1') then
        state_next <= idle;
    else
        state_next <= op;
    end if;
end case;
end process;
```

FSMD Design Examples

```
-- control path: output logic
ready <= '1' when state_reg=idle else '0';

-- data path: data register
process(clk, reset)
  begin
    if (reset = '1') then
      a_reg <= (others=>'0');
      n_reg <= (others=>'0');
      r_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      a_reg <= a_next;
      n_reg <= n_next;
      r_reg <= r_next;
    end if;
  end process;
```

FSMD Design Examples

```
-- data path: routing multiplexer
process(state_reg, a_reg, n_reg, r_reg,
        a_in, b_in, adder_out, sub_out)
begin
  case state_reg is
    when idle =>
      a_next <= a_reg;
      n_next <= n_reg;
      r_next <= r_reg;
    when ab0 =>
      a_next <= unsigned(a_in);
      n_next <= unsigned(b_in);
      r_next <= (others => '0');
    when load =>
      a_next <= unsigned(a_in);
      n_next <= unsigned(b_in);
      r_next <= (others => '0');
    when op =>
```


FSMD Design Examples

```
        a_next <= a_reg;
        n_next <= sub_out;
        r_next <= adder_out;
    end case;
end process;

-- data path: functional units
adder_out <= ("00000000" & a_reg) + r_reg;
sub_out <= n_reg - 1;

-- data path: status
a_is_0 <= '1' when a_in = "00000000" else '0';
b_is_0 <= '1' when b_in = "00000000" else '0';
count_0 <= '1' when n_next = "00000000" else '0';

-- data path: output
r <= std_logic_vector(r_reg);
end mult_seg_arch;
```

Use of a Register Value in a Decision Box

Most of the translation process is straightforward

One caveat is using a **register** in a Boolean expression of a decision box

This was avoided in our example by using *a_is_0*, *b_is_0* and *count_0* status signals inside the decision boxes

A more descriptive way is to use registers and input signals in the Boolean exprs.

For example, instead of *a_is_0 = 1*, we could use *a_in = 0*

A second example is to (try to) use the *n* register in the loop termination decision box
Unfortunately, we need to be careful here because the new value of *n* is **not available** until we exit the block


Therefore, the ASMD must differ from the pseudo-code shown earlier

```
n = n - 1;  
if ( n = 0 ) then ...
```

Use of a Register Value in a Decision Box

In the ASMD, the **old** value of n would be used in the decision box and one **extra** iteration would occur (which is **INcorrect**)

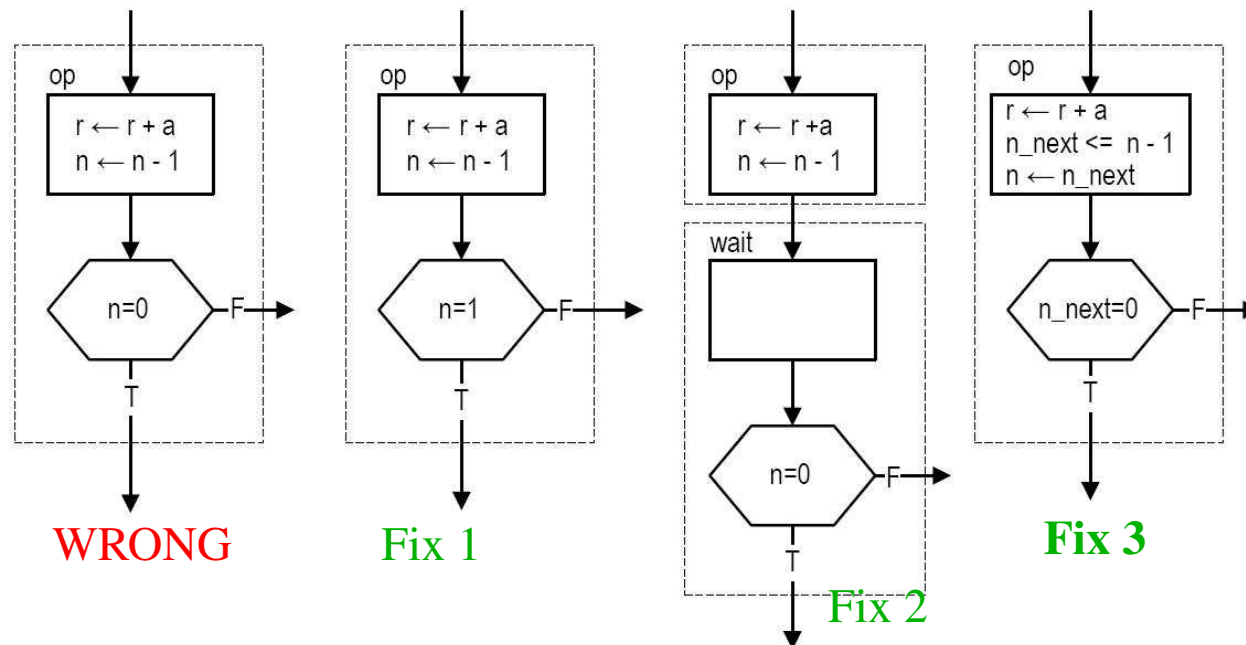One way to fix this problem is to use the condition of the previous iteration, e.g., $n = 1$ to terminate the loop (see below **Fix 1**)



Unfortunately, it is less clear what the intention is

Fix 2 adds a *wait* state -- this fixes the problem but is **clumsy** and **inefficient**

Use of a Register Value in a Decision Box

The best fix (**Fix 3**) is to use the *next value* in the Boolean expression

Since the next value is calculated during the *op* state, it is available at the end of the clock cycle and can be used in the *decision box*

Note that the VHDL code given actually uses the *n_next* signal

```
count_0 <= '1' when n_next = 0 else '0';
```

To express this in the ASMD chart, we have to split the RT operation

$$r \leftarrow f(.)$$

into two parts

```
r_next <= f(.)  
r ← r_next;
```

Here, the first part indicates that the next value of the *r* register is calculated and updated within the **current clk cycle**

See **Fix 3** for an example using the *n_next* signal

This is best b/c it is consistent with the pseudo-code and has no performance penalty

Two Segment VHDL Descriptions of FSMs

The previous 7 segment coding style can be easily reduced to two segments

```
architecture two_seg_arch of seq_mult is
  constant WIDTH: integer := 8;
  type state_type is (idle, ab0, load, op);
  signal state_reg, state_next: state_type;
  signal a_reg, a_next: unsigned(WIDTH-1 downto 0);
  signal n_reg, n_next: unsigned(WIDTH-1 downto 0);
  signal r_reg, r_next: unsigned(2*WIDTH-1 downto 0);
begin

  -- state and data register
  process(clk, reset)
    begin
      if (reset = '1') then
        state_reg <= idle;
        a_reg <= (others => '0');
        n_reg <= (others => '0');
        r_reg <= (others => '0');
```

Two Segment VHDL Descriptions of FSMDs

```
    elsif (clk'event and clk = '1') then
        state_reg <= state_next;
        a_reg <= a_next;
        n_reg <= n_next;
        r_reg <= r_next;
    end if;
end process;

-- combinational circuit
process(start, state_reg, a_reg, n_reg, r_reg, a_in,
        b_in, n_next)
begin

    -- default value
    a_next <= a_reg;
    n_next <= n_reg;
    r_next <= r_reg;
    ready <= '0';
```

Two Segment VHDL Descriptions of FSMs

```
case state_reg is
  when idle =>
    if (start = '1') then
      if (a_in = "00000000" or
          b_in = "00000000") then
        state_next <= ab0;
      else
        state_next <= load;
      end if;
    else
      state_next <= idle;
    end if;
  ready <= '1';
when ab0 =>
  a_next <= unsigned(a_in);
  n_next <= unsigned(b_in);
  r_next <= (others => '0');
  state_next <= idle;
```

Two Segment VHDL Descriptions of FSMs

```
    when load =>
        a_next <= unsigned(a_in);
        n_next <= unsigned(b_in);
        r_next <= (others => '0');
        state_next <= op;
    when op =>
        n_next <= n_reg - 1;
        r_next <= ("00000000" & a_reg) + r_reg;
        if (n_next = "00000000") then
            state_next <= idle;
        else
            state_next <= op;
        end if;
    end case;
end process;
r <= std_logic_vector(r_reg);
end two_seg_arch;
```


One Segment VHDL Descriptions of FSMs

Although possible, combining everything into one segment may introduce subtle problems and is not recommended

```
architecture one_seg_arch of seq_mult is
  constant WIDTH: integer := 8;
  type state_type is (idle, ab0, load, op);
  signal state_reg: state_type;
  signal a_reg, n_reg: unsigned(WIDTH-1 downto 0);
  signal r_reg: unsigned(2*WIDTH-1 downto 0);
begin

  process(clk, reset)
    variable n_next: unsigned(WIDTH-1 downto 0);
    begin
      if (reset = '1') then
        state_reg <= idle;
        a_reg <= (others => '0');
        n_reg <= (others => '0');
        r_reg <= (others => '0');
      end if;
    end process;
  end architecture one_seg_arch;
```

One Segment VHDL Descriptions of FSMs

```
elsif (clk'event and clk = '1') then
  case state_reg is
    when idle =>
      if (start = '1') then
        if (a_in = "00000000" or
          b_in = "00000000") then
          state_reg <= ab0;
        else
          state_reg <= load;
        end if;
      end if;
    when ab0 =>
      a_reg <= unsigned(a_in);
      n_reg <= unsigned(b_in);
      r_reg <= (others => '0');
      state_reg <= idle;
    when load =>
      a_reg <= unsigned(a_in);
```

One Segment VHDL Descriptions of FSMs

```
n_reg <= unsigned(b_in);
r_reg <= (others => '0');
state_reg <= op;

when op =>
    n_next := n_reg - 1;
    n_reg <= n_next;
    r_reg <= ("00000000" & a_reg) + r_reg;
    if (n_next = "00000000") then
        state_reg <= idle;
    end if;
end case;
end if;
end process;

ready <= '1' when (state_reg = idle) else '0';
r <= std_logic_vector(r_reg);
end one_seg_arch;
```

One Segment VHDL Descriptions of FSMs

There are several subtle problems

- Since a **register** is inferred for ANY signal within the clause

elsif (clk'event **and** clk = '1') **then**

the *next* value of a data register CANNOT be referred by a signal

To overcome this, we must define *n_next* as a **variable** for immediate assignment

- To avoid the unnecessary output buffer, the *ready* output signal has to be moved outside the process and be coded as a separate segment

Alternative Design of a Repetitive-Addition Multiplier


We discussed combinational **resource sharing** earlier

Since FSM allows RT operations to be scheduled, sharing can be achieved in a **time-multiplexing** fashion by assigning the same functional unit in different states

In the repetitive addition multiplier example, the *addition* and *decrement* operation can share a functional unit if they are placed in different states


Alternative Design of a Repetitive-Addition Multiplier

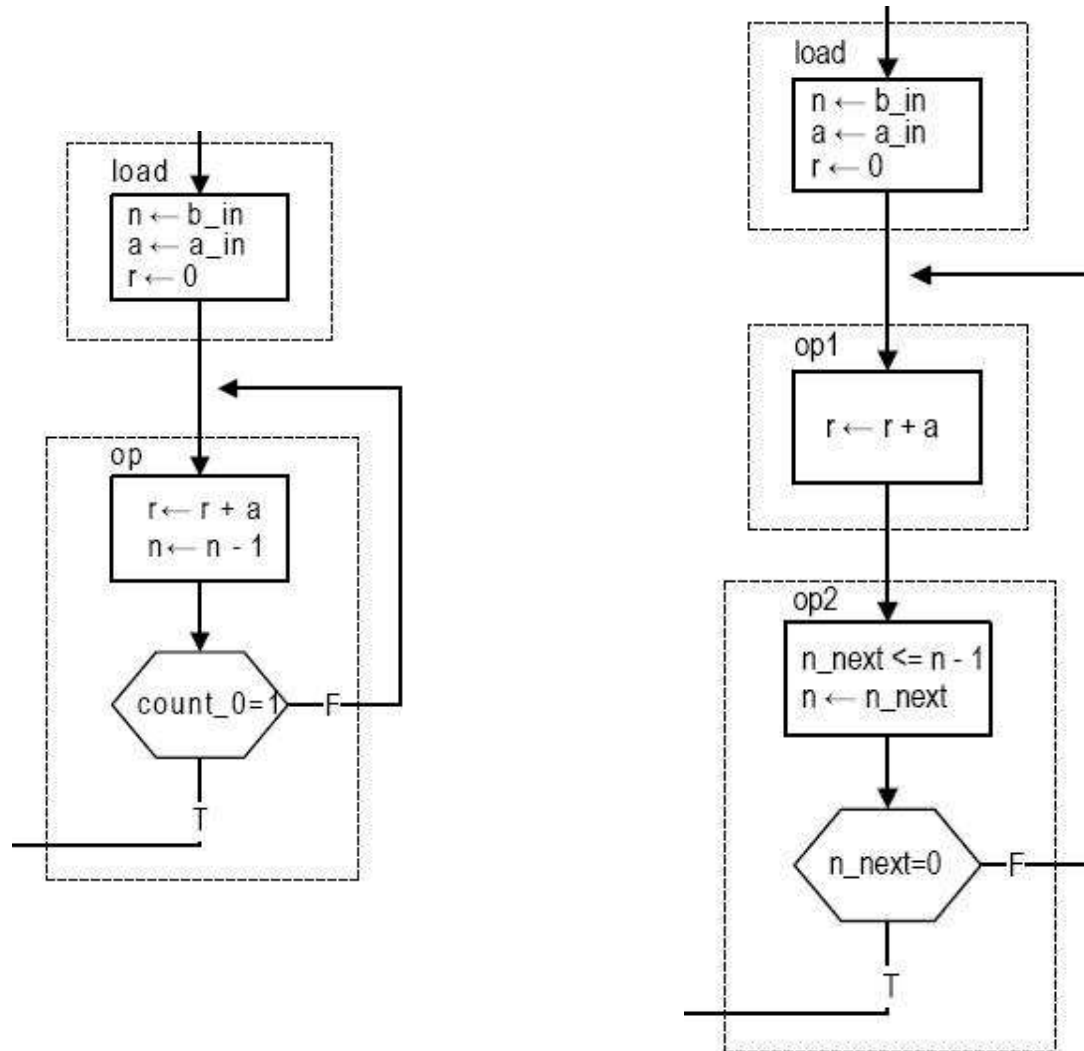This requires the *op* state to be split into *op1* and *op2* as shown below



Alternative Design of a Repetitive-Addition Multiplier

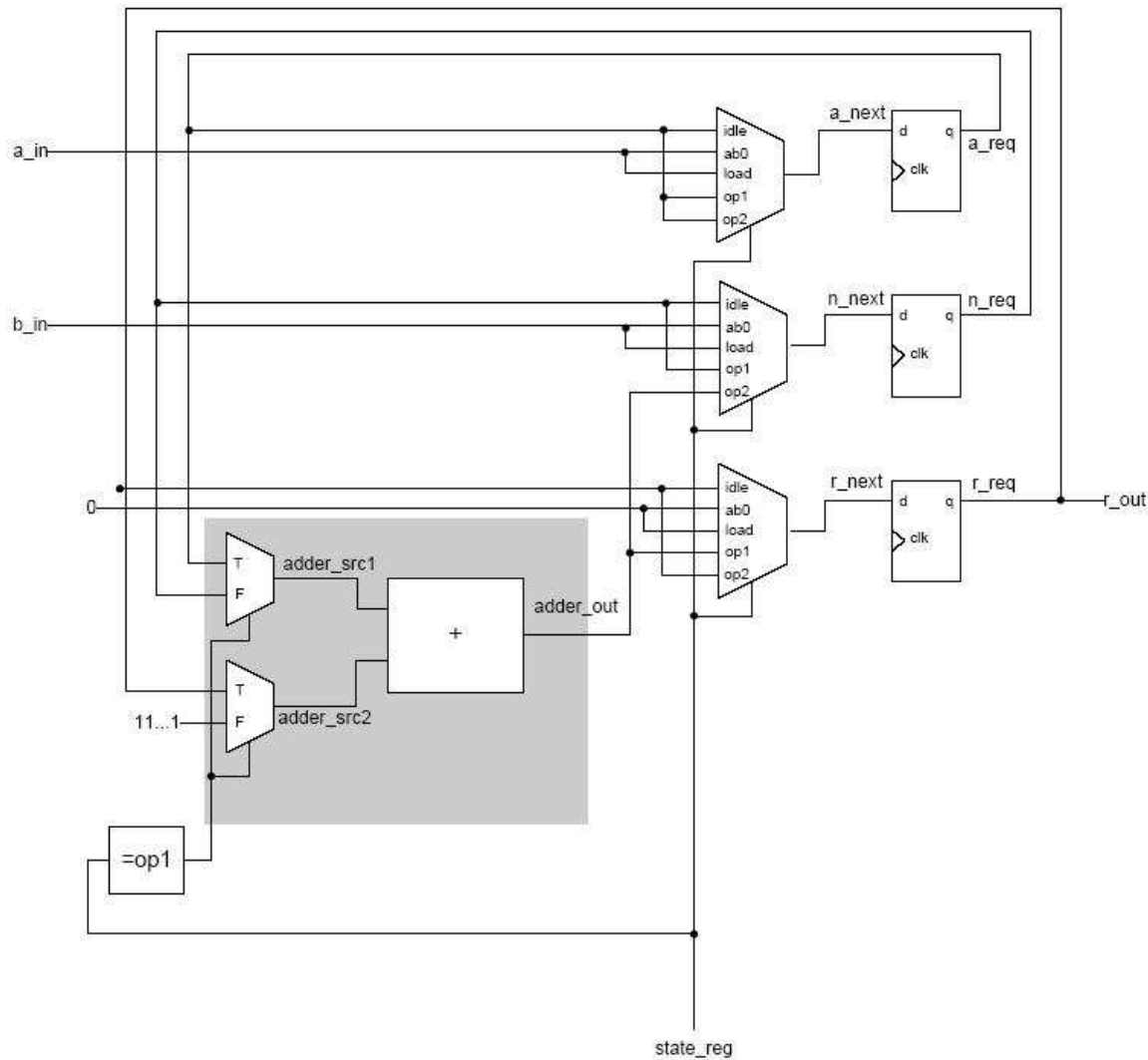The revised data path uses an additional multiplexer



Alternative Design of a Repetitive-Addition Multiplier

The following code makes explicit the sharing of the functional unit, given the limitations of RT-level optimization within synthesis tools

```
architecture sharing_arch of seq_mult is
  constant WIDTH: integer := 8;
  type state_type is (idle, ab0, load, op1, op2);
  signal state_reg, state_next: state_type;
  signal a_reg, a_next: unsigned(WIDTH-1 downto 0);
  signal n_reg, n_next: unsigned(WIDTH-1 downto 0);
  signal r_reg, r_next: unsigned(2*WIDTH-1 downto 0);
  signal adder_src1, adder_src2:
    unsigned(2*WIDTH-1 downto 0);
  signal adder_out: unsigned(2*WIDTH-1 downto 0);
begin

  -- state and data registers
  process(clk, reset)
    begin
```

Alternative Design of a Repetitive-Addition Multiplier

```
if (reset = '1') then
    state_reg <= idle;
    a_reg <= (others => '0');
    n_reg <= (others => '0');
    r_reg <= (others => '0');
elsif (clk'event and clk = '1') then
    state_reg <= state_next;
    a_reg <= a_next;
    n_reg <= n_next;
    r_reg <= r_next;
end if;
end process;

-- next-state logic/output logic and data path routing
process(start, state_reg, a_reg, n_reg, r_reg, a_in,
        b_in, adder_out, n_next)
```


Alternative Design of a Repetitive-Addition Multiplier

```
begin
  -- default value
  a_next <= a_reg;
  n_next <= n_reg;
  r_next <= r_reg;
  ready <= '0';
case state_reg is
  when idle =>
    if (start = '1') then
      if (a_in = "00000000" or
        b_in="00000000") then
        state_next <= ab0;
      else
        state_next <= load;
      end if;
    else
      state_next <= idle;
    end if;
```

Alternative Design of a Repetitive-Addition Multiplier

```
    ready <= '1';  
    when ab0 =>  
        a_next <= unsigned(a_in);  
        n_next <= unsigned(b_in);  
        r_next <= (others => '0');  
        state_next <= idle;  
    when load =>  
        a_next <= unsigned(a_in);  
        n_next <= unsigned(b_in);  
        r_next <= (others => '0');  
        state_next <= op1;  
    when op1 =>  
        r_next <= adder_out;  
        state_next <= op2;  
    when op2 =>  
        n_next <= adder_out(WIDTH-1 downto 0);  
        if (n_next = "00000000") then  
            state_next <= idle;
```

Alternative Design of a Repetitive-Addition Multiplier

```
        else
            state_next <= op1;
        end if;
    end case;
end process;

-- data path input routing and functional units
-- Note the n register is only 8-bits wide
process(state_reg, r_reg, a_reg, n_reg)
begin
    if (state_reg = op1) then
        adder_src1 <= r_reg;
        adder_src2 <= "00000000" & a_reg;
    else -- for op2 state
        adder_src1 <= "00000000" & n_reg;
        adder_src2 <= (others => '1');
    end if;
end process;
```

Alternative Design of a Repetitive-Addition Multiplier

```


adder_out <= adder_src1 + adder_src2;

-- output
r <= std_logic_vector(r_reg);
end sharing_arch;


```

Mealy-Controlled RT Operation

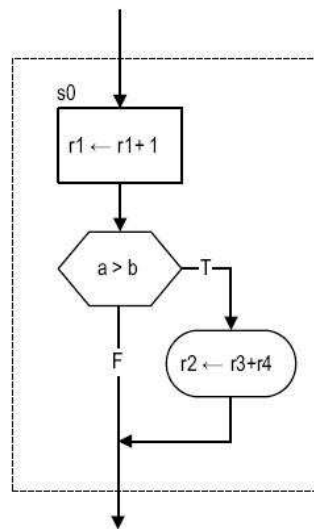The control signals connected to the data path are edge-sensitive, and therefore Mealy outputs can be used (they are faster and require fewer states)



(a) ASMD block

 

(b) Conceptual block diagram

Mealy-Controlled RT Operation

As shown, RT operations can appear in the conditional output box of an ASMD chart

$$r_2 \leftarrow r_3 + r_4$$

Note that this result is computed in parallel with the Moore output (r_1) and the comparison $a > b$

However, for the Moore output, there is only one possible outcome (r_1 is assigned $r_1 + 1$)

For the Mealy output, a MUX is added to select r_2 or $r_3 + r_4$ to store in r_2


For the original ASMD chart for the multiplier, the a_in and b_in signals are used in **both** the *idle* state (for comparison) and the *load* and *ab0* states for loading

This requires the external system that 'calls' the multiplier to hold the a_in and b_in signals for two clock cycles

The following modification to the ASMD uses Mealy-controlled RT operations to eliminate the two clock cycle requirement by merging *ab0* and *load* states to *idle*

Mealy-Controlled RT Operation

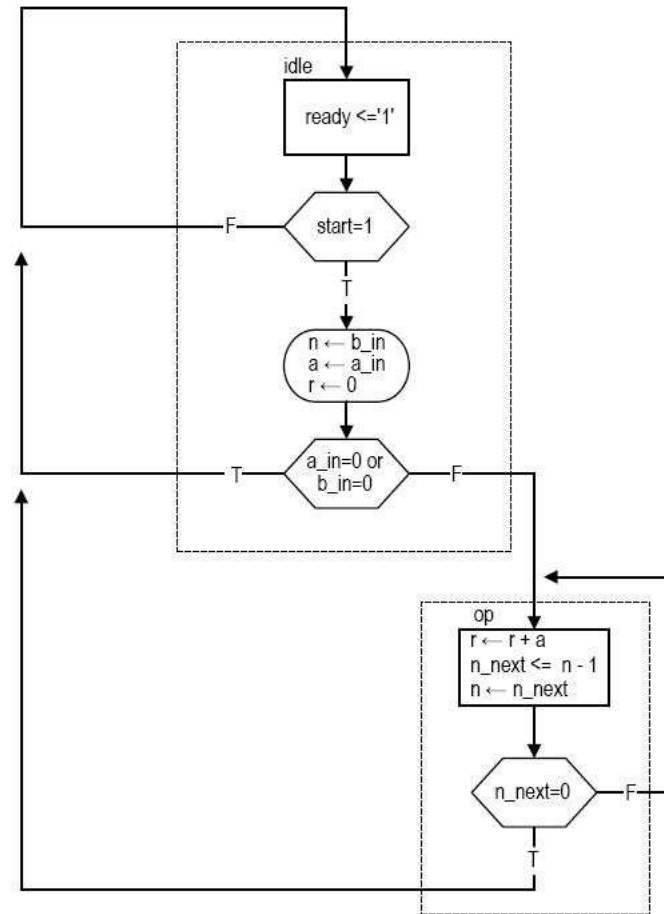The RT operations are **moved** into a *conditional output box*



Note that this change reduces the number of states from 4 to 2 and improves the performance

Mealy-Controlled RT Operation

```
architecture mealy_arch of seq_mult is
  constant WIDTH: integer := 8;
  type state_type is (idle, op);
  signal state_reg, state_next: state_type;
  signal a_reg, a_next: unsigned(WIDTH-1 downto 0);
  signal n_reg, n_next: unsigned(WIDTH-1 downto 0);
  signal r_reg, r_next: unsigned(2*WIDTH-1 downto 0);
begin

  -- state and data registers
  process(clk, reset)
    begin
      if (reset = '1') then
        state_reg <= idle;
        a_reg <= (others => '0');
        n_reg <= (others => '0');
        r_reg <= (others => '0');
```

Mealy-Controlled RT Operation

```
        elsif (clk'event and clk = '1') then
            state_reg <= state_next;
            a_reg <= a_next;
            n_reg <= n_next;
            r_reg <= r_next;
        end if;
    end process;

-- combinational circuit
process(start, state_reg, a_reg, n_reg, r_reg, a_in,
        b_in, n_next)
    begin
        a_next <= a_reg;
        n_next <= n_reg;
        r_next <= r_reg;
        ready <= '0';
    end process;
```


Mealy-Controlled RT Operation

```
case state_reg is
  when idle =>
    if (start = '1') then
      a_next <= unsigned(a_in);
      n_next <= unsigned(b_in);
      r_next <= (others => '0');
      if (a_in = "00000000" or
          b_in = "00000000") then
        state_next <= idle;
      else
        state_next <= op;
      end if;
    else
      state_next <= idle;
    end if;
  ready <= '1';
```

Mealy-Controlled RT Operation

```
    when op =>
        n_next <= n_reg - 1;
        r_next <= ("00000000" & a_reg) + r_reg;
        if (n_next = "00000000") then
            state_next <= idle;
        else
            state_next <= op;
        end if;
    end case;
end process;

r <= std_logic_vector(r_reg);
end mealy_arch;
```

Clock Rate and Performance of FSMD

The maximum clk rate of an FSMD is bounded by the setup time constraint, as it was in our earlier analysis

Clock Rate and Performance of FSMD

Unfortunately, an FSMD is more difficult to analyze because of the interaction between the control and data path loops

The interaction occurs by virtue of the *control* signals that control the data path, and the *status* signals generated by the data path

The exact value depends on where the *control* signals are needed and where the *status* signals are generated

Although software is needed to determine the exact maximum clock rate, it is possible, however, to establish a bound by considering *best* and *worst* case scenarios

The timing parameters for the **control** path are the same as those discussed earlier for an FSM

- $T_{cq(state)}$
- $T_{setup(state)}$
- T_{next} (max delay of next state logic)
- T_{output} (max delay of output logic)


Clock Rate and Performance of FSM

The timing parameters for the **data** path are as follows

- $T_{cq(data)}$
- $T_{setup(data)}$
- T_{func} (max delay of functional units -- likely to be the largest)
- T_{route} (max delay of routing MUXes)
- T_{dp} (max delay of combo logic in data path -- sum of T_{func} and $2 * T_{route}$)


T_c is use for the clock period

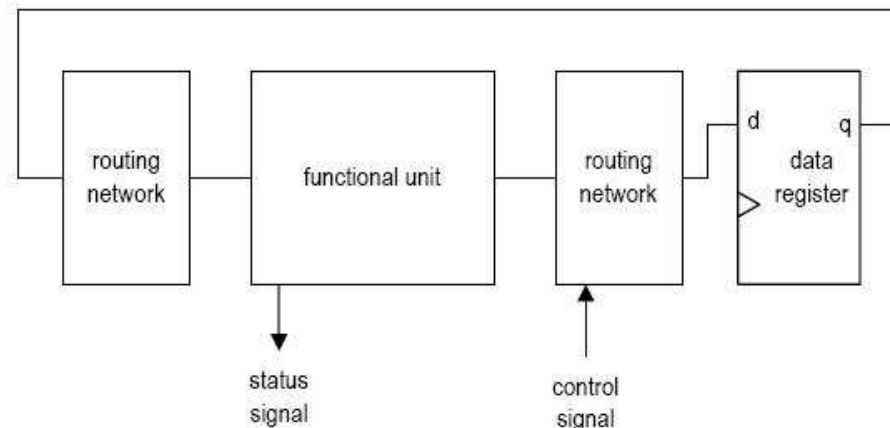In the best-case scenario, the **control signals** are needed at late stage in a data path operation and the **status signals** are generated in an early stage



Clock Rate and Performance of FSM

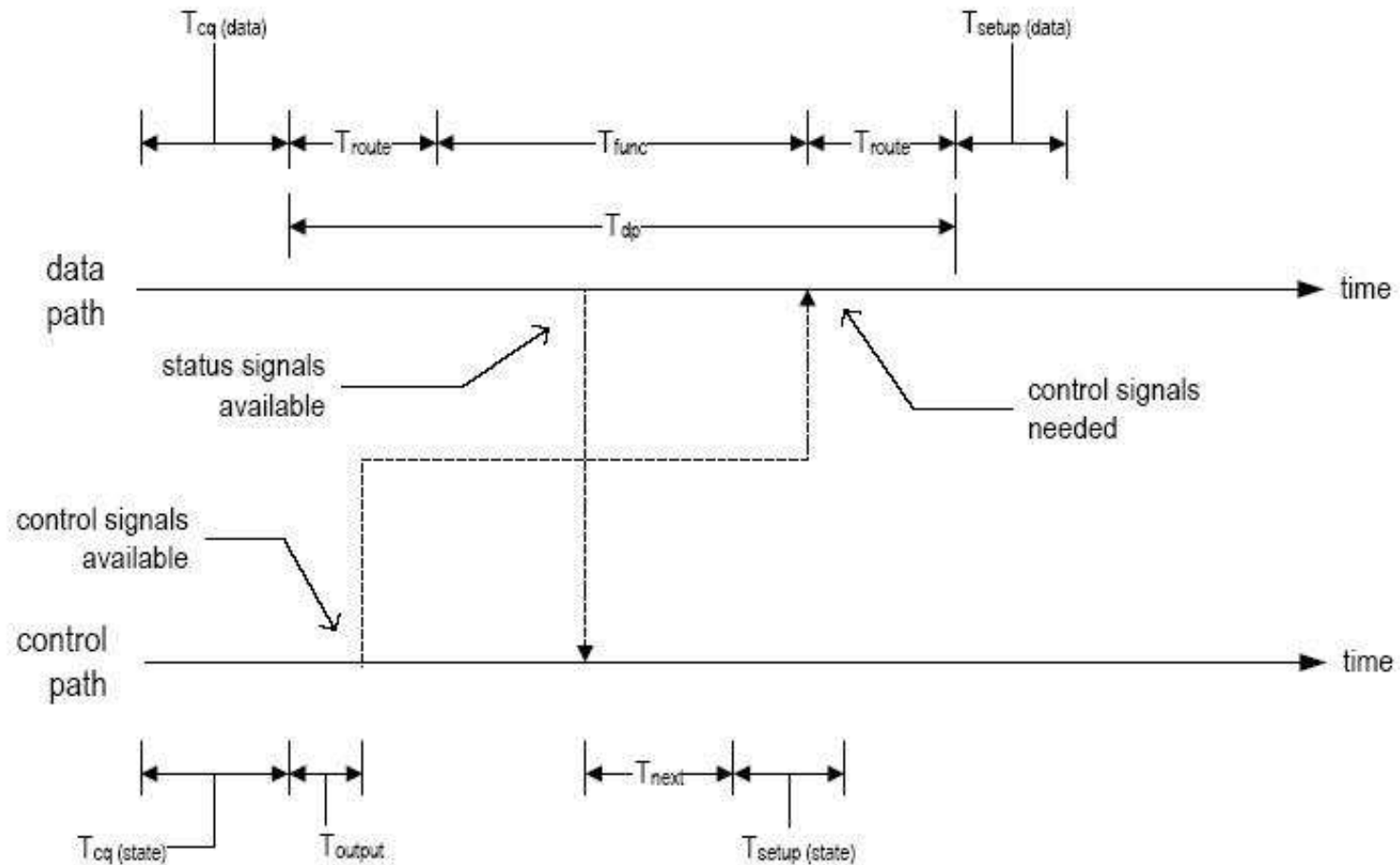The time line under the best case scenario




The **minimum clock period** of the FSM is the same as the clock period of the *data path*

$$T_c = T_{cq}(data) + T_{dp} + T_{setup}(data)$$

Clock Rate and Performance of FSMD

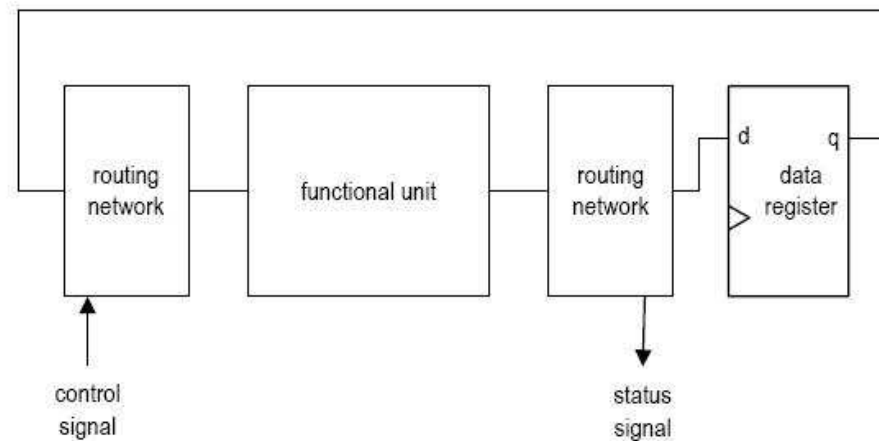The **worst-case scenario** occurs when the *control signals* are needed at early stage and the *status signals* available at late stage



Here, the data path **MUST** wait for the FSM to generate the output signals


And the control path **MUST** wait for the status signals to generate the next-state value

Except for the registers, there is **no overlap** between the control path and data path
(see next slide)

The minimum clk period is the delay of **all** combinational components

Clock Rate and Performance of FSM

Time line of **worst case** scenario

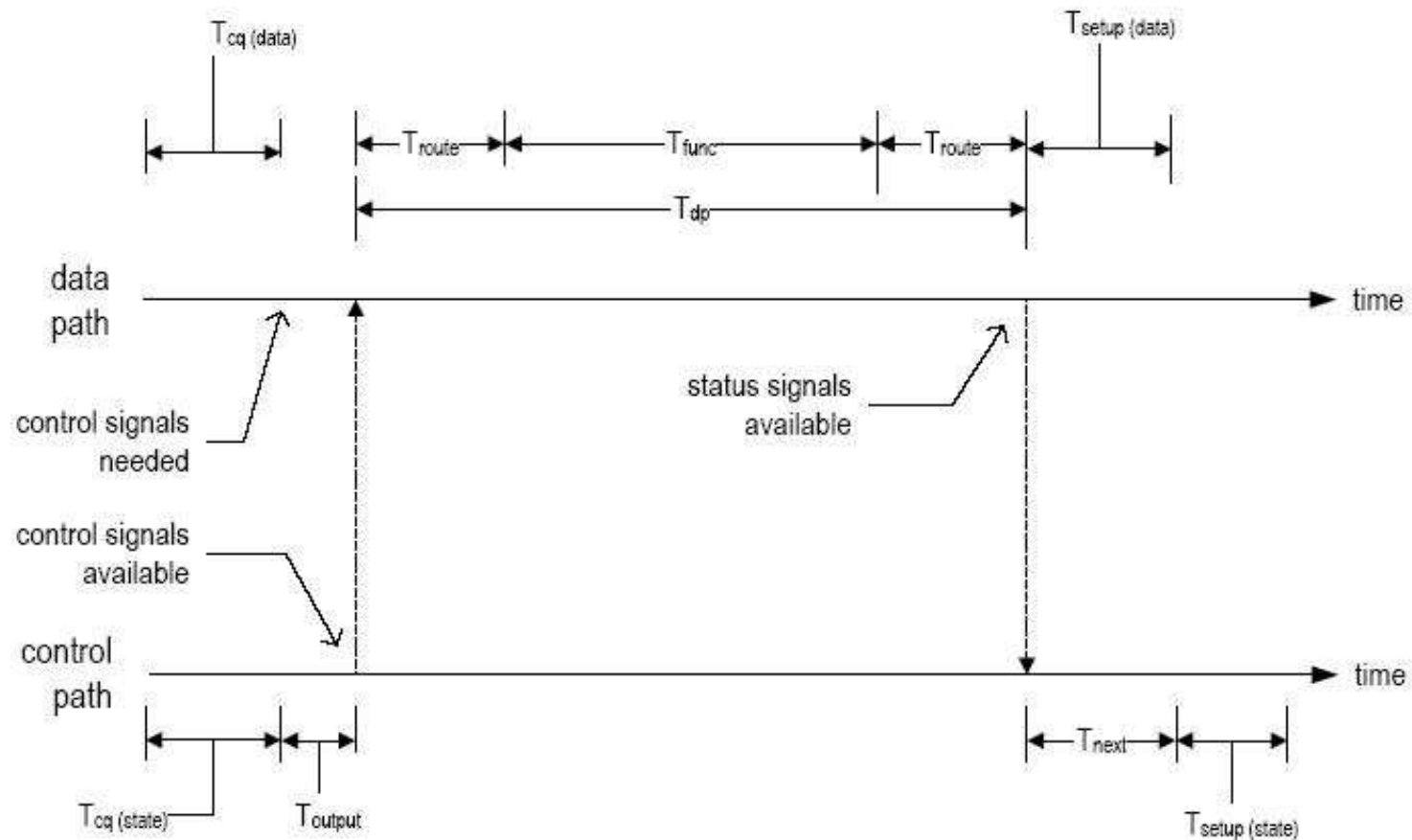

Worst case timing

$$T_c = T_{cq(\text{state})} + T_{\text{output}} + T_{dp} + T_{\text{next}} + T_{\text{setup}(\text{state})}$$

Clock Rate and Performance of FSMD

From these two extreme scenarios, we can establish the timing bounds (assuming the *state* register and *data* register have similar timing characteristics)

$$T_{cq} + T_{dp} + T_{setup} \leq T_c \leq T_{cq} + T_{output} + T_{dp} + T_{next} + T_{setup}$$

Bounds on the **maximum clk frequency** are given by

$$1 / (T_{cq} + T_{output} + T_{dp} + T_{next} + T_{setup}) \leq f \leq 1 / (T_{cq} + T_{dp} + T_{setup})$$

For a design with a complex *data* path, T_{dp} will be much larger than T_{next} and T_{output} and therefore the difference between the min and max bound is small

For a design with a complex *control* path, we need to minimize T_{next} and T_{output} to maximize performance, and therefore, we need to isolate and optimize the FSM

Performance of FSM

The computation performed by an FSM usually takes many clk cycles (K) to complete, and is given by

$$\text{Total time} = K * T_c$$

The value K is determined by the algorithm, input patterns etc.

There are usually trade-offs associated with K and T_c

For example, it is usually possible to **merge** computation steps, reducing the number of states but increasing T_c because of the larger T_{dp}

On the other hand, it is also possible to divide an operation into smaller steps, reducing T_c but increasing K (the number of steps)

Consider the multiplier, where b_{in} is an 8-bit input

Best case: $b_{in} = 0 \Rightarrow K = 2$

Worst case: $b_{in} = 255 \Rightarrow K = 257$

For an n -bit input:

Worst: $K = 2 + (2^n - 1)$ (2 is for the *idle* and *load* states)

Sequential Add-and-Shift Multiplier

The fact that this multiplication algorithm is proportional to 2^n makes it impractical

A better algorithm: *sequential add-and-shift* multiplier

\times		a_3	a_2	a_1	a_0	multiplicand			
		b_3	b_2	b_1	b_0	multiplier			
			a_3b_0	a_2b_0	a_1b_0	a_0b_0			
			a_3b_1	a_2b_1	a_1b_1	a_0b_1			
		a_3b_2	a_2b_2	a_1b_2	a_0b_2				
$+$	a_3b_3	a_2b_3	a_1b_3	a_0b_3					
	y_7	y_6	y_5	y_4	y_3	y_2	y_1	y_0	product

The algorithm involves three tasks:

- Multiply the digits of the multiplier (b_3, b_2, b_1 and b_0) by the multiplicand (A) one at a time to obtain $b_3 \cdot A, b_2 \cdot A, b_1 \cdot A$ and $b_0 \cdot A$.

The $b_i \cdot A$ operation is bitwise, and defined as

$$b_i \cdot A = (a_3 \cdot b_i, a_2 \cdot b_i, a_1 \cdot b_i, a_0 \cdot b_i)$$

Sequential Add-and-Shift Multiplier

- Shift $b_i * A$ to the left by i positions according to the position of digits b_i
- Add the shifted $b_i * A$ to obtain the final product

```
n = 0;
p = 0;
while (n != 8)
{
  if (b_in(n) = 1) then
    { p = p + (a_in << n); }
  n = n + 1;
}
return (p);
```

In hardware, it is expensive to do *indexing*, i.e., $b_in(n)$ and to build a generic shifter, i.e., $a_in \ll n$

Instead, we can carry out an equivalent operation by shifting a_in and b_in by one position in each iteration

Sequential Add-and-Shift Multiplier

We also count down n to remove the constant dependency and allow for a generic operand width

```
a = a_in;
b = b_in;
n = 8;
p = 0;

while (n != 0)
{
  if (b(0) = 1 )
    { p = p + a; }
  a = a << 1;
  b = b >> 1;
  n = n - 1;
}

return (p);
```

Sequential Add-and-Shift Multiplier

Last, we convert the while loop to an *if* and *goto* stmt

```
a = a_in;
```

```
b = b_in;
```

```
n = 8;
```

```
p = 0;
```

```
op: if (b(0) = 1) then
```

```
    { p = p + a; }
```

```
a = a << 1;
```

```
b = b >> 1;
```

```
n = n - 1;
```


```
if (n != 0) then
```

```
    { goto op; }
```

```
return(p);
```

Sequential Add-and-Shift Multiplier

The ASMD chart

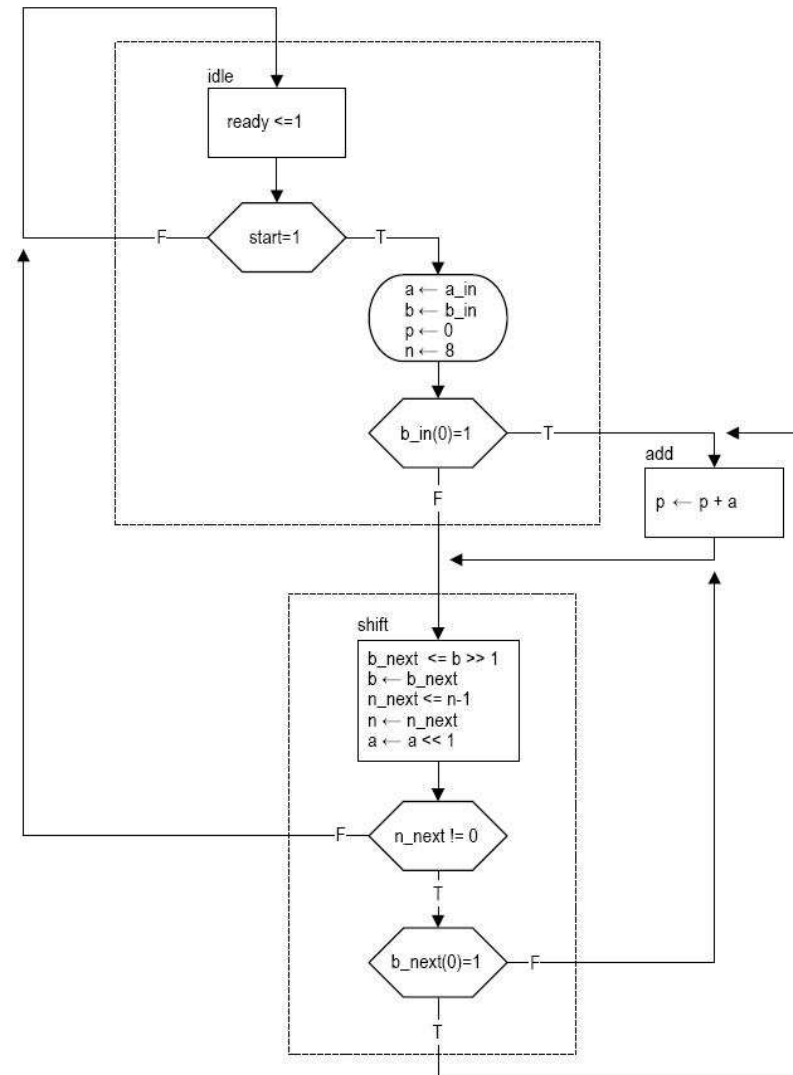

Sequential Add-and-Shift Multiplier

Since the two shift operations and the counter decrementing operation are independent, they are scheduled in the same state (performed in parallel)

Also, due to the **delayed store** of the RT operations, we use the *next* values, i.e., $b_next(0)$ and n_next , of the registers in the decision boxes

Last, the two shift operations, $a \ll 1$ and $b \gg 1$, can use the *concatenation* operation and require no logic

```
architecture shift_add_raw_arch of seq_mult is
  constant WIDTH: integer := 8;

  -- width of the counter
  constant C_WIDTH: integer := 4;
  constant C_INIT:
    unsigned(C_WIDTH-1 downto 0) := "1000";
  type state_type is (idle, add, shift);
  signal state_reg, state_next: state_type;
  signal b_reg, b_next: unsigned(WIDTH-1 downto 0);
```

Sequential Add-and-Shift Multiplier

```
signal a_reg, a_next: unsigned(2*WIDTH-1 downto 0);
signal n_reg, n_next: unsigned(C_WIDTH-1 downto 0);
signal p_reg, p_next: unsigned(2*WIDTH-1 downto 0);
begin

-- state and data registers
process(clk, reset)
  begin
    if (reset = '1') then
      state_reg <= idle;
      b_reg <= (others => '0');
      a_reg <= (others => '0');
      n_reg <= (others => '0');
      p_reg <= (others => '0');
    elsif (clk'event and clk = '1') then
      state_reg <= state_next;
      b_reg <= b_next;
      a_reg <= a_next;
```


Sequential Add-and-Shift Multiplier

```
        n_reg <= n_next;
        p_reg <= p_next;
    end if;
end process;

-- combinational circuit
process(start, state_reg, b_reg, a_reg, n_reg,
        p_reg, b_in, a_in, n_next, a_next)
begin
    b_next <= b_reg;
    a_next <= a_reg;
    n_next <= n_reg;
    p_next <= p_reg;
    ready <= '0';
    case state_reg is
        when idle =>
            if (start = '1') then
                b_next <= unsigned(b_in);
```

Sequential Add-and-Shift Multiplier

```
a_next <= "00000000" & unsigned(a_in);
n_next <= C_INIT;
p_next <= (others => '0');
if (b_in(0) = '1') then
    state_next <= add;
else
    state_next <= shift;
end if;
else
    state_next <= idle;
end if;
ready <= '1';
when add =>
    p_next <= p_reg + a_reg;
    state_next <= shift;
when shift =>
    n_next <= n_reg - 1;
    b_next <= '0' & b_reg (WIDTH-1 downto 1);
```

Sequential Add-and-Shift Multiplier

```
        a_next <= a_reg(2*WIDTH-2 downto 0) & '0';
        if (n_next /= "0000") then
            if (a_next(0) = '1') then
                state_next <= add;
            else
                state_next <= shift;
            end if;
        else
            state_next <= idle;
        end if;
    end case;
end process;

r <= std_logic_vector(p_reg);
end shift_add_raw_arch;
```

Sequential Add-and-Shift Multiplier

For an 8-bit input

Best case: $b = 0 \Rightarrow K = 1 + 8$ (shift only)

Worst case: $b = 255 \Rightarrow K = 1 + 8*2$ (add and shift)

For an n -bit input:

Worst case: $K = 2*n + 1$

There are several opportunities for improvement

- The operations in the *add* and *shift* states are independent and therefore, these two states can be merged

A *conditional output* box is used to implement the $p \leftarrow p + a$ operation


- In the data path, when a is added to the partial products, only the eight leftmost bits are involved and the remaining (trailing) bits are kept unchanged

We can reduce the 16-bit adder to a 9-bit adder (8-bit operand and 1-bit carry) by shifting the partial product to the right one position in each iteration


This also eliminates the need to shift multiplier A and reduces the width of the a register by half

Sequential Add-and-Shift Multiplier

Part (b) shows the improvements

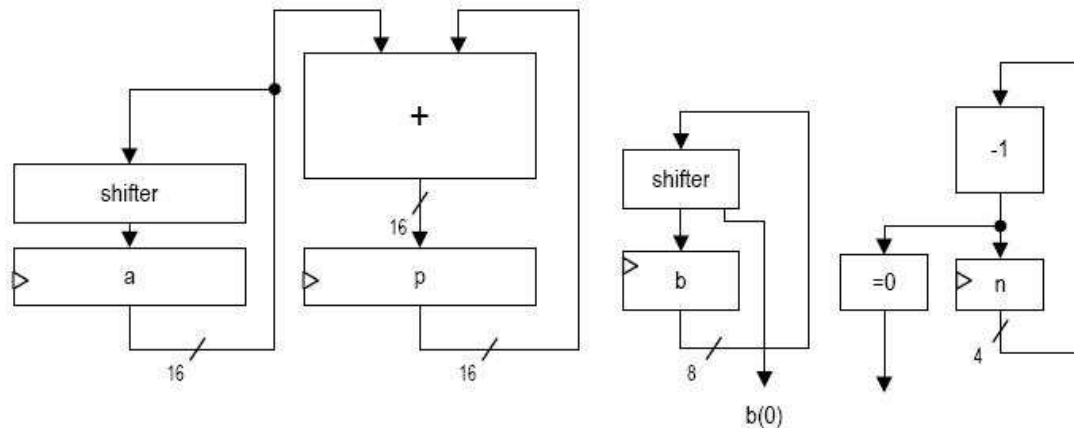

(a) Initial design

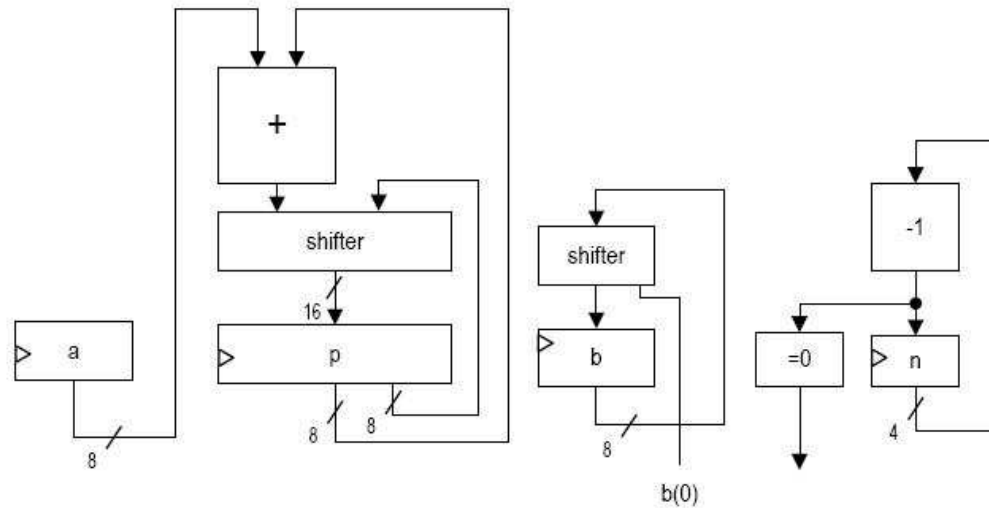

(b) "Shifting p register" design


Sequential Add-and-Shift Multiplier

The last improvement involves using the unused portion of the p register for operand b

Only the left portion of the p register contains valid data initially

The valid portion **expands** to the right one position in each iteration when the *shift-right* operation is performed

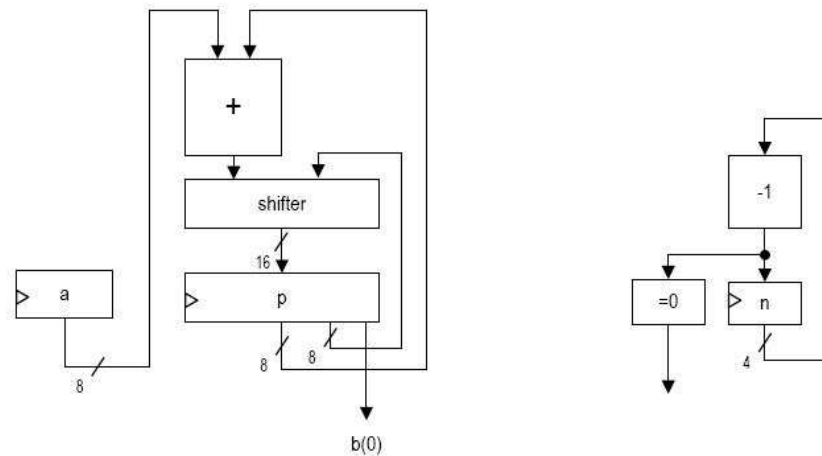
On the other hand, the b register has 8 valid bits initially and **shrinks** when the shift operation removes the LSB on each iteration



(c) Final design

Sequential Add-and-Shift Multiplier

Final ASMD

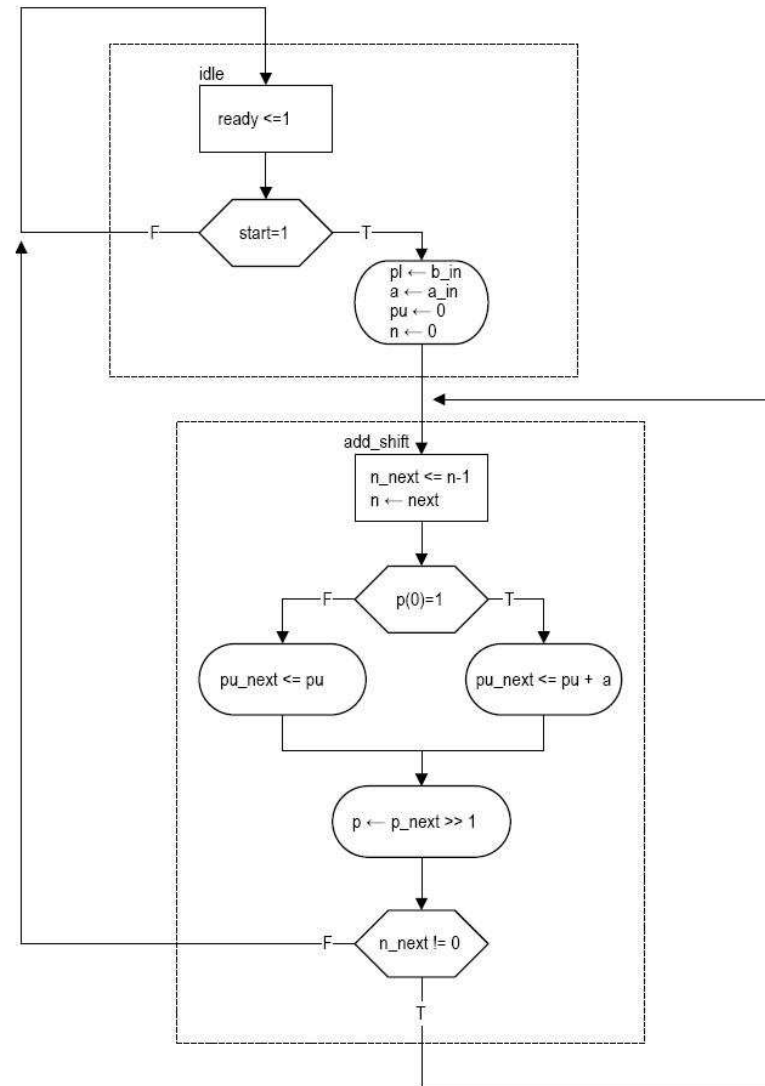

Sequential Add-and-Shift Multiplier

```
architecture shift_add_better_arch of seq_mult is
  constant WIDTH: integer := 8;
  -- width of the counter
  constant C_WIDTH: integer := 4;
  constant C_INIT:
    unsigned(C_WIDTH-1 downto 0) := "1000";
  type state_type is (idle, add_shft);
  signal state_reg, state_next: state_type;
  signal a_reg, a_next: unsigned(WIDTH-1 downto 0);
  signal n_reg, n_next: unsigned(C_WIDTH-1 downto 0);
  signal p_reg, p_next: unsigned(2*WIDTH downto 0);

  -- alias for the upper part and lower parts of p_reg
  alias pu_next: unsigned(WIDTH downto 0) is
    p_next(2*WIDTH downto WIDTH);
  alias pu_reg: unsigned(WIDTH downto 0) is
    p_reg(2*WIDTH downto WIDTH);
```


Sequential Add-and-Shift Multiplier

```
alias pl_reg: unsigned(WIDTH-1 downto 0) is
    p_reg(WIDTH-1 downto 0);

begin
-- state and data registers
process(clk, reset)
    begin
    if (reset = '1') then
        state_reg <= idle;
        a_reg <= (others => '0');
        n_reg <= (others => '0');
        p_reg <= (others => '0');
    elsif (clk'event and clk = '1') then
        state_reg <= state_next;
        a_reg <= a_next;
        n_reg <= n_next;
        p_reg <= p_next;
    end if;
end process;
```

Sequential Add-and-Shift Multiplier

```
-- combinational circuit
process(start, state_reg, a_reg, n_reg, p_reg,
        a_in, b_in, n_next, p_next)
begin
  a_next <= a_reg;
  n_next <= n_reg;
  p_next <= p_reg;
  ready <= '0';
  case state_reg is
    when idle =>
      if (start = '1') then
        p_next <= "000000000" & unsigned(b_in);
        a_next <= unsigned(a_in);
        n_next <= C_INIT;
        state_next <= add_shft;
      else
        state_next <= idle;
      end if;
```

Sequential Add-and-Shift Multiplier

```
        ready <= '1';
    when add_shft =>
        n_next <= n_reg - 1;

-- add if multiplier bit is '1'
        if (p_reg(0) = '1') then
            pu_next <= pu_reg + ('0' & a_reg);
        else
            pu_next <= pu_reg;
        end if;

-- shift
        p_next <= '0' & pu_next &
                pl_reg(WIDTH-1 downto 1);
        if (n_next /= "0000") then
            state_next <= add_shft;
```

Sequential Add-and-Shift Multiplier

```

        else
            state_next <= idle;
        end if;
    end case;
end process;

r <= std_logic_vector(p_reg(2*WIDTH-1 downto 0));
end shift_add_better_arch;

```

Comparison of three designs

Design method	# Clock cycles	Size of functional units	# Register bits
Repetitive-addition	2 to $2^n + 1$	$2n$ -bit adder, n -bit decrementor	$4n$
Add-and-shift (original)	$n + 1$ to $2n + 1$	$2n$ -bit adder, $\lceil \log_2(n + 1) \rceil$ -bit dec	$5n + \lceil \log_2(n + 1) \rceil$
Add-and-shift (refined)	$n + 1$	n -bit adder, $\lceil \log_2(n + 1) \rceil$ -bit dec	$3n + \lceil \log_2(n + 1) \rceil + 1$