

Combinational Circuit Design

This slide set covers

- Derivation of efficient HDL description
- Operator sharing
- Functionality sharing
- Layout-related circuits
- General circuits

Operator Sharing

Sharing of resources often results in a performance penalty at the benefit of area savings

| width | VHDL operator | | | | | | | | | |
|-------------------|---------------|-----|----------------|----------------|-----|-----------------|-----------------|----------------|----------------|-----|
| | nand | xor | > _a | > _d | = | +1 _a | +1 _d | + _a | + _d | mux |
| area (gate count) | | | | | | | | | | |
| 8 | 8 | 22 | 25 | 68 | 26 | 27 | 33 | 51 | 118 | 21 |
| 16 | 16 | 44 | 52 | 102 | 51 | 55 | 73 | 101 | 265 | 42 |
| 32 | 32 | 85 | 105 | 211 | 102 | 113 | 153 | 203 | 437 | 85 |
| 64 | 64 | 171 | 212 | 398 | 204 | 227 | 313 | 405 | 755 | 171 |
| delay (ns) | | | | | | | | | | |
| 8 | 0.1 | 0.4 | 4.0 | 1.9 | 1.0 | 2.4 | 1.5 | 4.2 | 3.2 | 0.3 |
| 16 | 0.1 | 0.4 | 8.6 | 3.7 | 1.7 | 5.5 | 3.3 | 8.2 | 5.5 | 0.3 |
| 32 | 0.1 | 0.4 | 17.6 | 6.7 | 1.8 | 11.6 | 7.5 | 16.2 | 11.1 | 0.3 |
| 64 | 0.1 | 0.4 | 35.7 | 14.3 | 2.2 | 24.0 | 15.7 | 32.2 | 22.9 | 0.3 |

Operator Sharing

Ideally, synthesis software can identify these opportunities automatically, but in practice, this is rarely the case.

There are usually lots of opportunities to share resources using the basic VHDL constructs b/c in many cases, operations are *mutually exclusive*

The *value expressions* in priority network and multiplexing network are mutually exclusive in the sense that only one result is routed to the output

Conditional signal assignment (same for *if stmt*)

```
sig_name <= value_expr_1 when boolean_expr_1 else  
           value_expr_2 when boolean_expr_2 else  
           value_expr_3 when boolean_expr_3 else  
           ...
```

Selected signal assignment (same for *case stmt*)

```
with select_expression select  
sig_name <= value_expr_1 when choice_1,  
           value_expr_2 when choice_2, ...  
           value_expr_n when choice_n;
```

Operator Sharing


If same operator is used in different expressions, it can be shared

Example 1: Original code:


```
r <= a+b when boolean_exp else
    a+c;
```

Revised code: here the **operands** are routed, not the output of the adder
 
```
src0 <= b when boolean_exp else
    c;
r <= a + src0;
```



(a) Original diagram

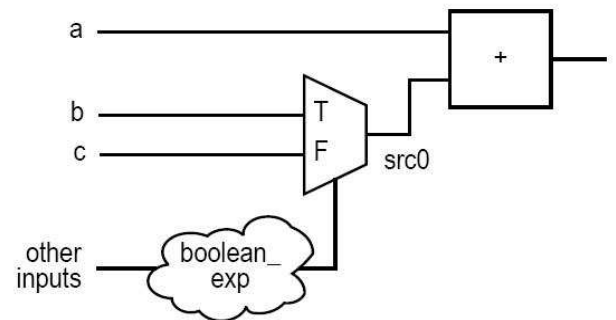

(b) Diagram with sharing

Original: **Area:** 2 adders, 1 MUX, **Delay:** $\max(T_{\text{adder}}, T_{\text{boolean}}) + T_{\text{MUX}}$

With Sharing: **Area:** 1 adders, 1 MUX, **Delay:** $T_{\text{boolean}} + T_{\text{MUX}} + T_{\text{adder}}$

Operator Sharing

Example 2: Original code:

```
process (a, b, c, d, ...)
  begin
    if boolean_exp_1 then
      r <= a+b;
    elsif boolean_exp_2 then
      r <= a+c;
    else
      r <= d+1;
    end if
  end process;
```



Revised code:

```
process (a, b, c, d, ...)
  begin
    if boolean_exp_1 then
      src0 <= a;
      src1 <= b;
```

Operator Sharing

```

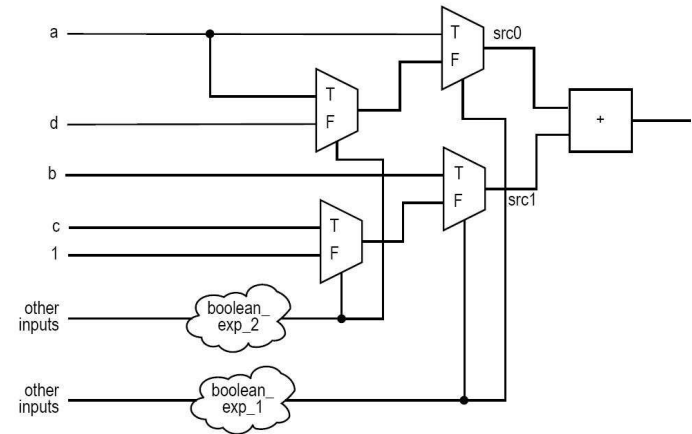 elsif boolean_exp_2 then
    src0 <= a;
    src1 <= c;
else
    src0 <= d;
    src1 <= "00000001"; -- MUX with constants can be
                        -- optimized by synthesis,
                        -- yielding more area savings
end if;
end process;
r <= src0 + src1;
    
```



Original: **Area:** 2 adders, 1 inc, 2 MUX

With Sharing: **Area:** 1 adder, 4 MUX

Operator Sharing

Example 3: Original code:

```
with sel select  
    r <= a+b when "00",  
        a+c when "01",  
        d+1 when others;
```


Revised code:

```
with sel_exp select  
    src0 <= a when "00" | "01",  
        d when others;  
with sel_exp select  
    src1 <= b when "00",  
        c when "01",  
        "00000001" when others;  
r <= src0 + src1;
```

Operator Sharing

Note that the revised implementation has longer delay because of:

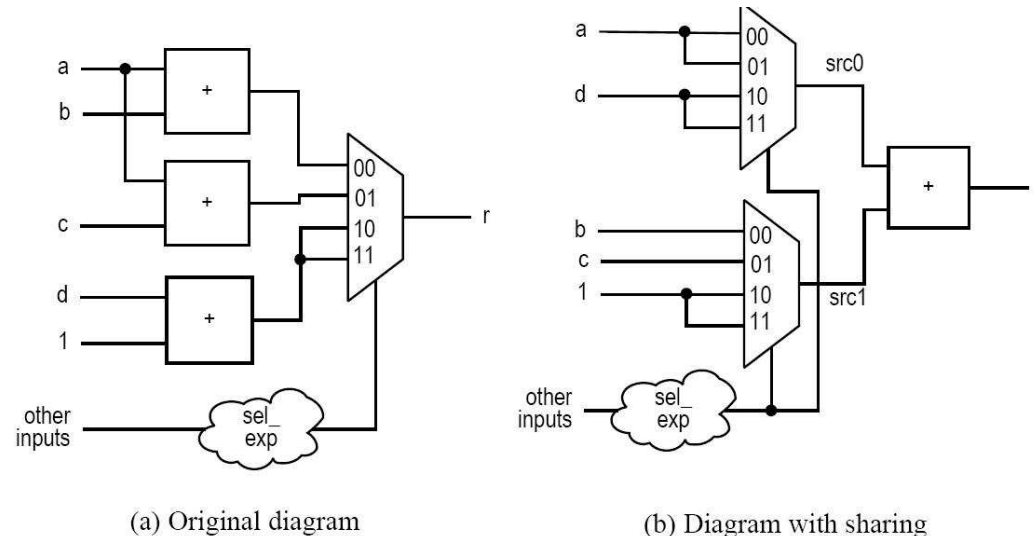- The increased number of cascaded components in some cases
- The restriction on the available parallelism in other cases



Original: **Area:** 2 adders, 1 inc, 1 MUX

With Sharing: **Area:** 1 adder, 2 MUX

Note that in the revised scheme, the *sel_exp* Boolean logic **MUST** be evaluated first before the addition takes place -- this is not the case in the original version


Operator Sharing

Example 4: Original code:

```

process (a, b, c, d, ...)
  begin
    if boolean_exp then
      x <= a + b;
      y <= (others=>'0');
    else
      x <= (others=>'1');
      y <= c + d;
    end if;
  end process;

```

 

(a) Original diagram

Original: **Area:** 2 adders, 2 MUX


Operator Sharing

Revised code:

```
process (a, b, c, d, ...)
  begin
    if boolean_exp then
      src0 <= a;
      src1 <= b;
      x <= sum;
      y <= (others=>'0');
    else
      src0 <= c;
      src1 <= d;
      x <= (others=>'1');
      y <= sum;
    end if;
  end process;
  sum <= src0 + src1;
```

Operator Sharing

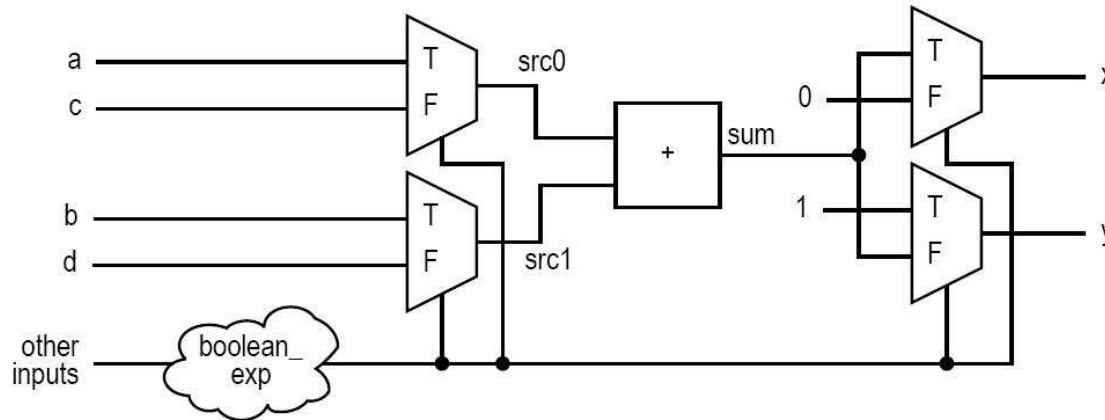Worst case situation in which operator has **no** common sources or destinations



With Sharing: **Area:**
1 adders, 4 MUX

Is the sharing worthwhile in this case?

1 adder saved in original version but 2 MUX added in revised scheme

It depends on the size of the adder -- if optimized for speed, then it can be significantly larger than 2 MUX

Summary

- Merit of sharing depends on the complexity of the operator and the routing circuit
- Complex operators provide a lot of area savings
- Cost is increased propagation delay because of serial operation

Functionality Sharing

A large circuit such as a microcontroller includes a lot of functions

Several functions may be related and can share a common circuit

Identifying these opportunities is more difficult and is something synthesis software can NOT do

Done in an *ad hoc* manner by designer and is based on his/her expertise

Consider *add-sub* circuit

| ctrl | operation |
|------|-----------|
| 0 | a + b |
| 1 | a - b |

Straightforward translation into VHDL:


```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity addsub is
```

Functionality Sharing

```
    port (  
        a,b: in std_logic_vector(7 downto 0);  
        ctrl: in std_logic;  
        r: out std_logic_vector(7 downto 0)  
    );  
end addsub;  
  
architecture direct_arch of addsub is  
    signal src0, src1, sum: signed(7 downto 0);  
begin  
    src0 <= signed(a);  
    src1 <= signed(b);  
    sum <= src0 + src1 when ctrl='0' else  
           src0 - src1;  
    r <= std_logic_vector(sum);  
end direct_arch;
```

Functionality Sharing

 This version is translated such that it includes an adder, subtractor and MUX



As we know, in 2's compliment, subtraction is implemented as $a + \bar{b} + 1$

architecture shared_arch **of** addsub **is**

```
signal src0, src1, sum: signed(7 downto 0);
```

```
signal cin: signed(0 downto 0); -- carry-in bit
```

```
begin
```

```
src0 <= signed(a);
```

```
src1 <= signed(b) when ctrl='0' else signed(not b);
```

```
cin <= "0" when ctrl='0' else "1";
```

```
sum <= src0 + src1 + cin;
```


```
r <= std_logic_vector(sum);
```

```
end shared_arch;
```

Functionality Sharing

The '+ 1' is implemented by setting the carry-in bit to '1' of the adder

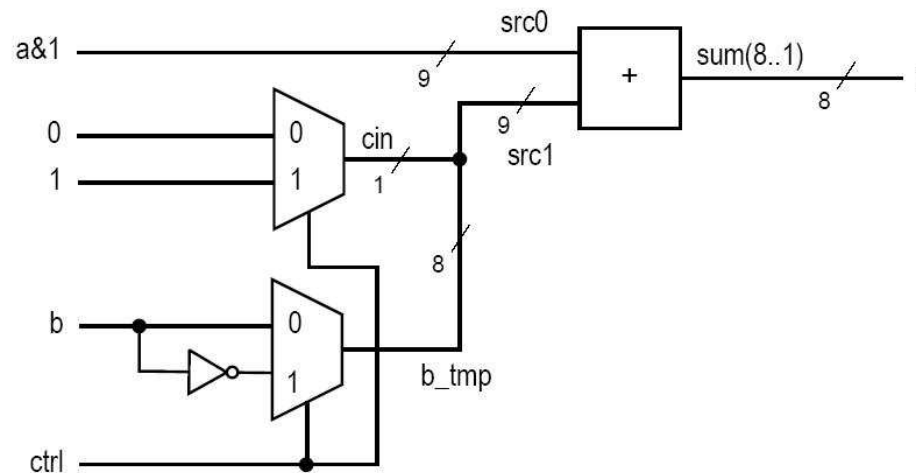Most synthesis software should deduce that the '+ cin' is one bit and can be implemented in this fashion



Alternatively, you can manually describe the carry-in in the adder by adding an extra bit to the adder and operands

Original operands $a_7a_6a_5a_4a_3a_2a_1a_0$ and $b_7b_6b_5b_4b_3b_2b_1b_0$

New operands $a_7a_6a_5a_4a_3a_2a_1a_01$ and $b_7b_6b_5b_4b_3b_2b_1b_0c_{in}$


Functionality Sharing

After the addition, discard the low order bit

```
architecture manual_carry_arch of addsub is
    signal src0, src1, sum: signed(8 downto 0);
    signal b_tmp: std_logic_vector(7 downto 0);
    signal cin: std_logic; -- carry-in bit
begin
    src0 <= signed(a & '1');
    b_tmp <= b when ctrl='0' else
        not b;
    cin <= '0' when ctrl='0' else
        '1';
    src1 <= signed(b_tmp & cin);
    sum <= src0 + src1;
    r <= std_logic_vector(sum(8 downto 1));
end manual_carry_arch;
```

Functionality Sharing

 As we know, *ieee.numeric_std* provides signed and unsigned, with signed in 2's complement format



Here, addition and subtraction operations are identical and therefore, the same hardware can be used for either data type

Functionality Sharing

Unfortunately, this is **not** true for the relational operators, and therefore we need to craft a control signal into the VHDL code

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity comp2mode is  
    port (  
        a,b: in std_logic_vector(7 downto 0);  
        mode: in std_logic;  
        agtb: out std_logic  
    );  
end comp2mode;  
  
architecture direct_arch of comp2mode is  
    signal agtb_signed, agtb_unsigned: std_logic;  
begin
```

Functionality Sharing

```
    agtb_signed <= '1' when signed(a) > signed(b) else
                    '0';
    agtb_unsigned <= '1' when unsigned(a) > unsigned(b)
                    else '0';
    agtb <= agtb_unsigned when (mode='0') else
            agtb_signed;
end direct_arch;
```

To create an opportunity for sharing, we need to handle the sign bit separately for signed operands

If the sign bits are **different**, then the positive number is larger for signed

If they are the **same**, compare the n-1 bits (without MSB) using normal comparison

Consider 1111 (-1), 1100 (-4), 1001(-7) -- after removing the MSB (sign bit)

111 > 100 > 001

Which is consistent with $-1 > -4 > -7$, so we can share the LSB compare logic

Functionality Sharing

```
architecture shared_arch of comp2mode is
  signal a1_b0, agtb_mag: std_logic;
begin
  a1_b0 <= '1' when a(7)='1' and b(7)='0' else
    '0';
  agtb_mag <= '1' when a(6 downto 0) > b(6 downto 0)
    else '0';
  agtb <= agtb_mag when (a(7)=b(7)) else
    a1_b0 when mode='0' else -- unsigned mode
    not a1_b0; -- signed mode
end shared_arch;
```

Rules are

- If a and b have same sign bit, compare in regular fashion
- If a 's sign bit is '1' and b 's sign bit is '0', a is greater than b when in **unsigned** mode and b is greater than a in signed mode
- If a 's sign bit is '0' and b 's sign bit is '1', reverse the previous result

New version is about 1/2 size of dual mode version

Functionality Sharing

Assume we need a *full comparator*, i.e., one that provides *greater-than*, *equal-to* and *less-than* -- straightforward approach

```
library ieee;  
use ieee.std_logic_1164.all;  
entity comp3 is  
    port (  
        a,b: in std_logic_vector(15 downto 0);  
        agtb, altb, aeqb: out std_logic  
    );  
end comp3 ;  
  
architecture direct_arch of comp3 is  
    begin  
        agtb <= '1' when a > b else '0';  
        altb <= '1' when a < b else '0';  
        aeqb <= '1' when a = b else '0';  
end direct_arch;
```

Functionality Sharing

An obvious change is to share the resources of two of the comparators to derive the third

Another optimization is to recognize that the *equal-to* comparator is faster and smaller than the other two

```
architecture share2_arch of comp3 is
  signal eq, lt: std_logic;
begin
  eq <= '1' when a = b else '0';
  lt <= '1' when a < b else '0';
  aeqb <= eq;
  altb <= lt;
  agtb <= not (eq or lt);
end share2_arch;
```

Text covers a

- **absolute difference** circuit
- **three function barrel shifter** circuit


Layout-Related Circuits

After synthesis, placement and routing will derive the actual physical layout of a digital circuit on a silicon chip

VHDL cannot specify the exact layout, but it can control the general "shape"


In general, "square" or 2-D circuits are better than a 1-D cascading-chain

 - Conditional signal assignment/if statement form a single "horizontal" cascading chain
- Selected signal assignment/case statement form a large "vertical" mux
- Neither is ideal



(a) Cascading-chain structure

1-D has long delay

 

Better, 2-D has shorter delay

Layout-Related Circuits

Consider the *reduced-xor* circuit (covered before), in which all input bits of the operand are XOR'ed to produce the output

The previous 1-D schematic is described as follows

```
library ieee;
use ieee.std_logic_1164.all;
entity reduced_xor is
    port (
        a: in std_logic_vector(7 downto 0);
        y: out std_logic
    );
end reduced_xor;

architecture cascade1_arch of reduced_xor is
begin
    y <= a(0) xor a(1) xor a(2) xor a(3) xor
        a(4) xor a(5) xor a(6) xor a(7);
end cascade1_arch;
```

Layout-Related Circuits

We can also use an 8-bit internal signal p to represent intermediate results

```
architecture cascade2_arch of reduced_xor is  
    signal p: std_logic_vector(7 downto 0);  
    begin  
        p(0) <= '0' xor a(0);  
        p(1) <= p(0) xor a(1);  
        p(2) <= p(1) xor a(2);  
        p(3) <= p(2) xor a(3);  
        p(4) <= p(3) xor a(4);  
        p(5) <= p(4) xor a(5);  
        p(6) <= p(5) xor a(6);  
        p(7) <= p(6) xor a(7);  
        y <= p(7);  
    end cascade2_arch;
```

The repetitive nature allows for a more compact **vector** form as shown below

Layout-Related Circuits

```
architecture cascade_compact_arch of reduced_xor is
  constant WIDTH: integer := 8;
  signal p: std_logic_vector(WIDTH-1 downto 0);
  begin
    p <= (p(WIDTH-2 downto 0) & '0') xor a;
    y <= p(WIDTH-1);
  end cascade_compact_arch;
```

Although this design uses the minimal number of *XOR* gates, it suffers from long propagation delay

Although the synthesis tool is likely to produce a 2-D structure given the simplicity of this circuit, the following is one way to guarantee it

```
architecture tree_arch of reduced_xor is
  begin
    y <= ((a(7) xor a(6)) xor (a(5) xor a(4))) xor
          ((a(3) xor a(2)) xor (a(1) xor a(0)));
  end tree_arch;
```

Layout-Related Circuits

Comparison of n-input reduced xor

- Cascading chain :

Area: (n-1) xor gates, **Delay:** (n-1), **Coding:** easy to modify (scale)

- Tree:

Area: (n-1) xor gates, **Delay:** $\log_2 n$, **Coding:** not so easy to modify

Consider a **reduced-xor-vector** circuit

$$y_0 = a_0$$

$$y_1 = a_1 \oplus a_0$$

$$y_2 = a_2 \oplus a_1 \oplus a_0$$

$$y_3 = a_3 \oplus a_2 \oplus a_1 \oplus a_0$$

$$y_4 = a_4 \oplus a_3 \oplus a_2 \oplus a_1 \oplus a_0$$

$$y_5 = a_5 \oplus a_4 \oplus a_3 \oplus a_2 \oplus a_1 \oplus a_0$$

$$y_6 = a_6 \oplus a_5 \oplus a_4 \oplus a_3 \oplus a_2 \oplus a_1 \oplus a_0$$

$$y_7 = a_7 \oplus a_6 \oplus a_5 \oplus a_4 \oplus a_3 \oplus a_2 \oplus a_1 \oplus a_0$$

Here, all combinations of the lower bits of the input signal are **xor**'ed to produce 8 outputs, y_i

The straightforward (no sharing) implementation is given below

Layout-Related Circuits

```
library ieee;
use ieee.std_logic_1164.all;
entity reduced_xor_vector is
  port (
    a: in std_logic_vector(7 downto 0);
    y: out std_logic_vector(7 downto 0)
  );
end reduced_xor_vector;

architecture direct_arch of reduced_xor_vector is
  begin
    y(0) <= a(0);
    y(1) <= a(1) xor a(0);
    y(2) <= a(2) xor a(1) xor a(0);
    y(3) <= a(3) xor a(2) xor a(1) xor a(0);
    y(4) <= a(4) xor a(3) xor a(2) xor a(1) xor a(0);
    y(5) <= a(5) xor a(4) xor a(3) xor a(2) xor a(1)
      xor a(0);
```

Layout-Related Circuits

```
y(6) <= a(6) xor a(5) xor a(4) xor a(3) xor a(2)
      xor a(1) xor a(0);
y(7) <= a(7) xor a(6) xor a(5) xor a(4) xor a(3)
      xor a(2) xor a(1) xor a(0);
end direct_arch;
```

This requires 28 **xor** gates if implemented un-optimized -- there are lots of *common sub-expressions* that can be shared

Code that shares is very similar to the *reduced-xor* code given earlier except all intermediate results are used as outputs

```
architecture shared1_arch of reduced_xor_vector is
  signal p: std_logic_vector(7 downto 0);
begin
  p(0) <= a(0);
  p(1) <= p(0) xor a(1);
  p(2) <= p(1) xor a(2);
  p(3) <= p(2) xor a(3);
```

Layout-Related Circuits

```

    p(4) <= p(3) xor a(4);
    p(5) <= p(4) xor a(5);
    p(6) <= p(5) xor a(6);
    p(7) <= p(6) xor a(7);
    y <= p;
end shared1_arch;

```

As before, the pattern of assignments can be coded more efficiently

```

architecture shared_compact_ar of reduced_xor_vector is
    constant WIDTH: integer := 8;
    signal p: std_logic_vector(WIDTH-1 downto 0);
    begin
    p <= (p(WIDTH-2 downto 0) & '0') xor a;
    y <= p;
end shared_compact_ar;

```

All of these designs specify a 1-D structure, with the critical path to $y(7)$

Text gives version with parenthesis to force 2-D tree-type design

Layout-Related Circuits


An *ad hoc* version that reduces both propagation delay to 3 gates AND uses only 12 **xor** gates

```
architecture optimal_tree_arch of reduced_xor_vector is
    signal p01, p23, p45, p67, p012,
           p0123, p456, p4567: std_logic;

begin
    p01 <= a(0) xor a(1);
    p23 <= a(2) xor a(3);
    p45 <= a(4) xor a(5);
    p67 <= a(6) xor a(7);
    p012 <= p01 xor a(2);
    p0123 <= p01 xor p23;
    p456 <= p45 xor a(6);
    p4567 <= p45 xor p67;
    y(0) <= a(0);
    y(1) <= p01;
    y(2) <= p012;
    y(3) <= p0123;
```

Layout-Related Circuits
 
```
y(4) <= p0123 xor a(4);  
y(5) <= p0123 xor p45;  
y(6) <= p0123 xor p456;  
y(7) <= p0123 xor p4567;  
end optimal_tree_arch;
```



Layout-Related Circuits

Comparison of n -input reduced-xor-vector

- Cascading chain

Area: $(n-1)$ xor gates, **Delay:** $(n-1)$, **Coding:** easy to modify (scale)

- Multiple trees

Area: $O(n^2)$ xor gates, **Delay:** $\log_2 n$, **Coding:** not so easy to modify

- Optimal tree

Area: $O(n \log_2 n)$ xor gates, **Delay:** $\log_2 n$, **Coding:** difficult to modify

Unlike the previous example, synthesis is not able to convert cascading chain to the optimal tree (parallel-prefix)

Next consider a **barrel shifter** -- direct implementation

```
library ieee;  
use ieee.std_logic_1164.all;  
entity rotate_right is  
    port (  
        a: in std_logic_vector(7 downto 0);
```


Layout-Related Circuits


(Barrel shifter)

```
        amt: in std_logic_vector(2 downto 0);
        y: out std_logic_vector(7 downto 0)
    );
end rotate_right;

architecture direct_arch of rotate_right is
    begin
        with amt select
            y<= a                                when "000",
            a(0) & a(7 downto 1)                when "001",
            a(1 downto 0) & a(7 downto 2) when "010",
            a(2 downto 0) & a(7 downto 3) when "011",
            a(3 downto 0) & a(7 downto 4) when "100",
            a(4 downto 0) & a(7 downto 5) when "101",
            a(5 downto 0) & a(7 downto 6) when "110",
            a(6 downto 0) & a(7) when others; -- 111
    end direct_arch;
```

Layout-Related Circuits

 The barrel shifter rotates the input a by the amount specified, from 0 to 7 rotates




The code is realized using eight 1-bit 8-to-1 MUXs

Layout-Related Circuits

Problems with this include

- Wide MUXs cannot be effectively mapped to certain device technologies
- Input wires, a , route to all MUXs, so loading and congestion grows as $O(n^2)$
- The 'single narrow strip' shape makes place and route difficult

Better to do the wiring in levels

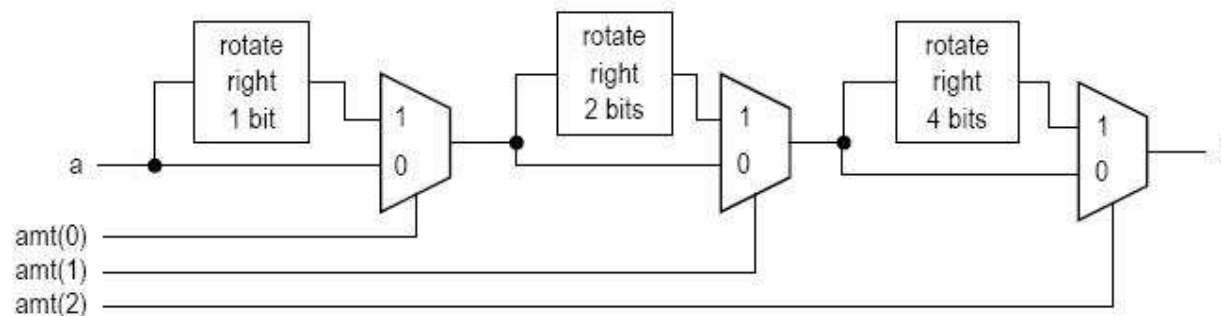

In each level, each bit of the amt signal determines if we rotate or pass through

Note that the rotate amounts are different depending on the bit's position

After passing through all three levels, the number of rotations performed is equal to the sum of those performed at each level

$$amt(2)*2^2 + amt(1)*2^1 + amt(0)*2^0$$

Layout-Related Circuits

```
architecture multi_level_arch of rotate_right is
  signal le0_out, le1_out, le2_out:
    std_logic_vector(7 downto 0);
begin
  -- level 0, shift 0 or 1 bit
  le0_out <= a(0) & a(7 downto 1) when amt(0)='1' else
    a;

  -- level 1, shift 0 or 2 bits
  le1_out <= le0_out(1 downto 0) & le0_out(7 downto 2)
    when amt(1)='1' else le0_out;

  -- level 2, shift 0 or 4 bits
  le2_out <= le1_out(3 downto 0) & le1_out(7 downto 4)
    when amt(2)='1' else le1_out;

  y <= le2_out;
end multi_level_arch;
```

Layout-Related Circuits

Comparison for n-bit shifter

- Direct implementation

n n-to-1 MUX

Vertical strip with $O(n^2)$ input wiring

Code not so easy to modify

- Staged implementation

$n \cdot \log_2 n$ 2-to-1 MUX (8 2-to-1 MUXs at each level for a total of 24)

Rectangular shaped

Code easier to modify

General Examples

- Gray code counter
- Signed addition with status
- Simple combinational multiplier

Gray code is a special sequence of values where only one bit changes in any two successive code.

Gray Code

Thus it minimizes the *number of transitions* that a signal switches between successive words

| binary code $b_3b_2b_1b_0$ | gray code $g_3g_2g_1g_0$ | gray code | incremented gray code |
|-------------------------------|-----------------------------|-----------|-----------------------|
| 0000 | 0000 | 0000 | 0001 |
| 0001 | 0001 | 0001 | 0011 |
| 0010 | 0011 | 0011 | 0010 |
| 0011 | 0010 | 0010 | 0110 |
| 0100 | 0110 | 0110 | 0111 |
| 0101 | 0111 | 0111 | 0101 |
| 0110 | 0101 | 0101 | 0100 |
| 0111 | 0100 | 0100 | 1100 |
| 1000 | 1100 | 1100 | 1101 |
| 1001 | 1101 | 1101 | 1111 |
| 1010 | 1111 | 1111 | 1110 |
| 1011 | 1110 | 1110 | 1010 |
| 1100 | 1010 | 1010 | 1011 |
| 1101 | 1011 | 1011 | 1001 |
| 1110 | 1001 | 1001 | 1000 |
| 1111 | 1000 | 1000 | 0000 |

Need to implement the gray code incremter on the right

Straightforward way is to translate the table into a *selected signal assignment* stmt

Gray Code

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity g_inc is  
    port (  
        g: in std_logic_vector(3 downto 0);  
        g1: out std_logic_vector(3 downto 0)  
    );  
end g_inc ;  
  
architecture table_arch of g_inc is  
    begin  
    with g select  
        g1 <= "0001" when "0000",  
            "0011" when "0001",  
            "0010" when "0011",  
            "0110" when "0010",  
            "0111" when "0110",
```

Gray Code

```
"0101" when "0111",  
"0100" when "0101",  
"1100" when "0100",  
"1101" when "1100",  
"1111" when "1101",  
"1110" when "1111",  
"1010" when "1110",  
"1011" when "1010",  
"1001" when "1011",  
"1000" when "1001",  
"0000" when others; -- "1000"  
  
end table_arch;
```

Although this VHDL code is simple, it is **not** scalable b/c revisions take on order $O(n^2)$

Unfortunately, there is no easy algorithm to derive the next Gray code directly

However, an algorithm **does exist** to *convert* between binary and Gray code, and therefore one implementation is to use a binary incrementer

Gray Code

So the algorithm is to 1) convert a Gray code to binary, 2) increment binary and 3) convert back

The conversion is based on the following

The i th bit (g_i) of the Gray code word is '1' if the i th bit and $(i + 1)$ th bit, i.e., b_i and b_{i+1} of the corresponding binary word are different

| binary code $b_3b_2b_1b_0$ | gray code $g_3g_2g_1g_0$ |
|-------------------------------|-----------------------------|
| 0000 | 0000 |
| 0001 | 0001 |
| 0010 | 0011 |
| 0011 | 0010 |
| 0100 | 0110 |
| 0101 | 0111 |
| 0110 | 0101 |
| 0111 | 0100 |
| 1000 | 1100 |
| 1001 | 1101 |
| 1010 | 1111 |
| 1011 | 1110 |
| 1100 | 1010 |
| 1101 | 1011 |
| 1110 | 1001 |
| 1111 | 1000 |

Binary to Gray

$$g_i = b_i \oplus b_{i+1} \longrightarrow$$

$$\begin{aligned} g_3 &= b_3 \oplus 0 = b_3 \\ g_2 &= b_2 \oplus b_3 \\ g_1 &= b_1 \oplus b_2 \\ g_0 &= b_0 \oplus b_1 \end{aligned}$$

Gray to Binary

$$b_i = g_i \oplus b_{i+1} \longrightarrow$$

$$\begin{aligned} b_3 &= g_3 \oplus 0 = g_3 \\ b_2 &= g_2 \oplus b_3 = g_2 \oplus g_3 \\ b_1 &= g_1 \oplus b_2 = g_1 \oplus g_2 \oplus g_3 \\ b_0 &= g_0 \oplus b_1 = g_0 \oplus g_1 \oplus g_2 \oplus g_3 \end{aligned}$$

Note recursive expansion is possible

Very similar to *reduced-xor-vector*

Gray Code

```
architecture compact_arch of g_inc is
  constant WIDTH: integer := 4;
  signal b, b1: std_logic_vector(WIDTH-1 downto 0);
  begin

  -- Gray to binary
  b <= g xor ('0' & b(WIDTH-1 downto 1));

  -- binary increment
  b1 <= std_logic_vector((unsigned(b)) + 1);

  -- binary to Gray
  g1 <= b1 xor ('0' & b1(WIDTH-1 downto 1));
end compact_arch;
```

This code is independent of the input size (revision time $O(1)$) and uses a binary adder (of which there are many to choose from!)

Signed Addition with Status

The default '+' VHDL operator does not allow for *status signals*

Common status signals reflecting the result of the addition include

- *zero*: Is the result 0?
- *sign*: What is the sign of the result?
- *overflow*: Did the result overflow?

Also, *carry* signals (*carry in* and *out*) pass information between successive additions

Needed, for example, when you build a 64-bit adder from 8-bit adders

Given these status signals, it is important to note that *overflow* must be checked first because the other status signals are *invalid* in this case

The following deductions can be made

- If the two operands have **different sign** bits, then overflow is NOT possible
- If the two operands *and* the result have the same sign, then overflow did not occur
- If the two operands have the same sign *but* the result has a different sign, overflow **occurred**

Signed Addition with Status

The following logic expression captures the last condition, with s_a , s_b and s_s representing the signs of the a and b operands and the sign of the sum, s

$$\text{overflow} = (s_a \bullet s_b \bullet \overline{s_s}) + (\overline{s_a} \bullet \overline{s_b} \bullet s_s)$$

Note that *zero* may be true when it shouldn't be if *overflow* occurred, e.g., summing "1000" and "1000" using a 4-bit adder produces "0000"

Similar arguments hold for *sign* -- sign of the above is '0' but it should be '1', therefore, if overflow occurs, then the *sign* signal should be inverted

The *carry_in* and *carry_out* signals are appended to the right and left, resp.

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity adder_status is  
  port (  
    a,b: in std_logic_vector(7 downto 0);
```

Signed Addition with Status

```
    cin: in std_logic;
    sum: out std_logic_vector(7 downto 0);
    cout, zero, overflow, sign: out std_logic
);
end adder_status;

architecture arch of adder_status is
    signal a_ext, b_ext, sum_ext: signed(9 downto 0);
    signal ovf: std_logic;
    alias sign_a: std_logic is a_ext(8);
    alias sign_b: std_logic is b_ext(8);
    alias sign_s: std_logic is sum_ext(8);
begin

-- bit extend the operands on both sides
a_ext <= signed('0' & a & '1');
b_ext <= signed('0' & b & cin);
sum_ext <= a_ext + b_ext;
```

Signed Addition with Status

```
    ovf <= (sign_a and sign_b and (not sign_s)) or
           ((not sign_a) and (not sign_b) and sign_s);

    cout <= sum_ext(9);

-- Invert sign if overflow occurred
    sign <= sum_ext(8) when ovf='0' else
           not sum_ext(8);

-- zero is invalid if overflow occurred
    zero <= '1' when (sum_ext(8 downto 1)=0 and ovf='0')
           else '0';
    overflow <= ovf;

    sum <= std_logic_vector(sum_ext(8 downto 1));
end arch;
```

Simple Combinational Multiplier

A simple multiplier can be constructed using *first principles*

| | | | | | | | | |
|----------|----------|----------|----------|----------|----------|----------|----------|--------------|
| \times | | | | a_3 | a_2 | a_1 | a_0 | multiplicand |
| | | | | b_3 | b_2 | b_1 | b_0 | multiplier |
| | | | | a_3b_0 | a_2b_0 | a_1b_0 | a_0b_0 | |
| | | | a_3b_1 | a_2b_1 | a_1b_1 | a_0b_1 | | |
| | | a_3b_2 | a_2b_2 | a_1b_2 | a_0b_2 | | | |
| $+$ | a_3b_3 | a_2b_3 | a_1b_3 | a_0b_3 | | | | |
| | y_7 | y_6 | y_5 | y_4 | y_3 | y_2 | y_1 | y_0 |
| | | | | | | | | product |

Simple algorithm:

- Multiply the digits of the multiplier, $b_3b_2b_1b_0$ by the multiplicand by A , one at a time to obtain b_3*A , b_2*A , b_1*A and b_0*A

Given b_i can only be '0' or '1', the product can only be '0' or A

Multiplication is performed using the **and** operation, i.e., $b_i*A = (a_3b_i, a_2b_i, a_1b_i, a_0b_i)$

Simple Combinational Multiplier

Simple algorithm:

- Shift $b_i * A$ to the left i positions
- Add the shifted $b_i * A$ terms to obtain the final product

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity mult8 is  
  port (  
    a, b: in std_logic_vector(7 downto 0);  
    y: out std_logic_vector(15 downto 0)  
  );  
end mult8;  
  
architecture comb1_arch of mult8 is  
  constant WIDTH: integer:=8;  
  signal au, bv0, bv1, bv2, bv3, bv4, bv5, bv6, bv7:  
    unsigned(WIDTH-1 downto 0);
```


Simple Combinational Multiplier

```
signal p0,p1,p2,p3,p4,p5,p6,p7,prod:
    unsigned(2*WIDTH-1 downto 0);
begin

    au <= unsigned(a);
    bv0 <= (others=>b(0));
    bv1 <= (others=>b(1));
    bv2 <= (others=>b(2));
    bv3 <= (others=>b(3));
    bv4 <= (others=>b(4));
    bv5 <= (others=>b(5));
    bv6 <= (others=>b(6));
    bv7 <= (others=>b(7));
    p0 <="00000000" & (bv0 and au);
    p1 <="0000000" & (bv1 and au) & "0";
    p2 <="000000" & (bv2 and au) & "00";
    p3 <="00000" & (bv3 and au) & "000";
    p4 <="0000" & (bv4 and au) & "0000";
```

Simple Combinational Multiplier

```
p5 <="000" & (bv5 and au) & "00000";  
p6 <="00" & (bv6 and au) & "000000";  
p7 <="0" & (bv7 and au) & "0000000";  
prod <= ((p0+p1)+(p2+p3)) + ((p4+p5)+(p6+p7));  
y <= std_logic_vector(prod);  
end comb1_arch;
```

See text for alternative architecture, as well as examples of a *Hamming distance* circuit and *programmable priority encoder*