

Concurrent Signal Assignment Statements

This slide set covers the *concurrent signal assignment* statements, which include the **conditional signal assignment** and **selected signal assignment** stmts

Topics include

- Simple signal assignment statement (conditional assign. without a condition)
- Conditional signal assignment statement
- Selected signal assignment statement
- Conditional vs. selected signal assignment

Simple signal assignment statement

```
signal_name <= projected_waveform;
```

For example

```
-- y changes after a or b changes + 10 ns  
y <= a + b + 1 after 10 ns;
```

Timing info ignored in synthesis and δ -delay is used for

```
signal_name <= value_expression;
```

Simple Signal Assignment Statements


Other examples:

```
status <= '1';
```

```
even <= (p1 and p2) or (p3 and p4);
```

```
arith_out <= a + b + c - 1;
```

Implementation of last statement

 

Note that this may be simplified during synthesis and that the size of the synthesized circuit can vary significantly for different stmts

Also note that it is syntactically correct for a signal to appear on **both** sides of a concurrent signal assignment

Simple Signal Assignment Statements

For example:

```
q <= ((not q) and (not en)) or (d and en);
```

Here, the q signal takes the value of d when en is '1', otherwise it takes the *inverse* of itself

Although this is syntactically correct, the statement forms a *closed feedback loop* and should be **avoided**

It may synthesize to an internal state (memory) in cases where the next value of q depends on the previous value, e.g.,

```
q <= (q and (not en)) or (d and en);
```

Or it may *oscillate* (as is true of the statement above)

This is **REALLY BAD PRACTICE** because the circuit becomes sensitive to internal propagation delay of its elements

It also confuses the synthesis tools and complicates the testing process

Conditional Signal Assignment Statements

Simplified syntax:

```

signal_name <=
    value_expr_1 when boolean_expr_1 else
    value_expr_2 when boolean_expr_2 else
    value_expr_3 when boolean_expr_3 else
    ...
    value_expr_n
  
```

The *boolean_expr_i* return **true** or **false** and are each evaluated from top-to-bottom until one is found to be *true*

When this occurs, the *value_expr_i* is assigned to the *signal_name* signal

This type of statement can be represented by a **multiplexer** circuit

input	output
s	x
00	a
01	b
10	c
11	d

This is the truth table for an 8-bit, **4-to-1 multiplexer**

Here, *a*, *b*, *c*, and *d* are input signals

s is also an input, i.e., a 2-bit signal the input data to route to the output

Conditional Signal Assignment Statements

```
library ieee;  
use ieee.std_logic_1164.all;  
entity mux4 is  
  port (  
    a, b, c, d: in std_logic_vector(7 downto 0);  
    s: in std_logic_vector(1 downto 0);  
    x: out std_logic_vector(7 downto 0)  
  );  
end mux4;  
  
architecture cond_arch of mux4 is  
  begin  
    x <= a when (s="00") else  
      b when (s="01") else  
      c when (s="10") else  
      d;  
  end cond_arch;
```

Conditional Signal Assignment Statements

Note that the use of *std_logic* data type, which has 9 possible values, makes the last statement assign *d* to *x* under more conditions than the expected *s = "11"* case

In fact, since each bit of *s* can assume 9 values, there are actually $9*9 = 81$ conditions for the two bit sequence including "0Z", "UX", "0-", etc

Therefore, the last statement assigns *d* to *x* under 77 (81-4) additional conditions, but these conditions are ONLY possible in simulations

Except for the limited use of 'Z', the *metavalues* are ignored by synthesis software

Some synthesis software allows the following alternative expression

```
x <= a when (s="00") else  
      b when (s="01") else  
      c when (s="10") else  
      d when (s="11") else  
      'X' ;
```

Conditional Signal Assignment Statements

Binary decoder: An n -to- 2^n decoder has an n -bit input and a 2^n -bit output, where each bit of the *output* represents an *input* combination

input	output
s	x
0 0	0001
0 1	0010
1 0	0100
1 1	1000

```
library ieee;
use ieee.std_logic_1164.all;
entity decoder4 is
  port (
    s: in std_logic_vector(1 downto 0);
    x: out std_logic_vector(3 downto 0)
  );
end decoder4;
```

Conditional Signal Assignment Statements

```

architecture cond_arch of decoder4 is
  begin
    x <= "0001" when (s="00") else
      "0010" when (s="01") else
      "0100" when (s="10") else
      "1000";
  end cond_arch;

```

Both the MUX and decoder **are a better match** to *selected signal assignment* (later)

Priority encoder: Checks the input requests and generates the code of the request with *highest priority*

input r	output code	output active
1---	11	1
01--	10	1
001-	01	1
0001	00	1
0000	00	0

There are four input requests, $r(3)$, ..., $r(0)$

The outputs include a 2-bit signal (*code*), which is the binary code of the highest priority request and a 1-bit signal *active* that indicates if there is an active request

Conditional Signal Assignment Statements

The $r(3)$ has the highest priority, i.e., when asserted, the other three requests are ignored and the *code* signal becomes "11"

When $r(3)$ is **not** asserted, the second highest request, $r(2)$ is examined

The *active* signal is to distinguish the last case, when $r(0)$ is asserted and the case in which NO request is asserted

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity prio_encoder42 is  
  port (  
    r: in std_logic_vector(3 downto 0);  
    code: out std_logic_vector(1 downto 0);  
    active: out std_logic  
  );  
end prio_encoder42;
```

Conditional Signal Assignment Statements

```

architecture cond_arch of prio_encoder42 is
  begin
    code <= "11" when (r(3)='1') else
              "10" when (r(2)='1') else
              "01" when (r(1)='1') else
              "00";
    active <= r(3) or r(2) or r(1) or r(0);
  end cond_arch;

```

The priority structure of the conditional signal assignment matches well this functionality

A simple ALU

input ctrl	output result
0--	src0 + 1
100	src0 + src1
101	src0 - src1
110	src0 and src1
111	src0 or src1

Input signals include *ctrl*, *src0* and *src1*

Output signal is *result*

ALU performs 5 functions, 3 arithmetic and 2 Boolean

The input and output are interpreted as *signed* integers when arithmetic ops are selected

Conditional Signal Assignment Statements

We will use *std_logic* data type for portability reasons and convert it to the desired data type, e.g., *signed*, in the architecture body

Once the arithmetic operation is performed, the result is converted back to *std_logic*

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity simple_alu is  
  port (  
    ctrl: in std_logic_vector(2 downto 0);  
    src0, src1: in std_logic_vector(7 downto 0);  
    result: out std_logic_vector(7 downto 0)  
  );  
end simple_alu;
```

Conditional Signal Assignment Statements

```
architecture cond_arch of simple_alu is
  signal sum, diff, inc: std_logic_vector(7 downto 0);
begin
  -- note conversion to signed and back to std_logic
  inc <= std_logic_vector(signed(src0)+1);
  sum <= std_logic_vector(signed(src0)+signed(src1));
  diff <= std_logic_vector(signed(src0)-signed(src1));
  result <= inc when ctrl(2)='0' else
    sum when ctrl(1 downto 0)="00" else
    diff when ctrl(1 downto 0)="01" else
    src0 and src1 when ctrl(1 downto 0)="10"
    else src0 or src1;
end cond_arch;
```

The conditional signal assignment statement implements a priority structure

This type of structure is naturally realized easily by the *sequential execution* of a CPU when expressed in a traditional programming language (*temporal*)

Conditional Signal Assignment Statements

In hardware, a *priority-routing* structure implements the priority structure (*spatial*)

```
signal_name <=
    value_expr_1 when boolean_expr_1 else
    value_expr_2 when boolean_expr_2 else
    value_expr_3 when boolean_expr_3 else
    ...
    value_expr_n
```

In order to construct a conditional signal assignment statement, three groups of hardware are needed:


- Value expression circuits
- Boolean expression circuits
- Priority routing network

The *boolean expression* circuits are used to control the *priority routing network* which determines which of the *value expression* circuits are connected to the output

The priority routing network is implemented by a series of *2-to-1 multiplexers*

Conditional Signal Assignment Statements


A 2-to-1 abstract MUX

 

With $sel = \text{true}$, the n -bit signal $i1$ is routed to the output, otherwise $i0$ is routed

Consider the statement
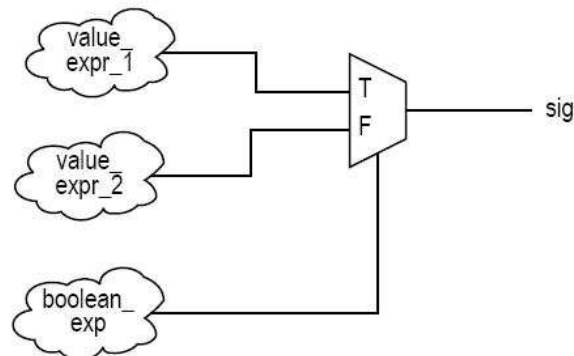
```
signal_name <= value_expr_1 when boolean_expr_1 else  
                value_expr_2;
```




Conditional Signal Assignment Statements

```

signal_name <= value_expr_1 when boolean_expr_1 else
               value_expr_2 when boolean_expr_2 else
               value_expr_3 when boolean_expr_3 else
               value_expr_4;

```

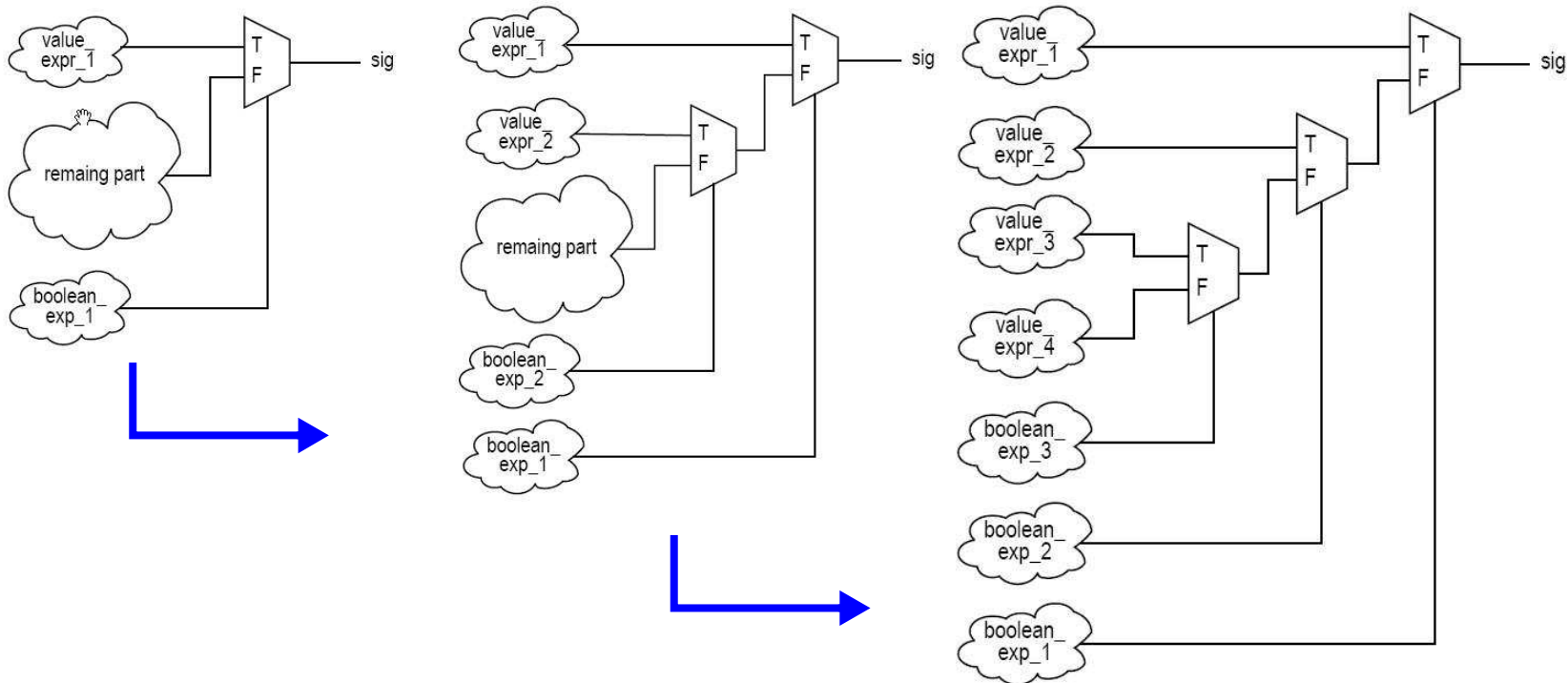


Basically, for each statement, another level is added

Bear in mind adding too many creates a long combinational delay

Conditional Signal Assignment Statements

Actual implementations

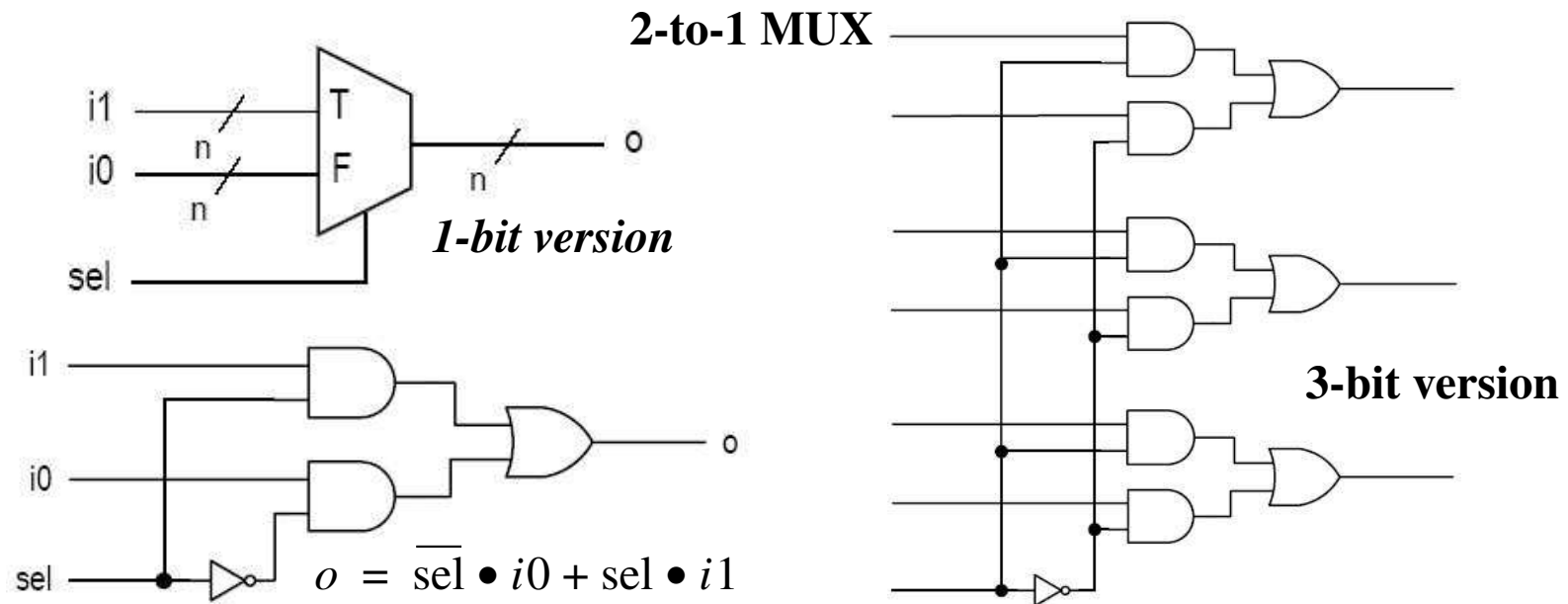

Consider

```
signal a, b, y: std_logic;
```

```
...
```

```
y <= '0' when a=b else '1';
```



How is the *condition part* actually implemented?

Conditional Signal Assignment Statements

The input type of $a=b$ is *std_logic* and the output type is Boolean

Although signals of type *std_logic* has nine values, during synthesis only '0' and '1' matter

  Logic '0' is used for **false** and logic '1' is used for **true**



$$y = \overline{(a \oplus b)} \cdot 1 + (a \oplus b) \cdot 0 \xrightarrow{\text{simplifies to}} y = (a \oplus b)$$

Consider



```
signal a, b, c, x, y, r: std_logic;
```

```
...
```

```
r <= a when x=y else  
    b when x>y else c;
```

Conditional Signal Assignment Statements

Conceptually

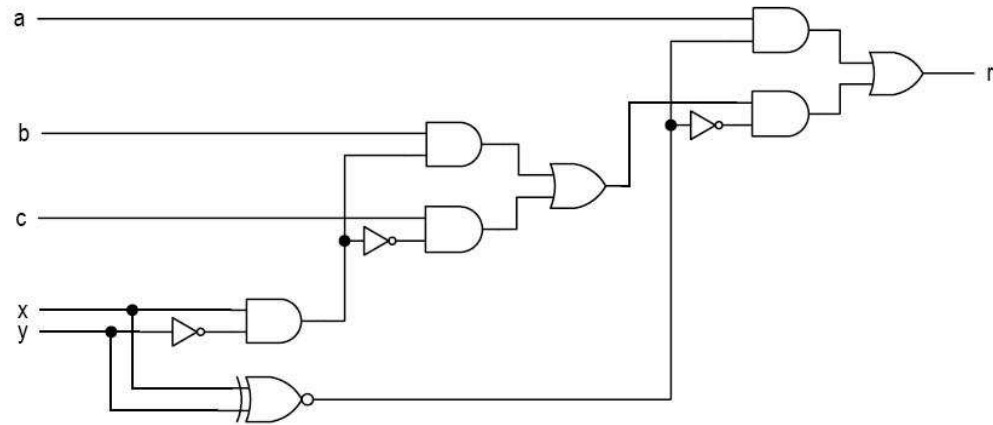 

Synthesize tools apply optimizations

Consider

```
signal a, b, r: unsigned(7 downto 0);
```

```
signal x, y: unsigned(3 downto 0);
```

...

```
r <= a+b when x+y>1 else
```


```
    a-b-1 when x>y and y!=0 else
```

```
    a+1;
```

...

Conditional Signal Assignment Statements

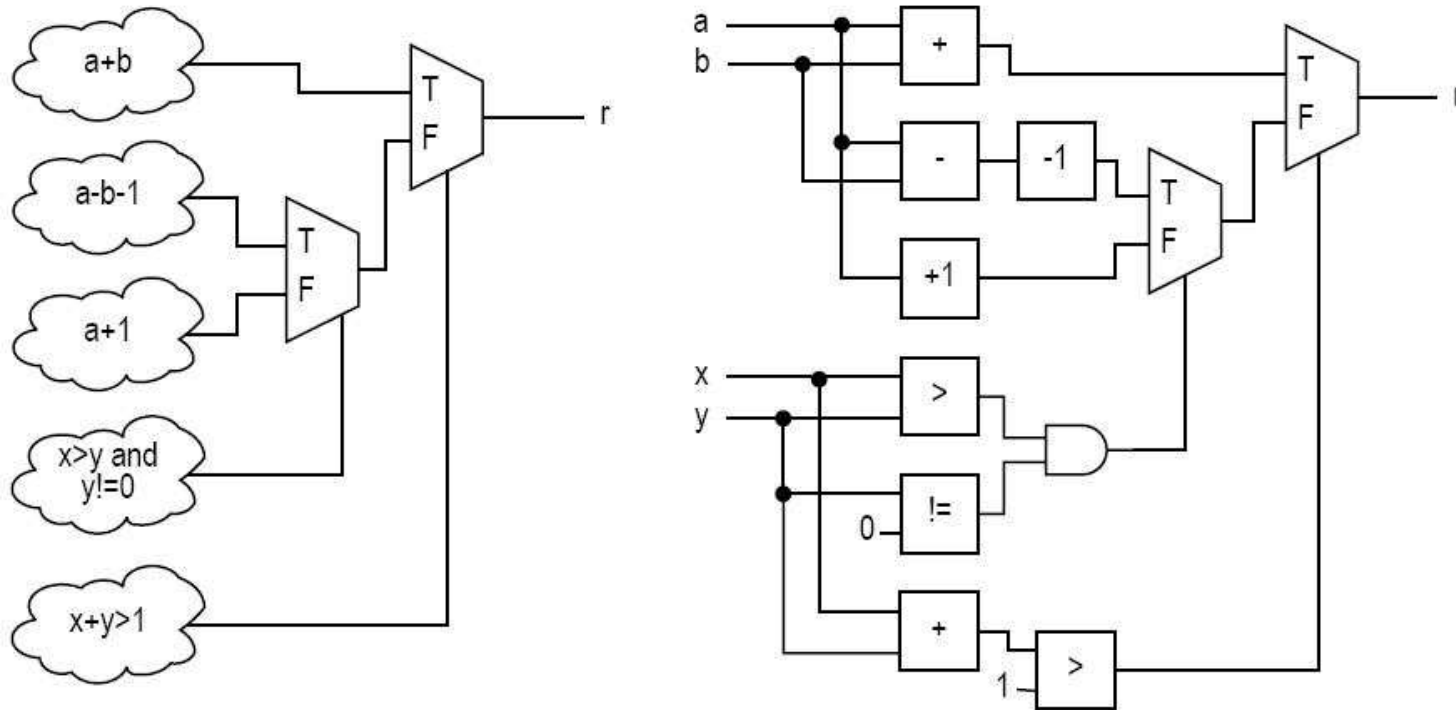Value and Boolean expressions are more involved



We can continue to refine the blocks on the left to gate-level components

Good coding practice can improve the implementation carried out by the synthesis tool dramatically (as we will see later)

Selected Signal Assignment Statements

Syntax

```
with select_expression select  
    signal_name <= value_expr_1 when choice_1,  
                    value_expr_2 when choice_2,  
                    value_expr_3 when choice_3,  
                    ...  
                    value_expr_n when choice_n;
```

Similar to a **case stmt** in a traditional programming language

The *select_expression* must produce a value of a discrete type or 1-D array

It can only have a finite number of possibilities

choice_i must be value of the data type, e.g., if *bit_vector(1 downto 0)* used in *select_expression*, then choices must be "00", "01", "10" and "11"

Choices must be **mutually exclusive** and **all inclusive**

others can be used as last *choice_n*

Selected Signal Assignment Statements

We saw this earlier in the conditional signal assignment material -- **entity** is the same

```
architecture sel_arch of mux4 is
```

```
  begin
```

```
    with s select
```

```
      x <= a when "00",
```

```
        b when "01",
```

```
        c when "10",
```

```
        d when others;
```

```
  end sel_arch;
```

Remember *std_logic* has 9 possible values so it's **not** possible to list the last entry as

```
    d when "11";
```

Alternatively (last line ignored during synthesis)

```
    x <= a when "00",
```

```
        b when "01",
```

```
        c when "10",
```

```
        d when "11",
```

```
        'X' when others; -- can also use '--'
```

Selected Signal Assignment Statements

For the **binary decoder** (2-to 2^2) we saw earlier

```
architecture sel_arch of decoder4 is  
  begin  
    with s select  
      x <= "0001" when "00",  
          "0010" when "01",  
          "0100" when "10",  
          "1000" when others;  
  end sel_arch;
```

For the **priority encoder** (4-to-2)

```
architecture sel_arch of prio_encoder42 is  
  begin  
    with r select  
      code <= "11" when "1000" | "1001" | "1010" | "1011" |  
                  "1100" | "1101" | "1110" | "1111",  
              "10" when "0100" | "0101" | "0110" | "0111",  
              "01" when "0010" | "0011",  
              others <= "00";
```

Selected Signal Assignment Statements

```
        "00" when others;  
    active <= r(3) or r(2) or r(1) or r(0);  
end sel_arch;
```

Recall that "11" is assigned to *code* if *r(3)* is '1'

The shortcut taken in the conditional assignment stmt, i.e.,

```
code <= "11" when (r(3)='1') else
```

can NOT be taken here and all 8 values that have a '1' for *r(3)* must be listed, e.g.,
"1000", "1001", "1010", "1011", ... "1111"

You might be tempted to make this more compact by using the '-' (don't-care) as

```
with r select  
code <= "11" when "1---",  
        "10" when "01--",  
        "01" when "001-",  
        "00" when others;
```

Selected Signal Assignment Statements

But this doesn't work since the '-' value never occurs in a real circuit

Because of this, the first three stmts are never executed and the whole clause becomes equivalent to

```
code <= "00";
```

The simple ALU:

```
architecture sel_arch of simple_alu is  
  signal sum, diff, inc: std_logic_vector(7 downto 0);  
  begin  
    inc <= std_logic_vector(signed(src0)+1);  
    sum <= std_logic_vector(signed(src0)+signed(src1));  
    diff <= std_logic_vector(signed(src0)-signed(src1));  
    with ctrl select  
      result <=  
        inc when "000"|"001"|"010"|"011",  
        sum when "100",  
        diff when "101",
```


Selected Signal Assignment Statements

```
        src0 and src1 when "110",  
        src0 or src1 when others; -- "111"  
end sel_arch;
```

Truth Table: A new application that selected signal assignment can implement

input	output
a b	y
00	0
01	1
10	1
11	1

```
library ieee;  
use ieee.std_logic_1164.all;  
entity truth_table is  
    port (  
        a, b: in std_logic;  
        y: out std_logic  
    );  
end truth_table;
```


Selected Signal Assignment Statements

```

architecture a of truth_table is
  signal tmp: std_logic_vector(1 downto 0);
begin
  tmp <= a & b; -- concatenate a and b
  with tmp select
    y <= '0' when "00", -- rows of the truth table
      '1' when "01",
      '1' when "10",
      '1' when others; -- "11"
end a;

```

 The conceptual implementation can be realized by a **multiplexing circuit**



Abstract (k+1)-to-1 MUX


Instead of **true** and **false** as *sel* signal choices,
sel is a data type of (k+1) values, c_0 through c_k

Selected Signal Assignment Statements

Consider a *select_expression* with a data type of 5 values: c0, c1, c2, c3, c4

```
with select_expression select
```
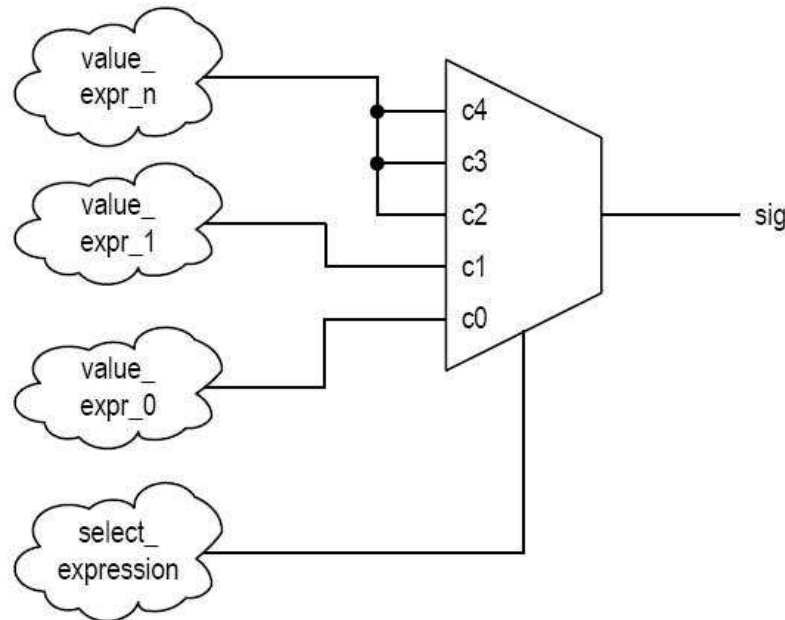
```
  signal_name <= value_expr_0 when c0,  
                value_expr_1 when c1,  
                value_expr_n when others;
```




All selected signal assignment statements have similar conceptual diagrams

You just need to be careful because the number of select items may become large and there are limitations here

Selected Signal Assignment Statements


Examples, 4-to-1 MUX

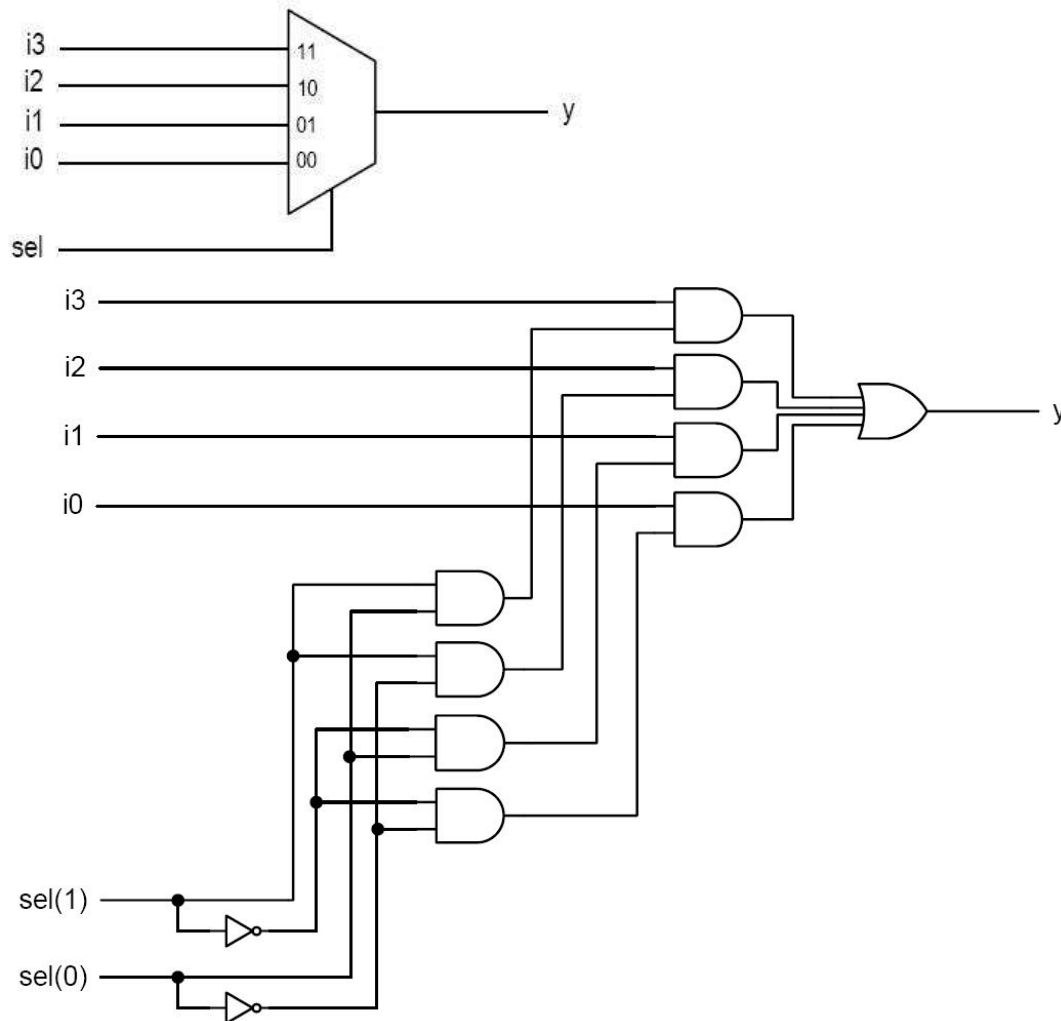

Here, the port names for the sel signal are assigned "00", "01", "10" and "11"

Selected Signal Assignment Statements
 
```
signal a, b, r: unsigned(7 downto 0);  
signal s: std_logic_vector(1 downto 0);  
...  
with s select  
    r <= a+1 when "11",  
        a-b-1 when "10",  
        a+b when others;
```



Let's compare and look at how to convert between **conditional** and **selected** signal assignment stmts

Conditional and Selected Signal Assignment Statements

Although the two statements imply a different routing structure (priority vs. non-priority), it is always possible to convert between the two

Consider

```
with sel select  
    sig <= value_expr_0 when c0,  
          value_expr_1 when c1 | c3 | c5,  
          value_expr_2 when c2 | c4,  
          value_expr_n when others;
```

The choices can be described using Boolean expression

```
sig <= value_expr_0 when (sel=c0) else  
      value_expr_1 when (sel=c1) or (sel=c3) or  
                        (sel=c5) else  
      value_expr_2 when (sel=c2) or (sel=c4) else  
      value_expr_n;
```

Conditional and Selected Signal Assignment Statements

To convert in the other direction requires a little more work

```
signal_name <=
    value_expr_0 when boolean_expr_0 else
    value_expr_1 when boolean_expr_1 else
    value_expr_2 when boolean_expr_2 else
    value_expr_n
```

We create a 3-bit auxiliary selection signal where each bit represents a Boolean expression as a means of preserving the desired priority

```
sel(2) <= '1' when bool_expr_0 else 0;
sel(1) <= '1' when bool_expr_1 else 0;
sel(0) <= '1' when bool_expr_2 else 0;
with sel select
    sig <= value_expr_0 when "100" | "101" | "110" | "111",
        value_expr_1 when "010" | "011",
        value_expr_2 when "001",
        value_expr_n when others;
```

This same structure works for any 3-when clause conversion

Conditional and Selected Signal Assignment Statements

Use **selected signal assignment** statement for circuits described by truth tables or truth-table like functions, such as decoders and multiplexers

Using it for priority structures can be inefficient

```
with r select  
    code <= "11" when "1000" | "1001" | "1010" | "1011" |  
                    "1100" | "1101" | "1110" | "1111",  
    ...
```

Here, 8 of the 16 ports of the multiplexer are connected to an identical expression

Use **conditional signal assignment** for circuits that need to give preferential treatment for certain conditions or to prioritize operations

```
pc_next <=  
    pc_reg + offset when (state=jump and a=b) else  
    pc_reg + 1 when (state=skip and flag='1') else  
    ...
```

As you can see, it can handle complicated conditions

Conditional and Selected Signal Assignment Statements

Using conditional signal assignment for truth tables is not efficient because it **over-specifies** the function

```
x <= a when (s="00") else  
      b when (s="01") else  
      c when (s="10") else  
      d;
```

But this can be written as

```
x <= c when (s="10") else  
      b when (s="01") else  
      a when (s="00") else  
      d;
```

Or in any other combination

This is **overspecified** because the conditional signal assignment gives priority to the first *when* clause but it is **not** needed

This may cause additional circuitry to be added during synthesis (BAD PRACTICE)