

Sequential Circuit Design: Principle

Outline:

- Overview of sequential circuits
- Synchronous circuits
- Danger of synthesizing asynchronous circuit
- Inference of basic memory elements
- Simple design examples
- Timing analysis
- Alternative one-segment coding style
- Use of variable for sequential circuit

Overview of sequential circuit

- Combinational vs sequential circuit

Sequential circuit: output is a function of current input and state (memory)

- Basic memory elements



D latch

D FF (Flip-Flop)


RAM (not possible to derive a portable, device-independent VHDL code to infer a RAM module)

D Latch

 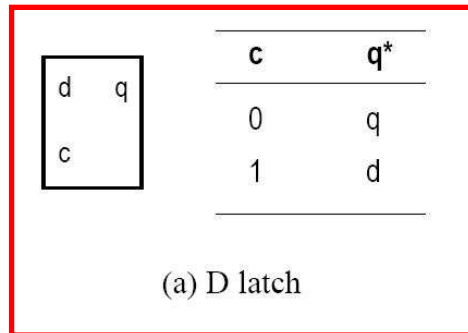
D latch is a *level* sensitive memory element, while the **D flip-flop (FF)** is an *edge* sensitive memory element



(b) pos-edge triggered D FF

 

(c) neg-edge triggered D FF

 


(d) D FF with asynchronous reset


Note that for the D latch, next state q^* is d when the control signal c (often clock) is high, while q^* is q when c is low

D Latch

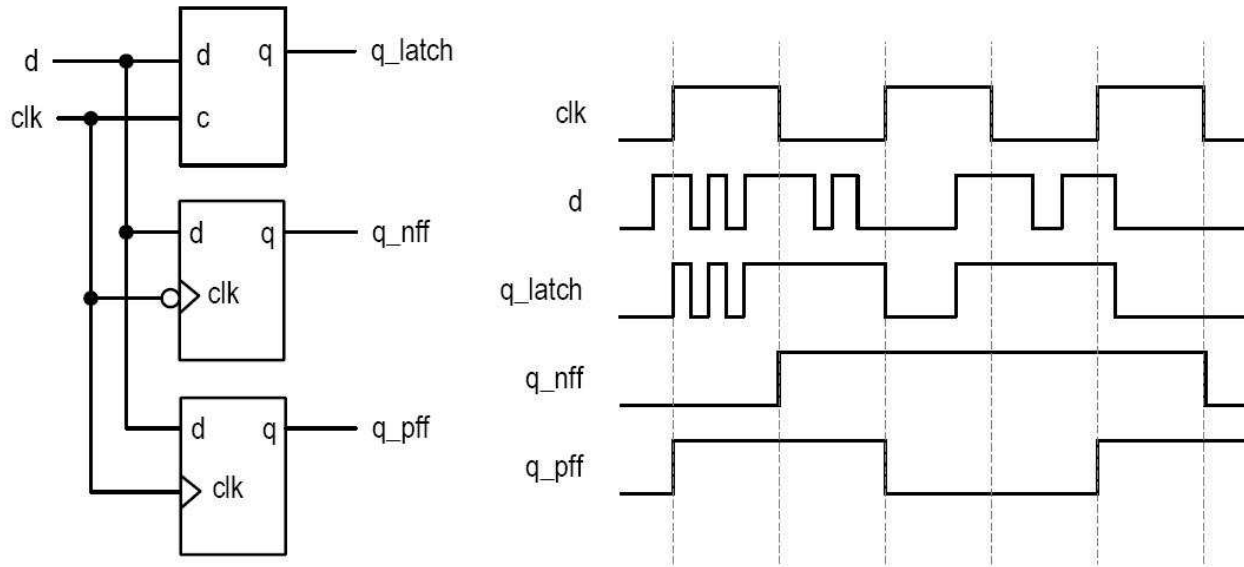Timing diagram for D-latch -- note that d is sampled and stored on falling edge of c .



 Since the latch is "transparent" when c is asserted, it may cause *racing* if a loop exists in the circuit




Cannot be used to *swap* data because of loop


Not often used in synthesis because of this

D Flip Flop (FF)

 
The D FF is only *activated* when the clk signal changes from 0 to 1.




(a) D latch

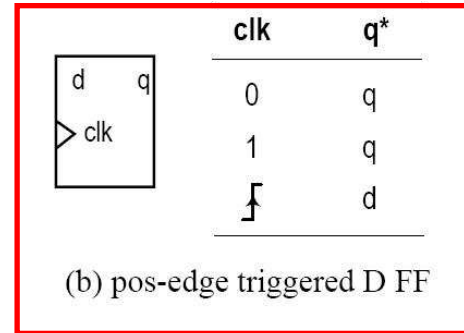

(b) pos-edge triggered D FF

 

(c) neg-edge triggered D FF

 

(d) D FF with asynchronous reset

Activation implies it samples the value on its d input, stores the value in its memory and propagates the value to its output q

D Flip Flop (FF)


D FF have advantages

- *glitches* on *d* do **not** effect the state of the memory
- There is no **race** condition -- swap circuits actually work

D FF disadvantages

- About twice as large as a D latch


Timing behavior of a D FF:

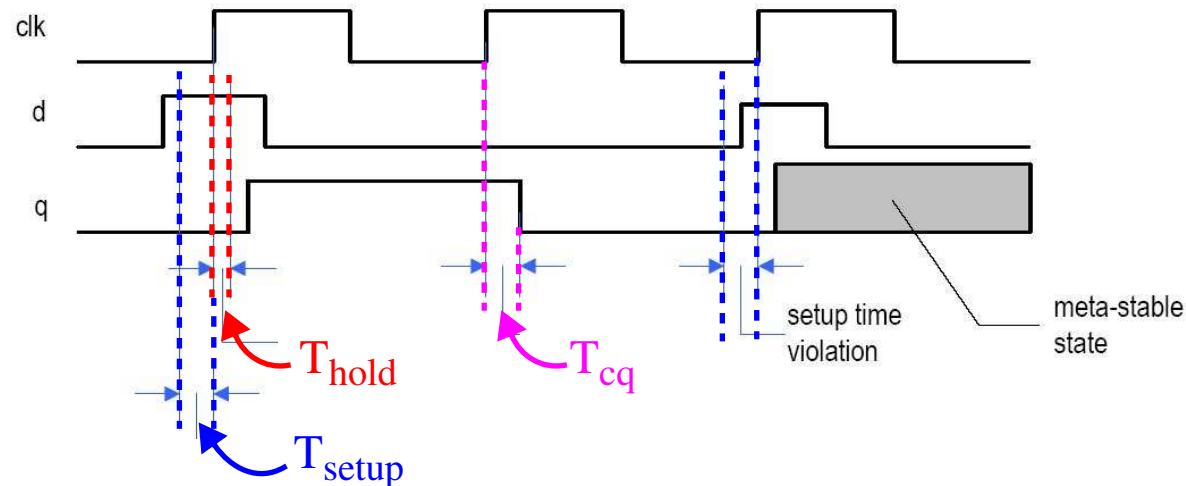

- Clock-to-q delay (T_{cq}): Delay required for sampled *d* value to show up on *q*

D Flip Flop (FF)

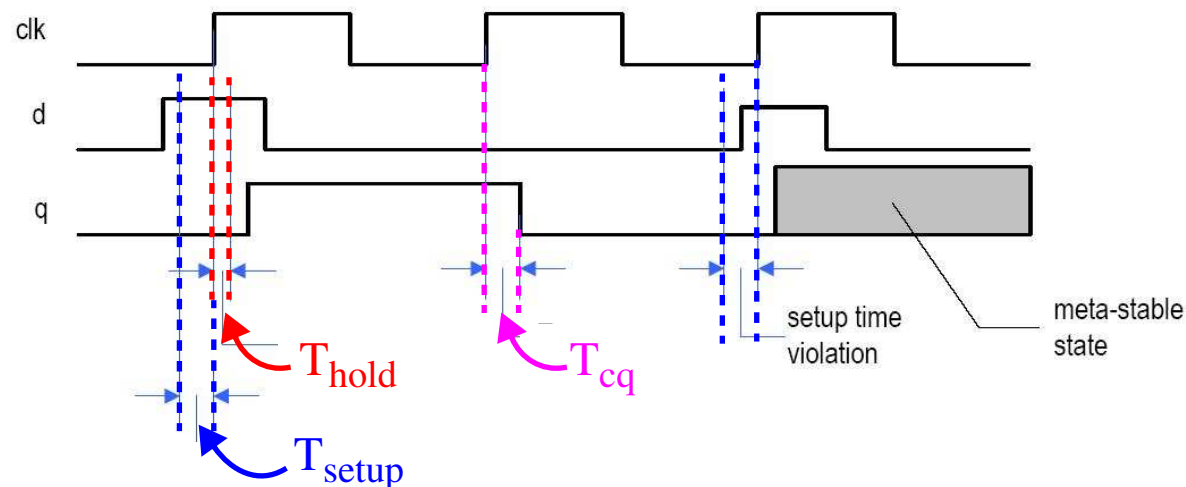- Setup time (T_{setup}): time *interval* that d must be stable for **before** the rising edge of clock
- Hold time (T_{hold}): time *interval* that d must be stable for **after** the rising edge.



T_{cq} corresponds to the propagation delay of a combinational circuit, while T_{setup} and T_{hold} are **timing constraints** -- d must be stable for a time interval around clk

If d changes during this interval, a *setup time* or *hold time* violation occurs and the D FF may enter a **metastable** state (q is neither a 0 or 1)

The Clock Signal

The clock signal plays a key role in sequential circuit design

Systems can be classified according to the clock signal arrangement

Globally synchronous circuit

All memory elements (D FFs) are controlled (*synchronized*) by a common global clock signal (most popular)

Globally asynchronous but locally synchronous circuit (GALS)

Used in cases in which the components of the design are spread too far apart to allow a single *synchronous* clock -- a globally asynchronous circuit results

However, the smaller subsystems use a synchronous clock internally

Special interface circuits needed between subsystems to ensure proper operation

Globally asynchronous circuits

No clock is used to coordinate the memory elements


The Clock Signal

Globally asynchronous circuits

There are two categories

- Systems that do not use the clock in a disciplined manner, for example, a *ripple counter*: clock port of an FF is connected to the *q* output of previous FF
Poor design and not recommended
- Systems that contain 'clockless' memory components such as the latch or a combinational circuit with feedback loops (*asynchronous circuit*)
Proper design is entirely different to synchronous circuits not recommended for HDL synthesis either

Synchronous circuit

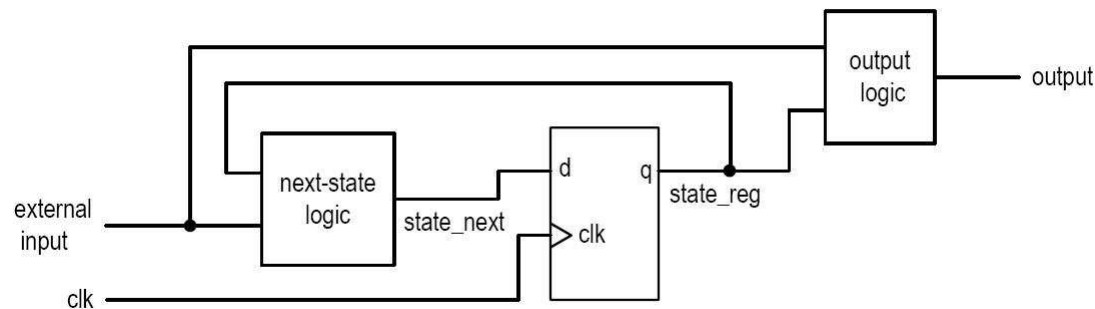

State registers (state_reg)
represent the memory elements

Next state logic
represent the combinational circuit that determines *state_next*

Synchronous Circuits

Operation is as follows:

- At the rising edge of the clock, *state_next* is sampled and stored into the register (and becomes the new value of *state_reg*)
- The external *inputs* and *state_reg* signals propagate through **next-state** and **output** logic to determine the new values of the *state_next* and *output* signals
- At the rising edge of the clock, the new value of *state_next* is sampled and stored and the process repeats

Note that the clock **period** needs to be large enough to accommodate the propagation delay of the *next-state* logic, the *clock-to-q* delay and the *setup time* of the FFs

Advantages of synchronous design

- A single global clock makes the task of satisfying the *timing constraints* of a design with of *thousands* of FFs manageable and doable
- The synchronous model separates the combinational components from the memory elements, making it possible to treat the combinational part by itself
- Propagation delay anomalies such as *hazards* can be dealt with easily by focusing on the worst case timing behavior

Synchronous Circuits

Therefore, the synchronous model reduces a complex sequential circuit to a single closed feedback loop and greatly simplifies the design process

Types of synchronous circuits

- **Regular** sequential circuit

State representation, transitions and next-state logic have a simple, regular pattern, as in an incrementor or shift register

- **Random** sequential circuit (FSM)

More complicated state transitions and no special relationship between states and their binary representations -- next-state logic is *random*

- **Combined** sequential circuit (FSM with a Data path, FSMD -- RTL)

Combines regular sequential circuit and an FSM, with FSM acting as control for the sequential circuit

Danger of Synthesizing an Asynchronous Circuit

Consider the D Latch described earlier

We can write VHDL code as follows to represent it

Danger of Synthesizing an Asynchronous Circuit

d	q
c	

c	q*
0	q
1	d

(a) D latch

```

library ieee;
use ieee.std_logic_1164.all;
entity dlatch is
  port (
    c: in std_logic;
    d: in std_logic;
    q: out std_logic
  );
end dlatch;

architecture demo_arch of dlatch is
  signal q_latch: std_logic;
begin

```

Danger of Synthesizing an Asynchronous Circuit



```

process (c, d, q_latch)
  begin
    if ( c='1' ) then
      q_latch <= d;
    else
      q_latch <= q_latch;
    end if;
  end process;
  q <= q_latch;
end demo_arch;

```

Synthesis software will recognize this as the code for a D latch and should infer a **predesigned** D-latch from the cell library

  But what if we try to synthesis it from scratch, using simple gates?




Danger of Synthesizing an Asynchronous Circuit

Here we see the implementation is combinational except for that the *output* is looped around as an input

Unfortunately, there is a serious *timing* problem with this circuit

 Assume all gates have a propagation delay of T and c , d and q are initially '1'



What happens when c changes from '1' to '0' at time t_0 ?

From the function table, q should be latched to the value of d ('1')

- 1) At t_0 , c changes to '0'
- 2) At t_1 , (after delay T), dc and cn change
- 3) At t_2 , (after delay $2T$), qcn changes (due to cn) and q changes (due to dc)
- 4) At t_3 , (after delay $3T$), q changes (due to qcn) and qcn changes (due to q)


Therefore, output q oscillates at period of $2T$ ←

Inference of Basic Memory Elements

You should use the following 'templates' to create latches and FFs, so that the *pre-designed* library cells are inferred by the synthesis tools.

D Latch

 - Eliminate the *else* branch to create a latch



(a) D latch

```

library ieee;
use ieee.std_logic_1164.all;
entity dlatch is
  port (
    c: in std_logic;
    d: in std_logic;
    q: out std_logic
  )

```

Inference of Basic Memory Elements


```
    );  
end dlatch;  
  
architecture arch of dlatch is  
    begin  
        -- c and d in sens. list b/c process sens. to both  
        process (c, d)  
            begin  
                if (c='1') then  
                    q <= d;  
                end if;  
            end process;  
    end arch;
```

Pos Edge-Triggered D FF

- No else branch -- NOTE **sensitivity** list

```
library ieee;  
use ieee.std_logic_1164.all;
```

Inference of Basic Memory Elements

 

(b) pos-edge triggered D FF

```

entity dff is
  port (
    clk: in std_logic;
    d: in std_logic;
    q: out std_logic
  );
end dff;

architecture arch of dff is
  begin
    process(clk) -- d not needed b/c process does nothing
      begin      -- when d changes (unlike latch)


```


Inference of Basic Memory Elements

```

-- 'event is true when clk changes, clk='1' is true when
-- NEW value of clk is '1' -- together means rising edge
    if (clk'event and clk='1') then -- can also use
        q <= d;                        -- rising_edge(clk)
    end if;                            -- if std_logic_logic_1164 incl.
end process;
end arch;

```

 Neg Edge-Triggered D FF

clk	q*
0	q
1	q
↓	d

...

```

if (clk'event and clk='0') then -- can also use
...                                -- falling_edge(clk)

```

Inference of Basic Memory Elements

D FF with Asynchronous Reset

- No else branch -- NOTE sensitivity list

	reset	clk	q*
d	1	-	0
q	0	0	q
clk	0	1	q
reset	0	\downarrow	d

```

library ieee;
use ieee.std_logic_1164.all;
entity dffr is
  port (
    clk: in std_logic;
    reset: in std_logic;
    d: in std_logic;
    q: out std_logic
  );
end dffr;

```

Inference of Basic Memory Elements

```
architecture arch of dffr is  
  begin  
    process (clk, reset)  
      begin  
        if (reset='1') then  
          q <= '0';  
        elsif rising_edge(clk) then  
          q <= d;  
        end if;  
      end process;  
  end arch;
```

Register

- Multiple D FFs with same clock and reset

```
library ieee;  
use ieee.std_logic_1164.all;
```


Inference of Basic Memory Elements

```
entity reg8 is
  port (
    clk, reset: in std_logic;
    d: in std_logic_vector(7 downto 0);
    q: out std_logic_vector(7 downto 0)
  );
end reg8;

architecture arch of reg8 is
  begin
    process (clk, reset)
      begin
        if (reset='1') then
          q <= (others=>'0');
        elsif (clk'event and clk='1') then
          q <= d;
        end if;
      end process; end arch;
```

Simple Design Examples

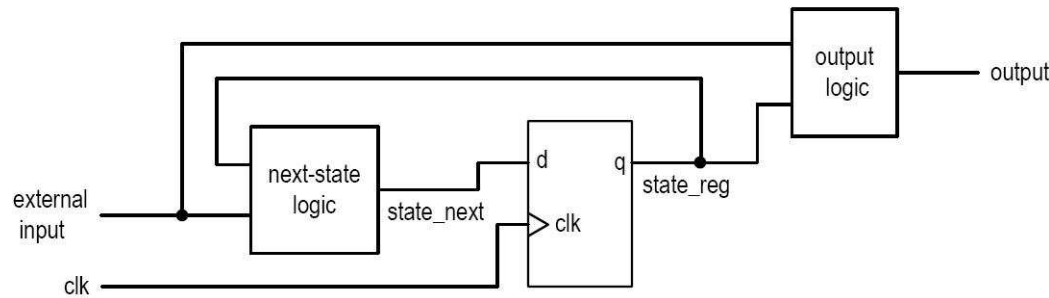Easiest way to create a sequential circuit is to follow the block diagram




- Build the register
- Code the next-state and output logic (combinational circuits)

D FF with Sync Enable

- Note that the *en* is sampled on rising edge of clock

reset	clk	en	q*
1	-	-	0
0	0	-	q
0	1	-	q
0	⌈	0	q
0	⌈	1	d

(a) Function table

 

(b) Conceptual diagram

If *en* is '0', or is changing from '0' to '1', FF keeps *q*

If *en* is '1', or is changing from '1' to '0', FF stores *q_next*

Simple Design Examples

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity dff_en is  
  port (  
    clk: in std_logic;  
    reset: in std_logic;  
    en: in std_logic;  
    d: in std_logic;  
    q: out std_logic  
  );  
end dff_en;  
  
architecture two_seg_arch of dff_en is  
  signal q_reg: std_logic;  
  signal q_next: std_logic;  
begin
```

Simple Design Examples

```
-- D FF
process (clk, reset)
  begin
    if (reset='1') then
      q_reg <= '0';
    elsif (clk'event and clk='1') then
      q_reg <= q_next;
    end if;
  end process;

-- next-state logic
q_next <= d when en ='1' else
      q_reg;


-- output logic
q <= q_reg;
end two_seg_arch;
```

Simple Design Examples

Toggle (T) FF -- t is sampled at rising edge

reset	clk	t	q*
1	-	-	0
0	0	-	q
0	1	-	q
0	f	0	q
0	f	1	q'

(a) Function table

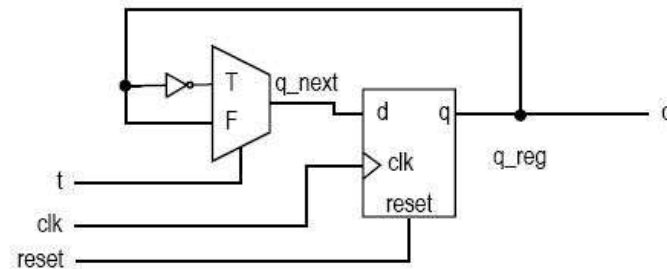

(b) Conceptual diagram

```

library ieee;
use ieee.std_logic_1164.all;
entity tff is
  port (
    clk: in std_logic;
    reset: in std_logic;
    t: in std_logic;
    q: out std_logic
  );
end tff;

```


Simple Design Examples

```
architecture two_seg_arch of tff is
  signal q_reg: std_logic;
  signal q_next: std_logic;
begin


  -- D FF
  process(clk, reset)
    begin
      if (reset='1') then
        q_reg <= '0';
      elsif (clk'event and clk='1') then
        q_reg <= q_next;
      end if;
    end process;

  -- next-state logic
  q_next <= q_reg when t='0' else
    not(q_reg);
```

Simple Design Examples

```
-- output logic
q <= q_reg;
end two_seg_arch;
```

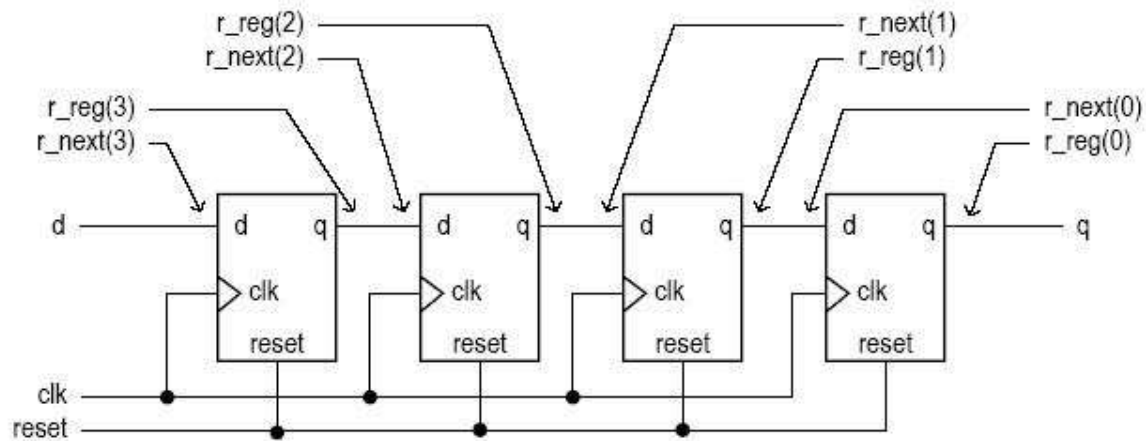
Free-Running Shift Register (no control signals)



Can be used to carry out parallel-to-serial conversion


Conceptually, we can re-arrange the FFs into a column and treat them as a single memory block (see below)

Simple Design Examples

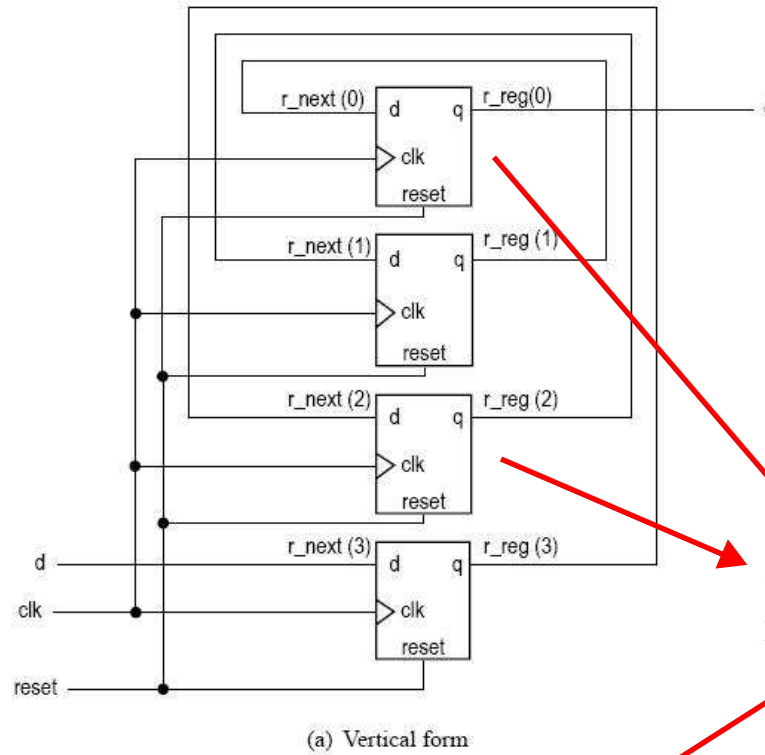

Combinational logic

Collapse into memory block

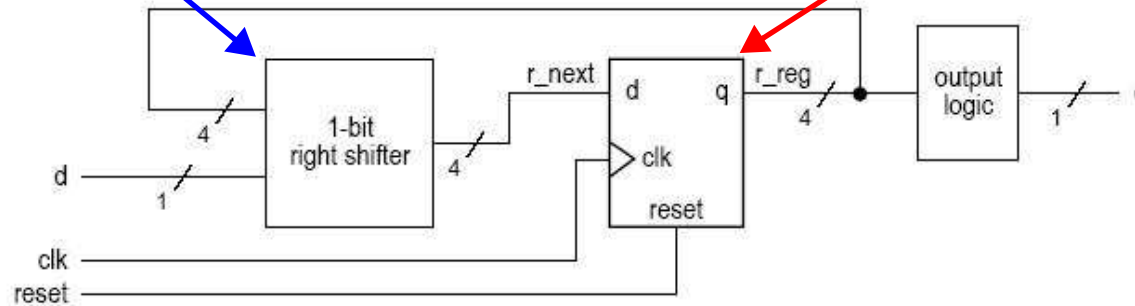

Simple Design Examples

```
library ieee;
use ieee.std_logic_1164.all;
entity shift_right_register is
  port (
    clk, reset: in std_logic;
    d: in std_logic;
    q: out std_logic
  );
end shift_right_register;

architecture two_seg_arch of shift_right_register is
  signal r_reg: std_logic_vector(3 downto 0);
  signal r_next: std_logic_vector(3 downto 0);
begin

  -- register
  process(clk, reset)
    begin
```

Simple Design Examples

```
if (reset='1') then
    r_reg <= (others=>'0');
elsif (clk'event and clk='1') then
    r_reg <= r_next;
end if;
end process;


-- next-state logic (shift right 1 bit)
r_next <= d & r_reg(3 downto 1);

-- output
q <= r_reg(0);
end two_seg_arch;
```

Simple Design Examples

Universal Shift Register

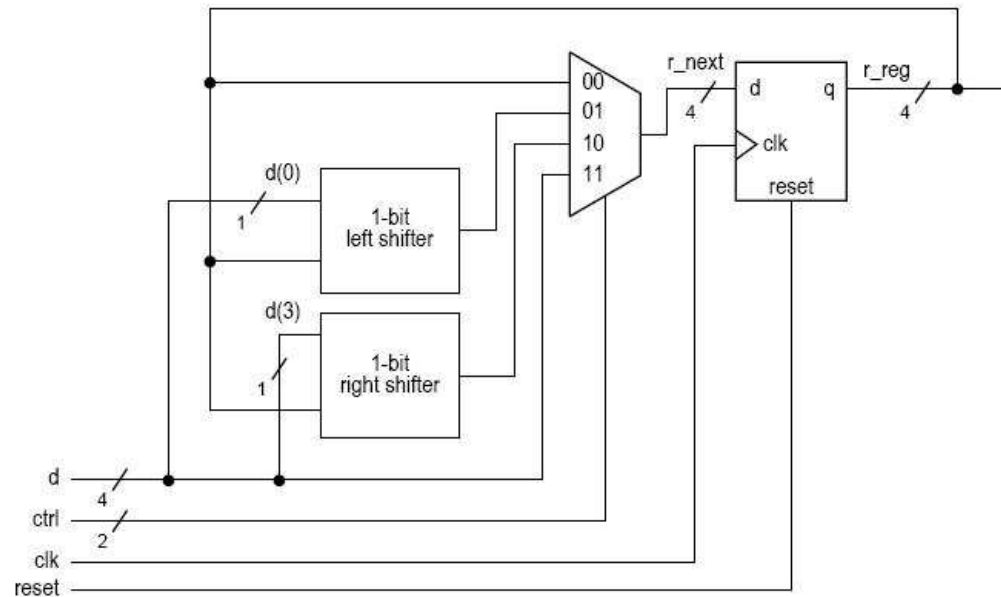- Designed to implement 4 ops: parallel load, shift right, shift left, pause



```

library ieee;
use ieee.std_logic_1164.all;

entity shift_register is
  port (
    clk, reset: in std_logic;

```

Simple Design Examples

```
    ctrl: in std_logic_vector(1 downto 0);
    d: in std_logic_vector(3 downto 0);
    q: out std_logic_vector(3 downto 0)
);
end shift_register;

architecture two_seg_arch of shift_register is
    signal r_reg: std_logic_vector(3 downto 0);
    signal r_next: std_logic_vector(3 downto 0);
begin

    -- register
    process(clk, reset)
        begin
            if (reset='1') then
                r_reg <= (others=>'0');
            elsif (clk'event and clk='1') then
                r_reg <= r_next;
            end if;
        end process;
    end architecture two_seg_arch;
```

Simple Design Examples

```
        end if;
    end process;

-- next-state logic
with ctrl select
    r_next <=
        r_reg                                when "00", -- no op
        r_reg(2 downto 0) & d(0)             when "01", -- sft left
        d(3) & r_reg(3 downto 1)             when "10", -- sft right
        d                                    when others;

-- output
q <= r_reg;
end two_seg_arch;
```


Simple Design Examples**Arbitrary Sequence Counter**

input pattern	output pattern
000	011
011	110
110	101
101	111
111	000

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity arbi_seq_counter4 is  
    port (  
        clk, reset: in std_logic;  
        q: out std_logic_vector(2 downto 0)  
    );  
end arbi_seq_counter4;
```

Simple Design Examples

```
architecture two_seg_arch of arbi_seq_counter4 is
  signal r_reg: std_logic_vector(2 downto 0);
  signal r_next: std_logic_vector(2 downto 0);
begin

  -- register
  process(clk, reset)
    begin
      if (reset='1') then
        r_reg <= (others=>'0');
      elsif (clk'event and clk='1') then
        r_reg <= r_next;
      end if;
    end process;
```

Simple Design Examples

```
-- next-state logic
r_next <= "011" when r_reg="000" else
         "110" when r_reg="011" else
         "101" when r_reg="110" else
         "111" when r_reg="101" else
         "000"; -- r_reg="111"

-- output logic
q <= r_reg;
end two_seg_arch;
```

Free-Running Binary Counter

- With a *max_pulse* output: asserted when counter is all '1's

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
```

Simple Design Examples

```
entity binary_counter4_pulse is
  port (
    clk, reset: in std_logic;
    max_pulse: out std_logic;
    q: out std_logic_vector(3 downto 0)
  );
end binary_counter4_pulse;

architecture two_seg_arch of binary_counter4_pulse is
  signal r_reg: unsigned(3 downto 0);
  signal r_next: unsigned(3 downto 0);
begin

  -- register
  process(clk, reset)
  begin
    if (reset='1') then
      r_reg <= (others=>'0');
    
```

Simple Design Examples

```
        elsif (clk'event and clk='1') then
            r_reg <= r_next;
        end if;
    end process;

    -- next-state logic
    r_next <= r_reg + 1;

    -- output logic
    q <= std_logic_vector(r_reg);
    max_pulse <= '1' when (r_reg="1111") else
        '0';
end two_seg_arch;
```


Note that it 'wraps' automatically

Poor practice -- may confuse some synthesis tools b/c **mod** op is not synthesizable

```
r_next <= (r_reg + 1) mod 16;
```

Simple Design Examples

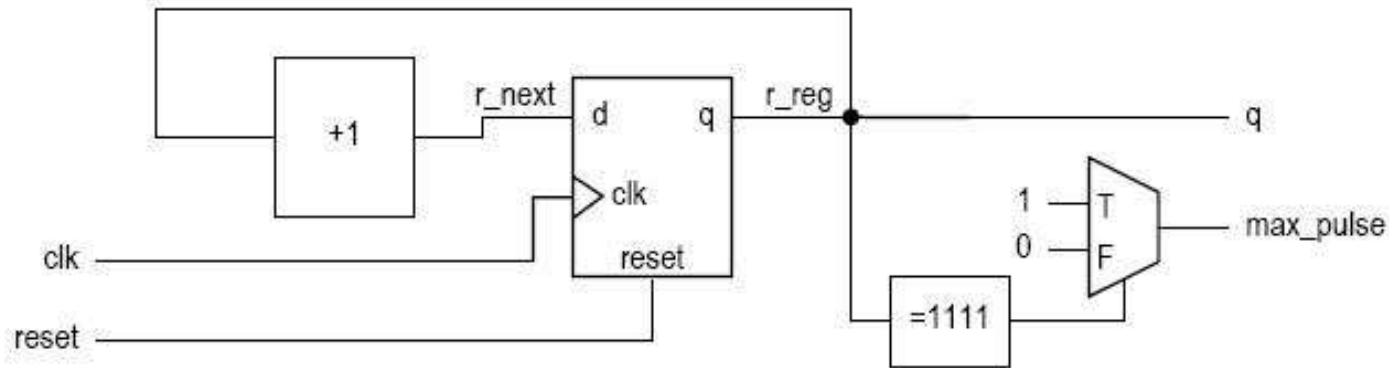RTL schematic of free running binary counter



Binary Counter

- Bells & whistles

syn_clr	load	en	q*	operation
1	—	—	00...00	synchronous clear
0	1	—	d	parallel load
0	0	1	q+1	count
0	0	0	q	pause

Simple Design Examples

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity binary_counter4_feature is  
  port (  
    clk, reset: in std_logic;  
    syn_clr, en, load: in std_logic;  
    d: in std_logic_vector(3 downto 0);  
    q: out std_logic_vector(3 downto 0)  
  );  
end binary_counter4_feature;  
  
architecture two_seg_arch of binary_counter4_feature is  
  signal r_reg: unsigned(3 downto 0);  
  signal r_next: unsigned(3 downto 0);  
begin
```

Simple Design Examples

```
-- register
process (clk, reset)
  begin
    if (reset='1') then
      r_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;

-- next-state logic
r_next <= (others=>'0') when syn_clr='1' else
  unsigned(d) when load='1' else
  r_reg + 1 when en = '1' else
  r_reg;
-- output logic
q <= std_logic_vector(r_reg);
end two_seg_arch;
```


Simple Design Examples**Decade (mod-10) Counter**

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity mod10_counter is
  port (
    clk, reset: in std_logic;
    q: out std_logic_vector(3 downto 0)
  );
end mod10_counter;

architecture two_seg_arch of mod10_counter is
  constant TEN: integer := 10;
  signal r_reg: unsigned(3 downto 0);
  signal r_next: unsigned(3 downto 0);
begin
  -- register
```

Simple Design Examples


```
process (clk, reset)
  begin
    if (reset='1') then
      r_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;

  -- next-state logic
  r_next <= (others=>'0') when r_reg=(TEN-1) else
    r_reg + 1;

  -- output logic
  q <= std_logic_vector(r_reg);
end two_seg_arch;
```

Simple Design Examples

RTL schematic

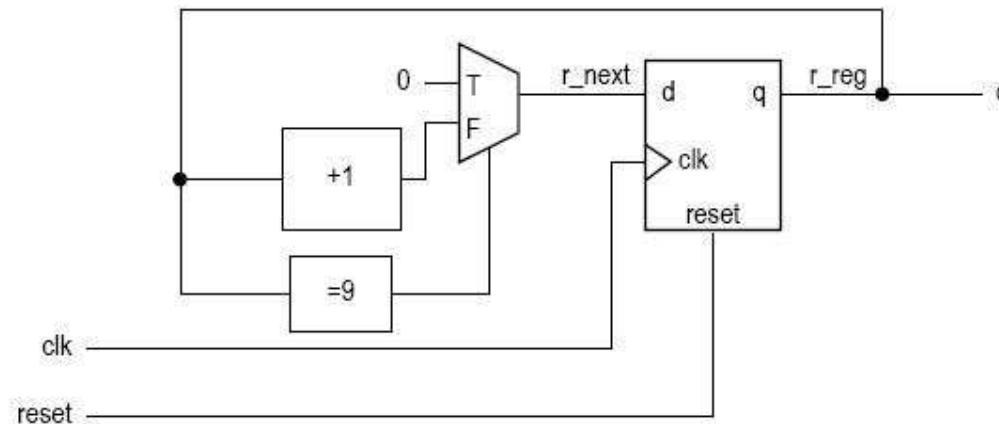

Programmable *mod-m* Counter

- Can be modified to use a constant m between "0010" and "1111"

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
use ieee.numeric_std.all;
```

```
entity prog_counter is
```

```
  port (
```

```
    clk, reset: in std_logic;
```

```
    m: in std_logic_vector(3 downto 0);
```

Simple Design Examples

```
        q: out std_logic_vector(3 downto 0)
    );
end prog_counter;

architecture two_seg_clear_arch of prog_counter is
    signal r_reg: unsigned(3 downto 0);
    signal r_next: unsigned(3 downto 0);
    begin

    -- register
    process(clk, reset)
        begin
            if (reset='1') then
                r_reg <= (others=>'0');
            elsif (clk'event and clk='1') then
                r_reg <= r_next;
            end if;
        end process;
```

Simple Design Examples

```

-- next-state logic
r_next <= (others=>'0') when
            r_reg=(unsigned(m)-1) else
            r_reg + 1;

-- output logic
q <= std_logic_vector(r_reg);
end two_seg_clear_arch;

```

Contains a *incrementor*, a *decrementor* and *comparator* but note that the statement

```
r_reg = (unsigned(m) - 1);
```

can be written as

```
(r_reg + 1) = unsigned(m)
```

```

architecture two_seg_effi_arch of prog_counter is
    signal r_reg: unsigned(3 downto 0);
    signal r_next, r_inc: unsigned(3 downto 0);
begin

```

Simple Design Examples


```
-- register
process (clk, reset)
  begin
    if (reset='1') then
      r_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;

-- next-state logic
r_inc <= r_reg + 1;
r_next <= (others=>'0') when r_inc=unsigned(m) else
  r_inc;


-- output logic
q <= std_logic_vector(r_reg);
end two_seg_effi_arch;
```

Simple Design Examples

RTL schematics

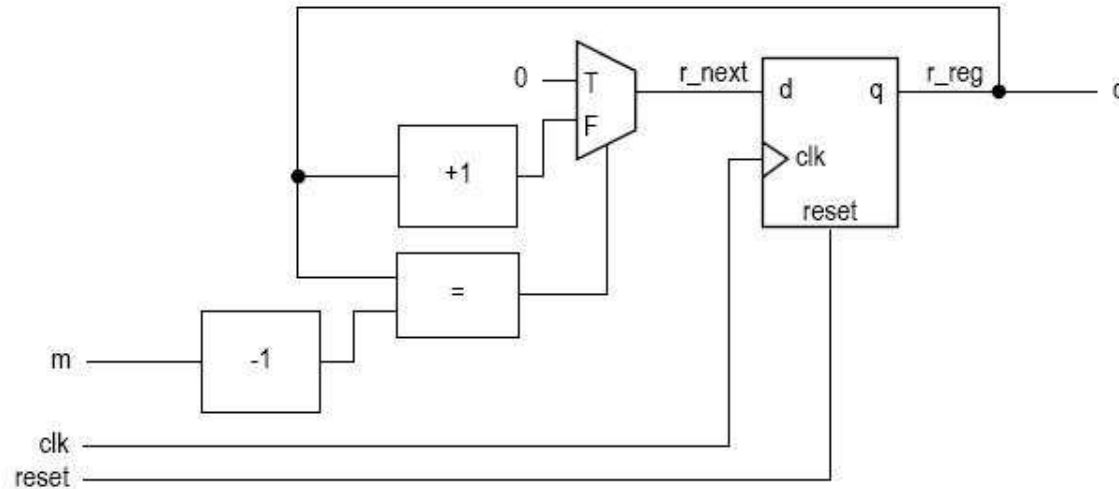

(a) Block diagram of initial design

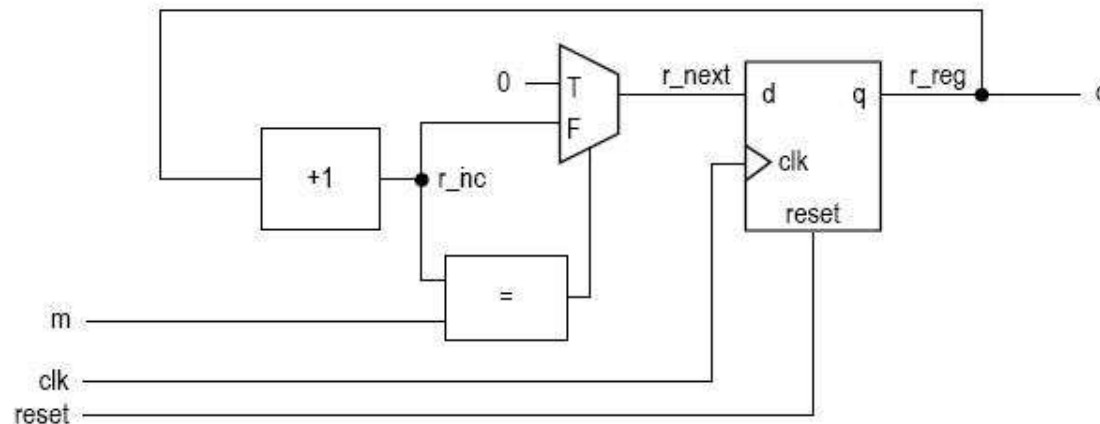

(b) Block diagram of more efficient design

Timing Analysis


Combinational circuit:

Characterized by propagation delay

Sequential circuit:

Has to satisfy setup/hold time constraint and is characterized by *maximal clock rate* (e.g., 200 MHz counter, 2.4 GHz Pentium II)

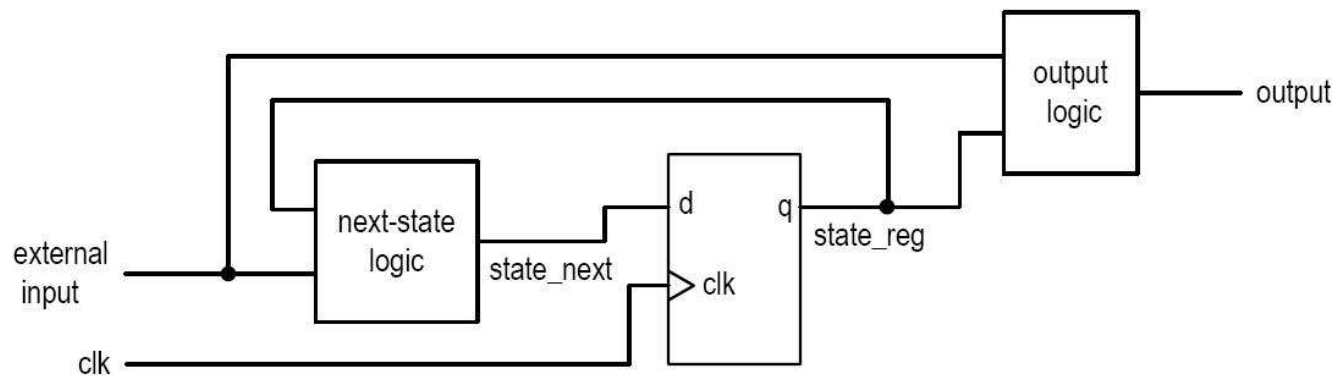Setup time and *clock-to-q* delay of register and the propagation delay of next-state logic are embedded in clock rate



state_next signal must satisfy the timing constraints for the FFs

Timing Analysis

$state_next$ delay is effected by three sources

- $state_reg$ output -- part of the same loop and sync'ed by same clock (timing below)
- **synchronized** external input from a subsystem that uses the same clock
- **unsynchronized** external input -- must use *synchronization* circuit

For the first 2 items, we can adjust clock rate to prevent timing violations

From the timing diagram below (which shows the timing behavior of the closed loop system), at time t_0 , the clock changes from '0' to '1'


We assume $state_next$ does not change within the setup and hold periods

After the clock-to-q delay (T_{cq}), the register's output, $state_reg$, stabilizes at time t_1 (which is $t_0 + T_{cq}$)

Since $state_reg$ is input to the next-state logic, the output of next-state logic changes at times $T_{next(min)}$ and $T_{next(max)}$ which represent fastest and slowest paths through it

Therefore, $state_next$ changes at t_2 ($t_1 + T_{next(min)}$) and stabilizes at t_3 ($t_1 + T_{next(max)}$)

Timing Analysis

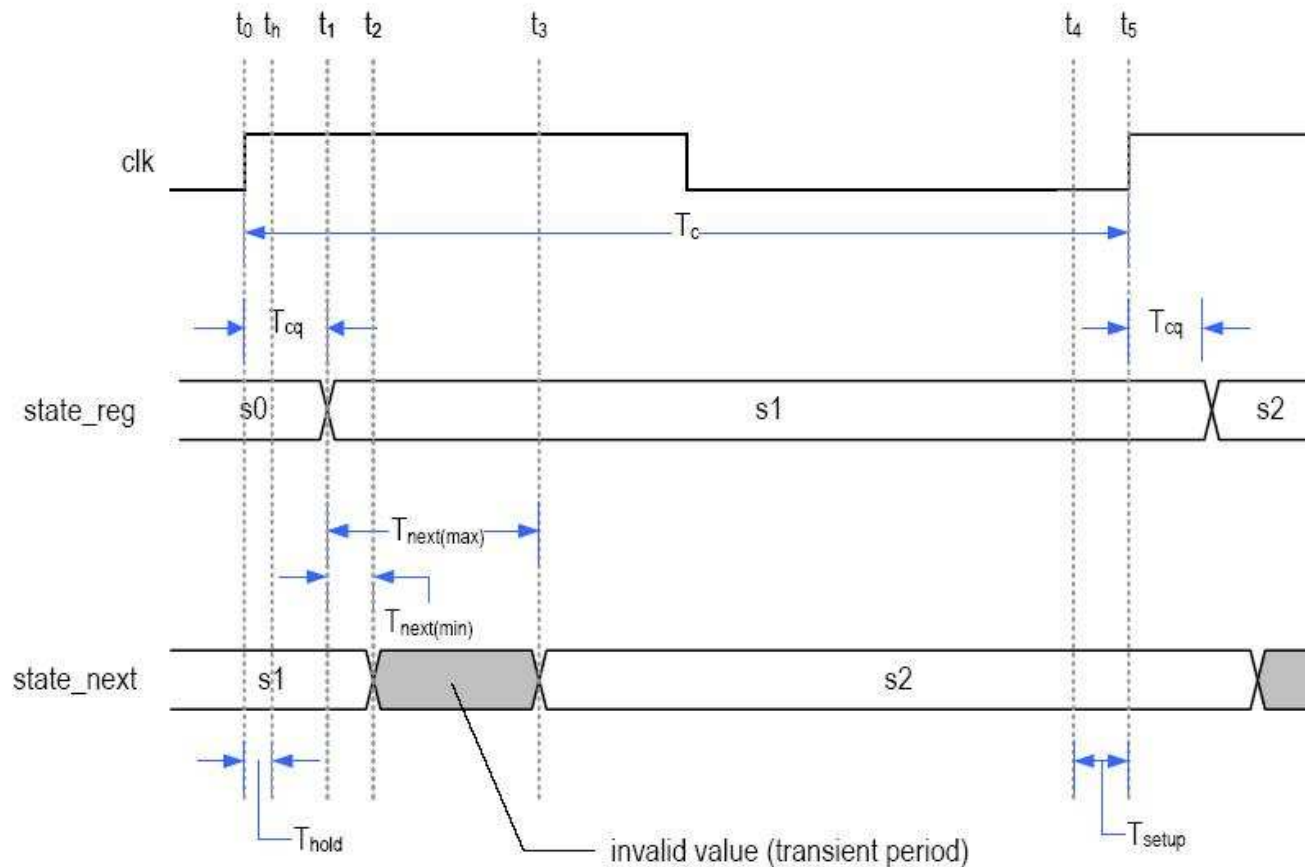

At time t_5 , a new rising clock edge arrives and the current clock cycle ends
 $next_state$ is sampled at t_5 which is $t_0 + T_c$ -- the clock period

Next consider the setup time constraint

Timing Analysis

The setup time constraint indicates that *state_next* MUST be stabilized at least T_{setup} before the next sampling edge at t_5 -- given by t_4 in the timing diagram

$$t_3 < t_4$$

From timing diagram

$$t_3 = t_0 + T_{cq} + T_{next(max)}$$

$$t_4 = t_5 - T_{setup} = t_0 + T_c - T_{setup}$$

The inequality above can be re-written as

$$t_0 + T_{cq} + T_{next(max)} < t_0 + T_c - T_{setup}$$

which simplifies to

$$T_{cq} + T_{next(max)} + T_{setup} < T_c$$



Therefore, minimal **clock period** is

$$T_{c(min)} = T_{cq} + T_{next(max)} + T_{setup}$$

Timing Analysis

For a given technology, T_{cq} and T_{setup} of a D FF are obtained a data sheet

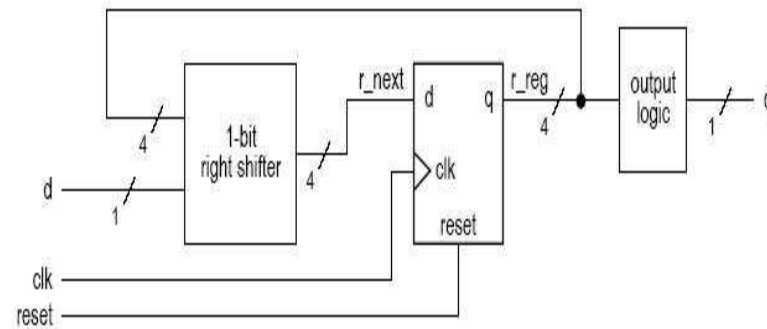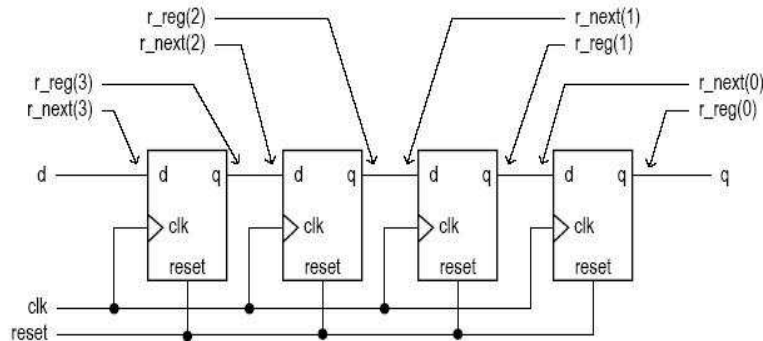Therefore, we can determine the minimum clock period (maximum clock rate) once the propagation delay of the next-state logic



Let $T_{cq} = 1 \text{ ns}$ and $T_{setup} = 0.5 \text{ ns}$


Since 1 bit shift logic only involves routing (no gates) -- assuming 0 delay associated with the wires, then max frequency is $1/1.5 \text{ ns} = 666.7 \text{ MHz}$

Text goes over other examples which incorporate combinational blocks where delay is > 0 .

Timing Analysis

Hold Time Violation

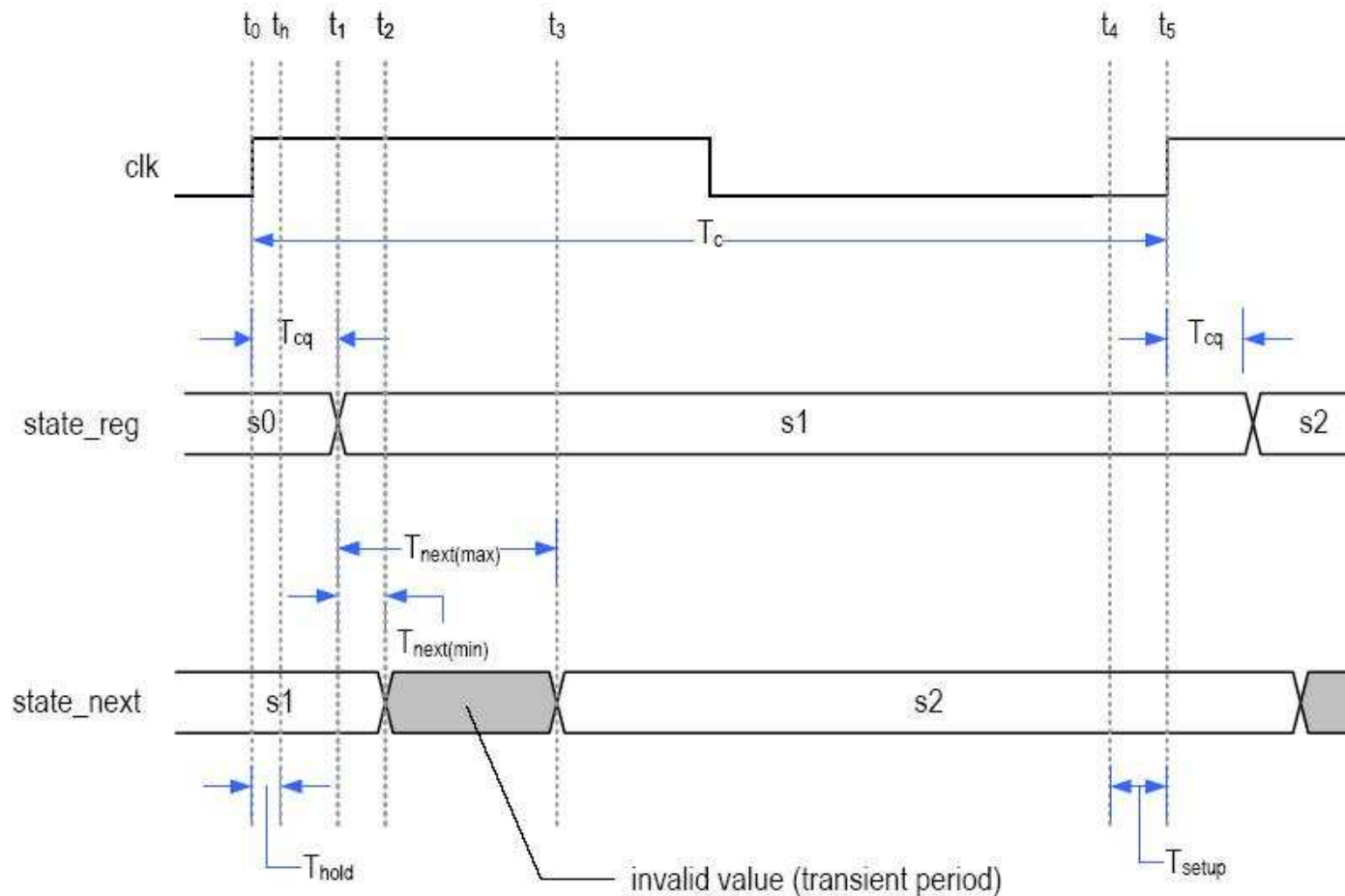Period of time that the input signal must be stabilized after the sampling edge



start_next must be stable between t_0 and t_h ($t_0 + T_{hold}$)

Timing Analysis

The earliest time that $state_next$ changes is t_2

$$t_h < t_2$$

And

$$t_2 = t_0 + T_{cq} + T_{next(min)}$$

$$t_h = t_0 + T_{hold}$$

Then

$$t_0 + T_{hold} < t_0 + T_{cq} + T_{next(min)}$$

Simplifying

$$T_{hold} < T_{cq} + T_{next(min)}$$

In cases in which the output of one FF drives the input to the next (no gate delays),

$T_{next(min)}$ can be close to 0 and

$$T_{hold} < T_{cq}$$


Manufacturers usually guarantee this relationship holds on these *intrinsic* parameters of the FF, but one concern is related to clock skew to be discussed

Timing Analysis

We need to also consider the timing characteristics of **external inputs and outputs** (in addition to the closed loop just discussed)

The outputs of a circuit can be divided into *Moore outputs* and *Mealy outputs*.

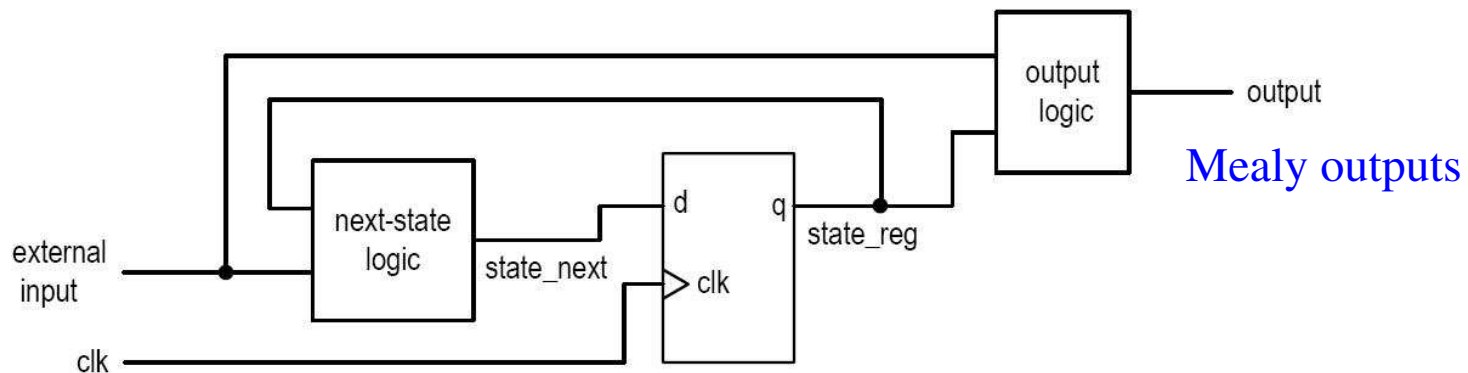For Moore outputs, the output signal is a function of *system state*, i.e., the state registers only, while Mealy outputs depend on both the state and external inputs



The two types can co-exist in the same circuit

The main timing parameter for both types is T_{co} -- the time required to obtain a valid output signal after the *rising* edge of the clock

Timing Analysis

T_{co} is the sum of the clock-to-q delay of the FF and propagation delay of the output logic

$$T_{co} = T_{cq} + T_{output}$$

Note that for Mealy, the input can affect the output **directly**

Text covers timing issues related to external *synchronized* inputs

Alternative One-Segment Coding Style

Although it is possible to combine the memory elements with next-state and output logic into one segment, you should avoid this coding practice b/c it is error prone

Consider the **D FF with Sync Enable** covered earlier

```
architecture one_seg_arch of dff_en is  
  begin  
    process (clk, reset)  
      begin
```


Alternative One-Segment Coding Style


```

if (reset='1') then
    q <= '0';
elsif (clk'event and clk='1') then
    if (en='1') then
        q <= d;
    end if;
    end if;
end process;
end one_seg_arch;

```

reset	clk	en	q*
1	-	-	0
0	0	-	q
0	1	-	q
0	f	0	q
0	f	1	d

(a) Function table

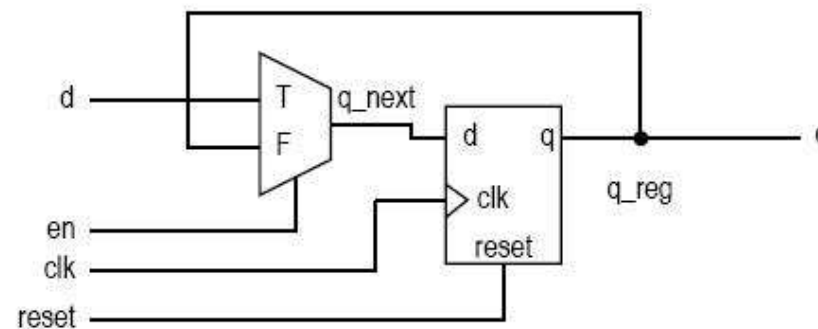

(b) Conceptual diagram

Alternative One-Segment Coding Style

The difference is the addition of the *if* ($en = '1'$) *then* statement added inside the *elsif* branch

We interpret this as "at the rising edge of *clk*, if *en* is '1', *q* gets the value of the *d* input"

The absence of the *else* implies that if *en* is **not** '1', the *q* keeps its previous value
This correctly describes the function of the *en* signal

Consider the **T FF** discussed earlier

```
architecture one_seg_arch of tff is
  signal q_reg: std_logic;
begin

  process(clk, reset)
    begin
      if (reset='1') then
        q_reg <= '0';
```

Alternative One-Segment Coding Style

```
    elsif (clk'event and clk='1') then
        if (t='1') then
            q_reg <= not q_reg;
        end if;
    end if;
end process;
q <= q_reg;
end one_seg_arch;
```


Here, the internal signal *q_reg* represents **both** the content and the output of a FF

The following statement appears strange at first glance

```
q_reg <= not q_reg;
```

The interpretation is that the *q_reg* on the right side represents the current value of the FF and (**not** *q_reg*) represents the new value

On the rising edge of *clk*, the new value is stored into the FF named *q_reg*

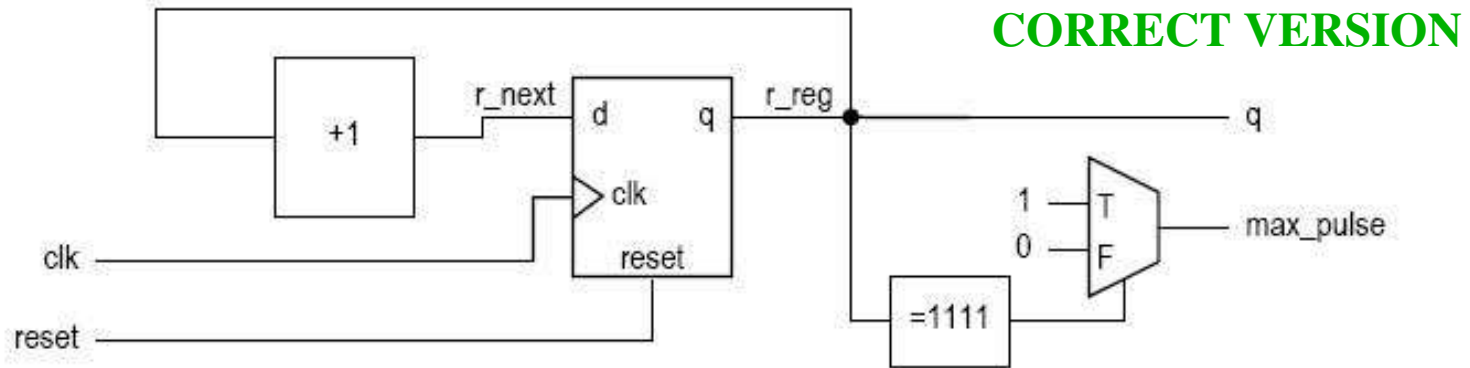Alternative One-Segment Coding StyleConsider the **Free-Running Binary Counter**The following code is an **INCORRECT** one-segment version

```

architecture not_work_one_seg_glitch_arch
    of binary_counter4_pulse is
    signal r_reg: unsigned(3 downto 0);
    begin

    process(clk, reset)
    begin
    if (reset='1') then
        r_reg <= (others=>'0');

```

Alternative One-Segment Coding Style

```
elsif (clk'event and clk='1') then
    r_reg <= r_reg + 1;
    if (r_reg = "1111") then
        max_pulse <= '1';
    else
        max_pulse <= '0';
    end if;
end if;
end process;
q <= std_logic_vector(r_reg);
end not_work_one_seg_glitch_arch;
```


This does NOT work as expected because the following is INSIDE the *if (clk'event...*

```
if (r_reg = "1111") then
    max_pulse <= '1';
else
    max_pulse <= '0';
end if;
```

Alternative One-Segment Coding Style

This creates a 1-bit register for *max_pulse* -- which works as a buffer and creates a **1 clock signal delay** of the output pulse

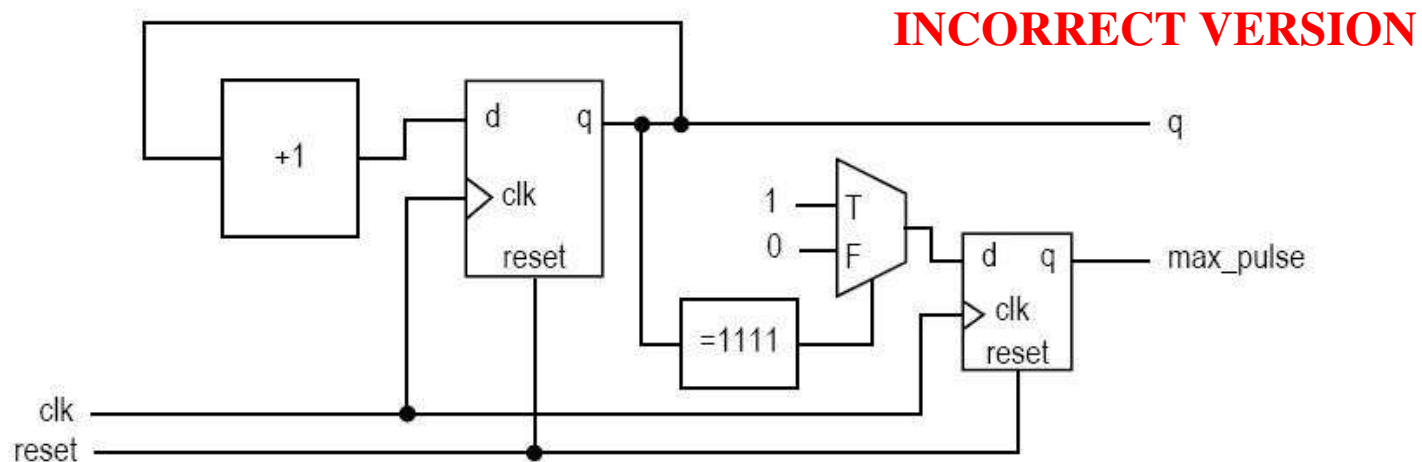max_pulse will be asserted with *r_reg* = "0000"



To correct, you must move the output logic outside the process

```
architecture work_one_seg_glitch_arch
```

```
    of binary_counter4_pulse is
```

```
    signal r_reg: unsigned(3 downto 0);
```

```
begin
```

Alternative One-Segment Coding Style

```
process (clk, reset)
  begin
    if (reset='1') then
      r_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      r_reg <= r_reg + 1;
    end if;
  end process;
  q <= std_logic_vector(r_reg);
  max_pulse <= '1' when r_reg = "1111" else
    '0';
end work_one_seg_glitch_arch;
```

One more example -- consider the **Programmable Counter**

```
architecture not_work_one_arch of prog_counter is
  signal r_reg: unsigned(3 downto 0);
begin
```

Alternative One-Segment Coding Style

```
process (clk, reset)
  begin
    if (reset='1') then
      r_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      r_reg <= r_reg + 1;
      if (r_reg = unsigned(m)) then
        r_reg<= (others=>'0');
      end if;
    end if;
  end process;
  q <= std_logic_vector(r_reg);
end not_work_one_arch;
```

Does NOT work as expected because a signal is NOT updated until **the end of the process**.

Alternative One-Segment Coding Style

Thus r_reg is updated to r_reg+1 at the end, and not when *if* ($r_reg = unsigned(m)$) *then* is performed.

The comparison uses the OLD VALUE of r_reg

Thus, you actually built a $mod-(m+1)$ counter instead

To fix, move incrementing operation **outside** the process

```
architecture work_one_arch of prog_counter is
  signal r_reg: unsigned(3 downto 0);
  signal r_inc: unsigned(3 downto 0);
begin

  process (clk, reset)
    begin
      if (reset='1') then
        r_reg <= (others=>'0');
      elsif (clk'event and clk='1') then
```

Alternative One-Segment Coding Style

```
        if (r_inc = unsigned(m)) then
            r_reg <= (others=>'0');
        else
            r_reg <= r_inc;
        end if;
    end if;
end process;
r_inc <= r_reg + 1;
q <= std_logic_vector(r_reg);
end work_one_arch;
```

Using Variables in Sequential Circuit Descriptions

A variable can also be assigned under the *clk'event* **and** *clk = '1'* condition, but whether a FF is created or not depends on how it is used

If a variable is assigned a value **before** it is used, it will get a value on each invocation of the process and therefore, there is not need to *remember* its previous value

Using Variables in Sequential Circuit Descriptions

If, on the other hand, it is **read before being assigned to**, it needs to use the value stored from the previous process execution, and therefore needs to be stored

Using a variable to infer memory is error prone -- you should use signals instead

The proper use of variables is to use them to store intermediate results (the first scenario above)

Consider these three uses

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity variable_ff_demo is  
  port (  
    a,b,clk: in std_logic;  
    q1,q2,q3: out std_logic  
  );  
end variable_ff_demo;
```

Using Variables in Sequential Circuit Descriptions

```
architecture arch of variable_ff_demo is
  signal tmp_sig1: std_logic;
begin

  -- attempt 1
  process(clk)
    begin
      if (clk'event and clk='1') then
        tmp_sig1 <= a and b;
        q1 <= tmp_sig1;
      end if;
    end process;

  -- attempt 2
  process(clk)
    variable tmp_var2: std_logic;
    begin
```

Using Variables in Sequential Circuit Descriptions


```
    if (clk'event and clk='1') then
        tmp_var2 := a and b;
        q2 <= tmp_var2;
    end if;
end process;

-- attempt 3
process(clk)
    variable tmp_var3: std_logic;
begin
    if (clk'event and clk='1') then
        q3 <= tmp_var3;
        tmp_var3 := a and b;
    end if;
end process;
end arch;
```

Using Variables in Sequential Circuit Descriptions

The first attempt uses **signals** with the assignment occurring before the use

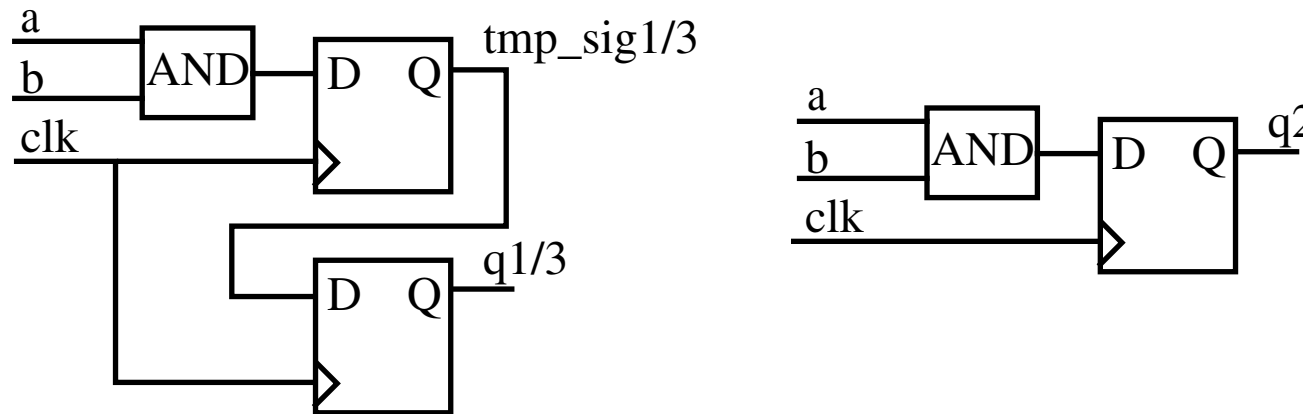However, this DOES NOT MATTER for signals -- a register is INFERRED because the assignments occur within the *if stmt*



Interpretation: on the rising edge of clk

- The value of **a and b** will be sampled and stored into a FF named *tmp_sig1*
- The **old** value (**not** the current value) of **a AND b** from the *tmp_sig1* signal will be stored into FF named *q1*

Using Variables in Sequential Circuit Descriptions

Attempt 2 is the proper way of using a variable -- yields the circuit on the right

Attempt 3 references the variable before using it, and generates the circuit on the left

We can use a variable to fix the problem we had with the one-segment version of the **mod-m** counter

```
architecture variable_arch of prog_counter is
  signal r_reg: unsigned(3 downto 0);
begin

  process (clk, reset)
    begin
      if (reset = '1') then
        r_reg <= (others => '0');
      elsif (clk'event and clk' = '1') then
        q_tmp := r_reg + 1;
        if (q_tmp = unsigned(m)) then
          r_reg <= (others => '0');
```

Using Variables in Sequential Circuit Descriptions

```
        else
            r_reg <= q_tmp;
        end if;
    end if;
end process;
q <= std_logic_vector(r_reg);
end variable_arch;
```