 


**Datapath Operators: Comparison***Magnitude Comparators:*



May be built from an adder, complementer (XOR gates) and a zero detect unit.



Think about the modifications necessary to make it a signed comparator  
(Hint: A couple of XOR gates).

  **Datapath Operators: Binary Counters**

Asynchronous: Based on the Toggle register.




"Ripple Carry" Binary counter

Not a good choice for performance and testability (with no reset).



**Datapath Operators: Binary Counters**

Synchronous counter.

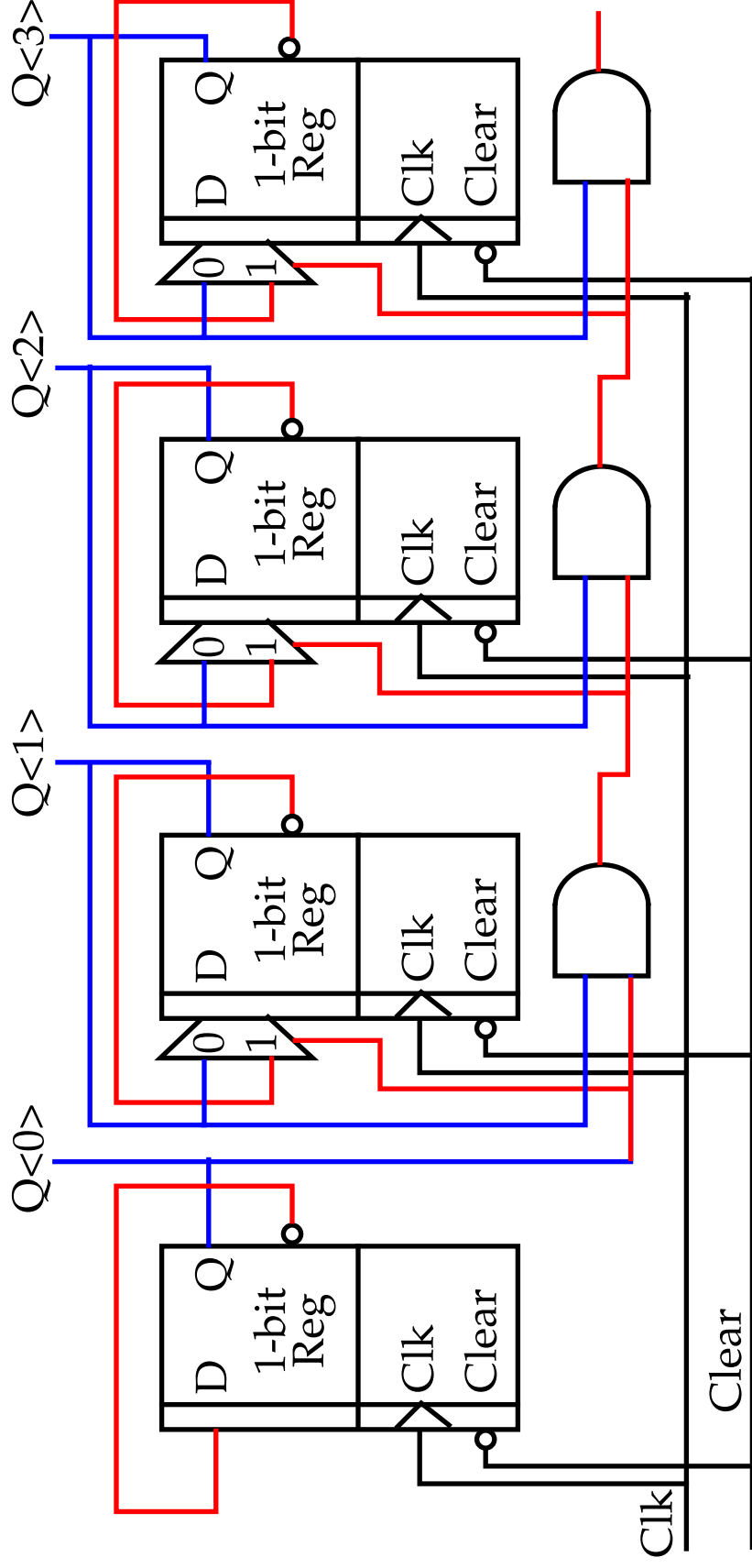

Replace AND gate with an adder for up/down counting capability.

Weste and Eshraghian also show a version that can be initialized.

**Datapath Operators: Multiplication**

Multiplication can be broken down into two steps:

- Computation of partial products.
- Accumulation of the shifted partial products.

$$\begin{array}{r}
 1100 \\
 \times 0101 \\
 \hline
 1100 \\
 0000 \\
 1100 \\
 0000 \\
 \hline
 0111100
 \end{array}$$

Binary multiplication equivalent to  
AND operation

Multipliers may be classified by the format in which data words are accessed:

- Serial
- Serial/parallel
- Parallel

The parallel form computes the partial products in parallel.

**Datapath Operators: Multiplication**  
 Parallel Unsigned Multiplication:

Multiplying 2 unsigned binary integers results in:

$$X = \sum_{i=0}^{m-1} X_i \cdot 2^i$$

$$Y = \sum_{j=0}^{n-1} Y_j \cdot 2^j$$

$$P = X \times Y = \sum_{i=0}^{m-1} X_i \cdot 2^i \sum_{j=0}^{n-1} Y_j \cdot 2^j = \sum_{k=0}^{m+n-1} P_k \cdot 2^k$$

|       |       |       |       |              |
|-------|-------|-------|-------|--------------|
| $X_3$ | $X_2$ | $X_1$ | $X_0$ | Multiplicand |
| $Y_3$ | $Y_2$ | $Y_1$ | $Y_0$ | Multiplier   |

|          |          |          |          |       |
|----------|----------|----------|----------|-------|
| $X_3Y_0$ | $X_2Y_0$ | $X_1Y_0$ | $X_0Y_0$ |       |
| $X_3Y_1$ | $X_2Y_1$ | $X_1Y_1$ | $X_0Y_1$ |       |
| $X_3Y_2$ | $X_2Y_2$ | $X_1Y_2$ | $X_0Y_2$ |       |
| $X_3Y_3$ | $X_2Y_3$ | $X_1Y_3$ | $X_0Y_3$ |       |
| $P_7$    | $P_6$    | $P_5$    | $P_4$    | $P_3$ |
|          | $P_2$    | $P_1$    | $P_0$    |       |

There are  $m \cdot n$  summands produced by a set of  $m \cdot n$  AND gates in parallel.




**Datapath Operators: Multiplication**
 
## Parallel Multiplication:

Multiplication is carried out using a bitwise AND of the operands,  $X_i$  and  $Y_i$ .


Most of the work (and delay) is in summing the partial products.



A  $N \times N$  multiplier requires:  
 $N(N-2)$  full adders  
 $N$  half adders  
 $N^2$  AND gates

**Datapath Operators: Multiplication**

Array multiplier:

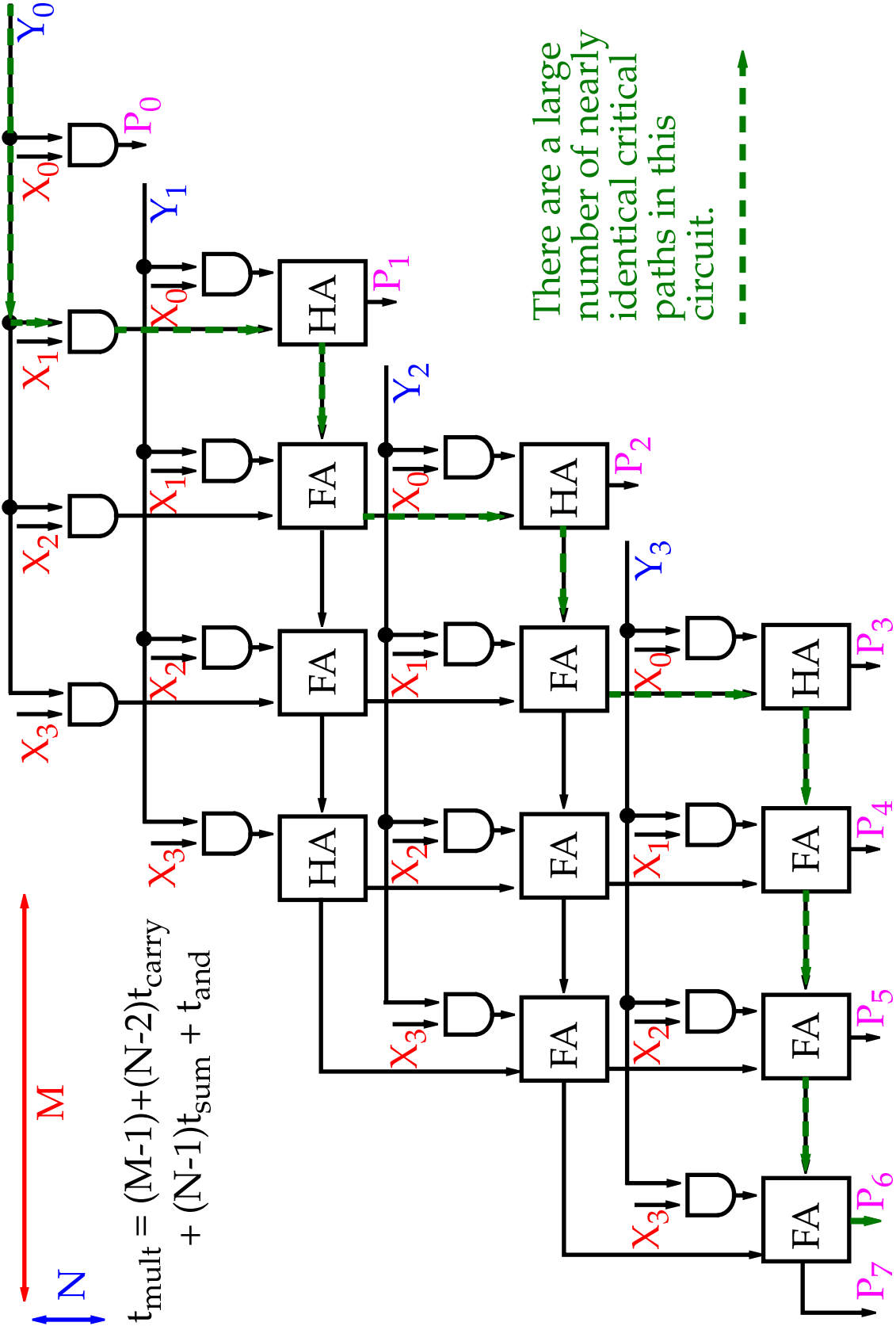

$$t_{\text{mult}} = (M-1) + (N-2)t_{\text{carry}} + (N-1)t_{\text{sum}} + t_{\text{and}}$$



**Datapath Operators: Multiplication**

From the delay expression and the fact that all critical paths have the same length, minimizing  $t_{\text{mult}}$  requires minimizing both  $t_{\text{carry}}$  and  $t_{\text{sum}}$ .

This is in contrast with the adder where minimizing  $t_{\text{carry}}$  was key.

The transmission gate adder is a good choice here.

**Parallel Signed Multiplication:**

**Baugh-Wooley algorithm:** Only 3 additional adders required over the unsigned version.

$$A = -a_{m-1}2^{m-1} + \sum_{i=0}^{m-2} a_i 2^i$$

$$B = -b_{m-1}2^{m-1} + \sum_{i=0}^{m-2} b_i 2^i$$


Let A and B represent signed integers.

Expanding shows that the last two rows of summands are all negative so the algorithm simply adds in their negations.

$$\begin{aligned} P &= \left( -a_{m-1}2^{m-1} + \sum_{i=0}^{m-2} a_i 2^i \right) \left( -b_{n-1}2^{n-1} + \sum_{i=0}^{n-2} b_i 2^i \right) \\ &= a_{m-1}b_{n-1}2^{m+n-2} + \sum_{i=0}^{m-2} \sum_{j=0}^{m-2n-2} a_i b_j 2^i + j - \sum_{i=0}^{m-2} a_{m-1} b_i 2^{m-1+i} \end{aligned}$$



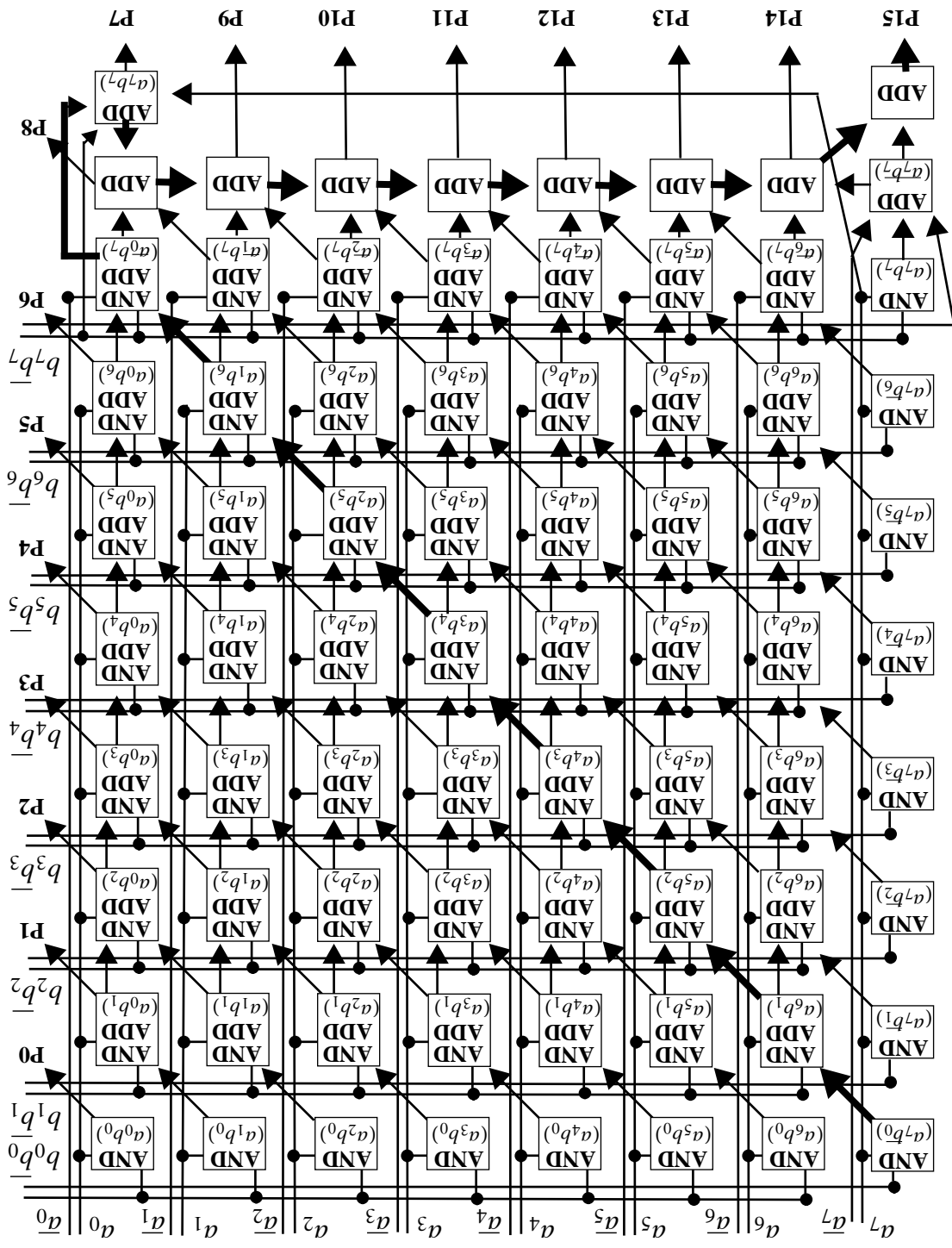
### Datapath Operators: Multiplication Parallel Signed Multiplication:



**Datapath Operators: Multiplication**

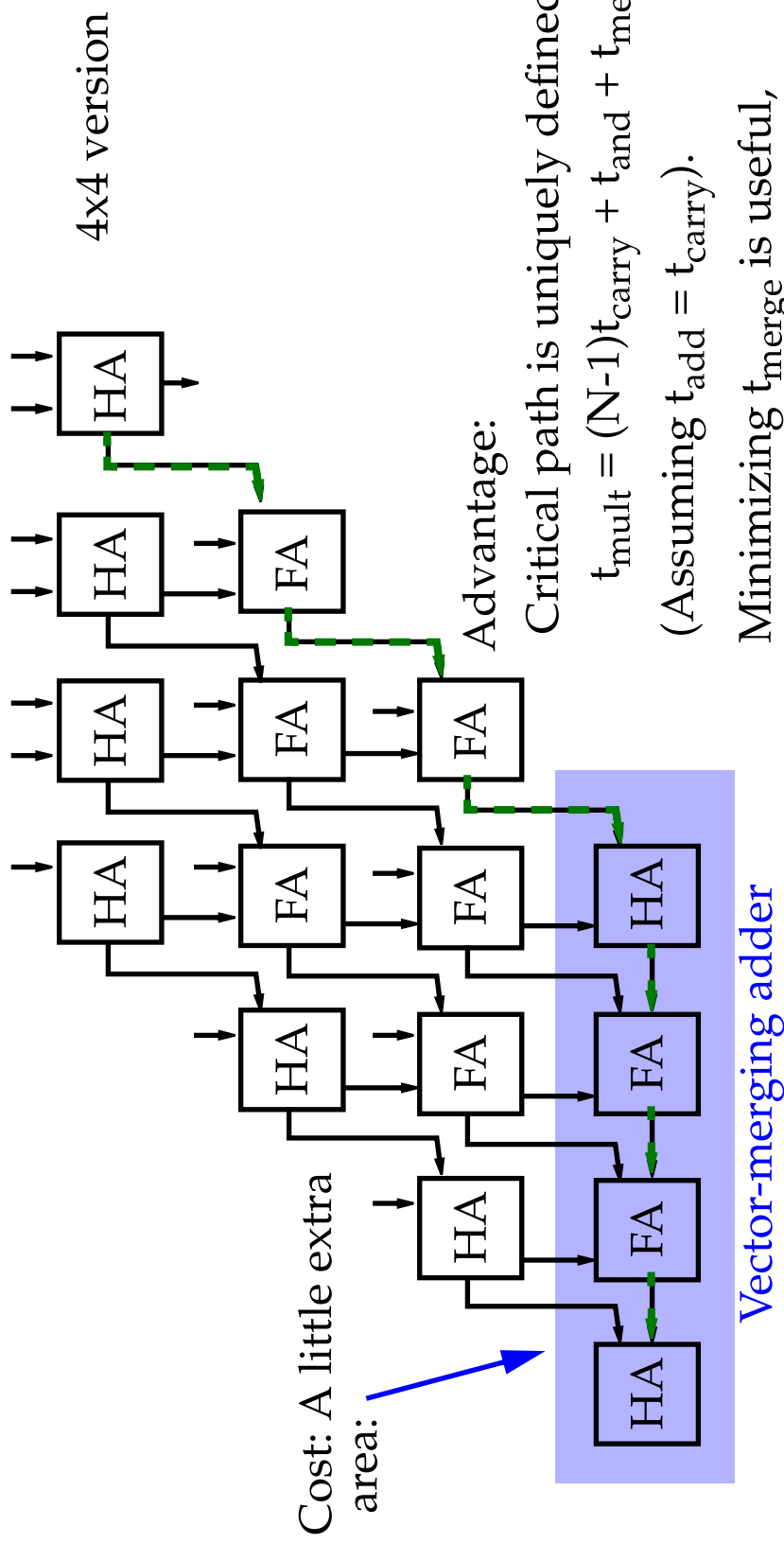**Carry-Save Multiplier:**

Carry bits can be passed diagonally downwards instead of to the left.




Here the carry bits are not immediately added but rather “saved” for the next adder stage.



**Datapath Operators: Multiplication**

Serial Unsigned Multiplication:

If area is a concern.

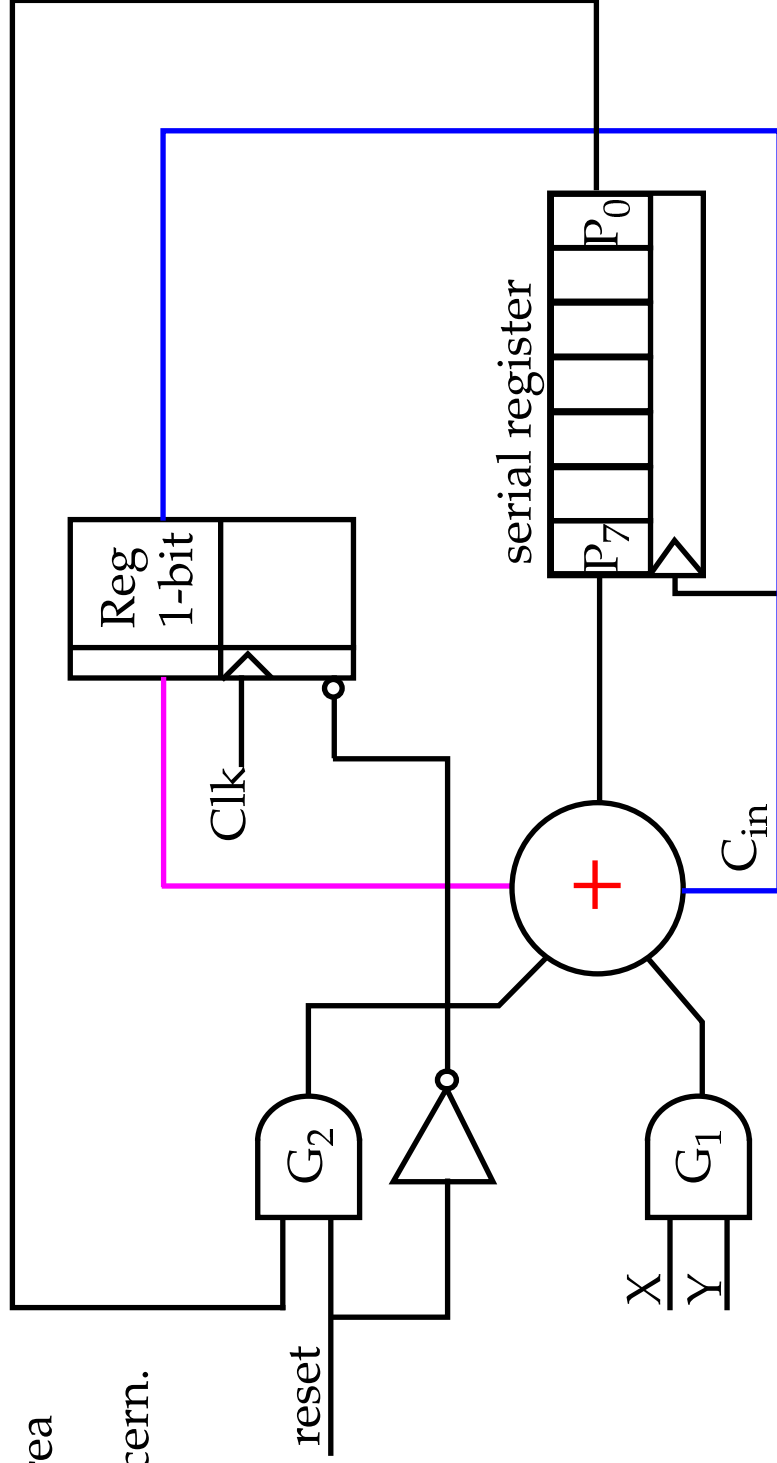

$X_i$  and  $Y_i$  delivered serially to the inputs of  $G_1$  at different rates. Computes the summands row-wise from right to left.

Disadv: Quadratic delay:  $t_{mult} = M \times N \times t_{carry}$

Serial/Parallel Unsigned Multiplier shown in Weste and Eshraghian.



**Datapath Operators: Multiplication**

## Booth Encoding:

A special encoding of the multiplier word reduces the number of required addition stages and speeds up multiplication substantially.

Radix-4 scheme:

$$Y = \sum_{j=0}^{(N-1)/2} Y_j 4^j \text{ with } (Y_j \in \{-2, -1, 0, 1, 2\})$$

The number of partial products (and additions) is halved, resulting in area and speed advantage.

The disadvantage is a somewhat more involved multiplier cell.




AND operation replaced with inversion and shift logic.

Virtually every multiplier in use employs the Booth scheme.

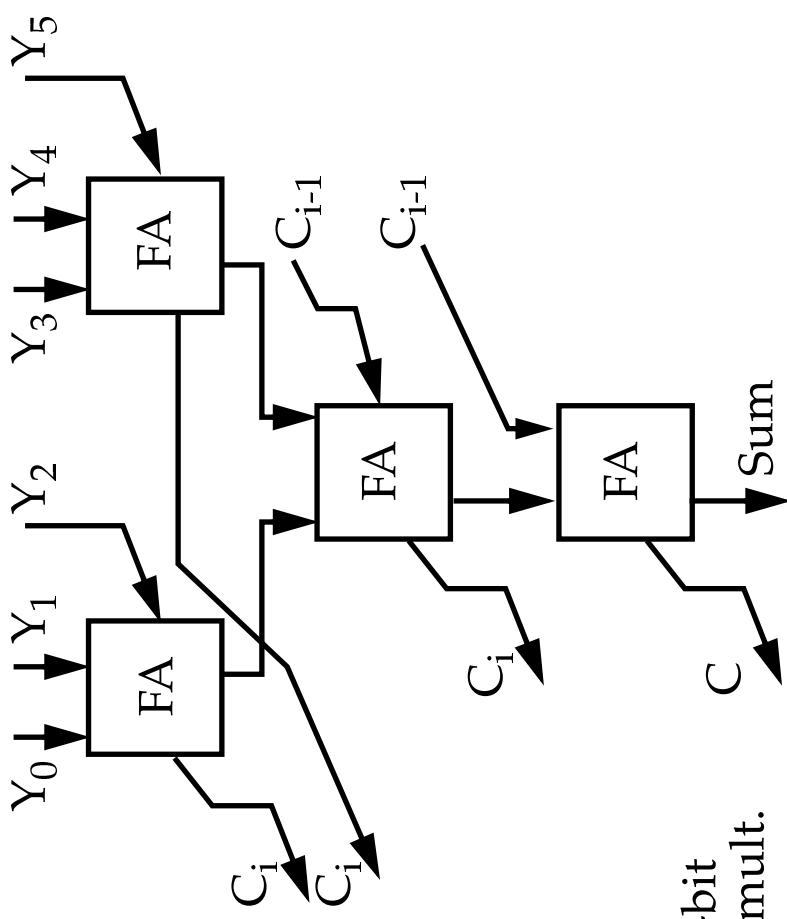  **Datapath Operators: Multiplication**

Wallace Multiplier:

Trees can be used to replace the linear partial-sum adders:



Slice of a 6-bit carry-save mult.

# of ripple stages is  $N-2$


Adv:  $O(\log_2 N)$  mult time.

Disadv: Very irregular -- difficult to layout.




**Datapath Operators: Shifters**

Right/Left 1-bit shifter:

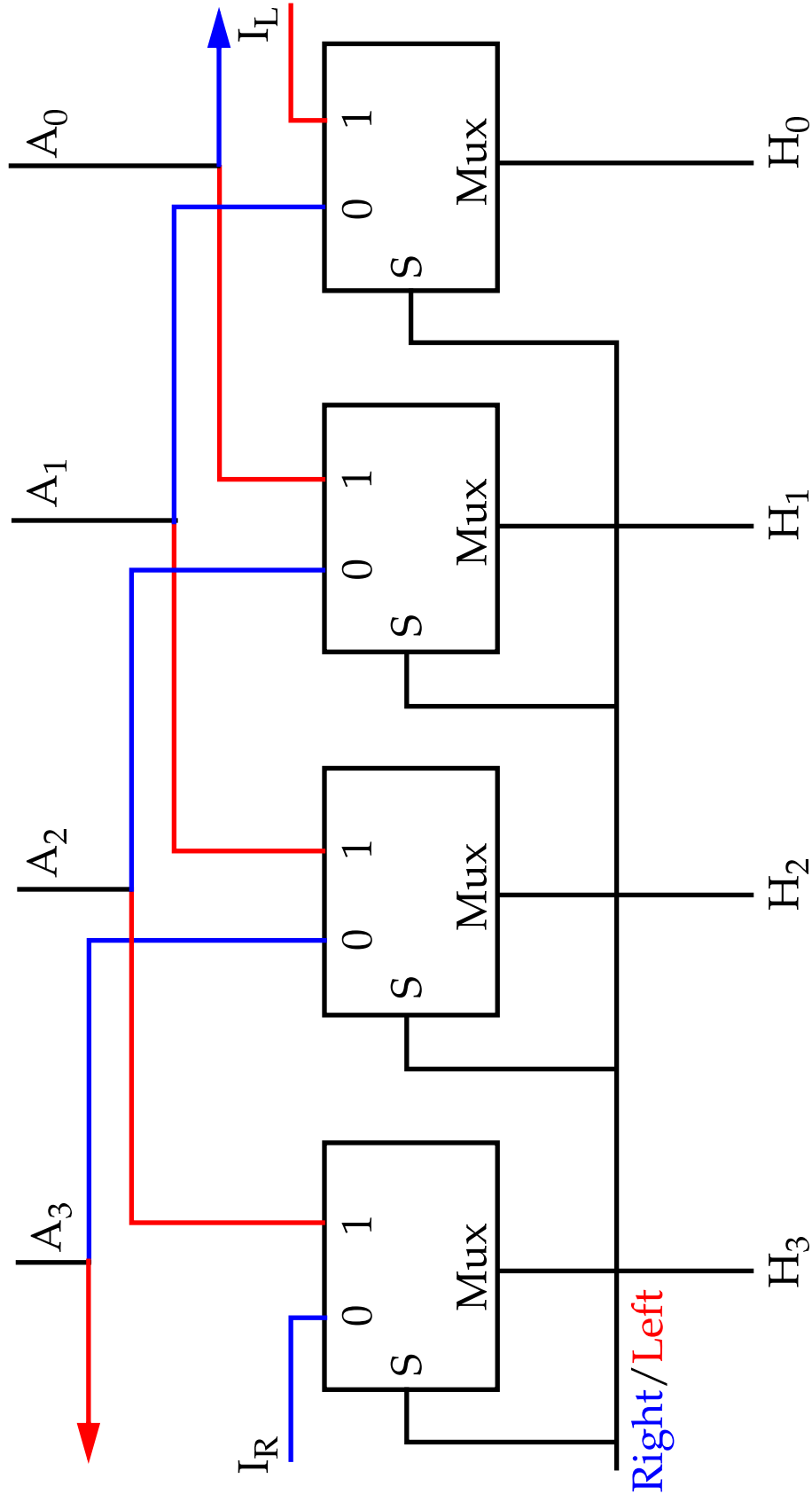

**Datapath Operators: Shifters**

Barrel shifter:

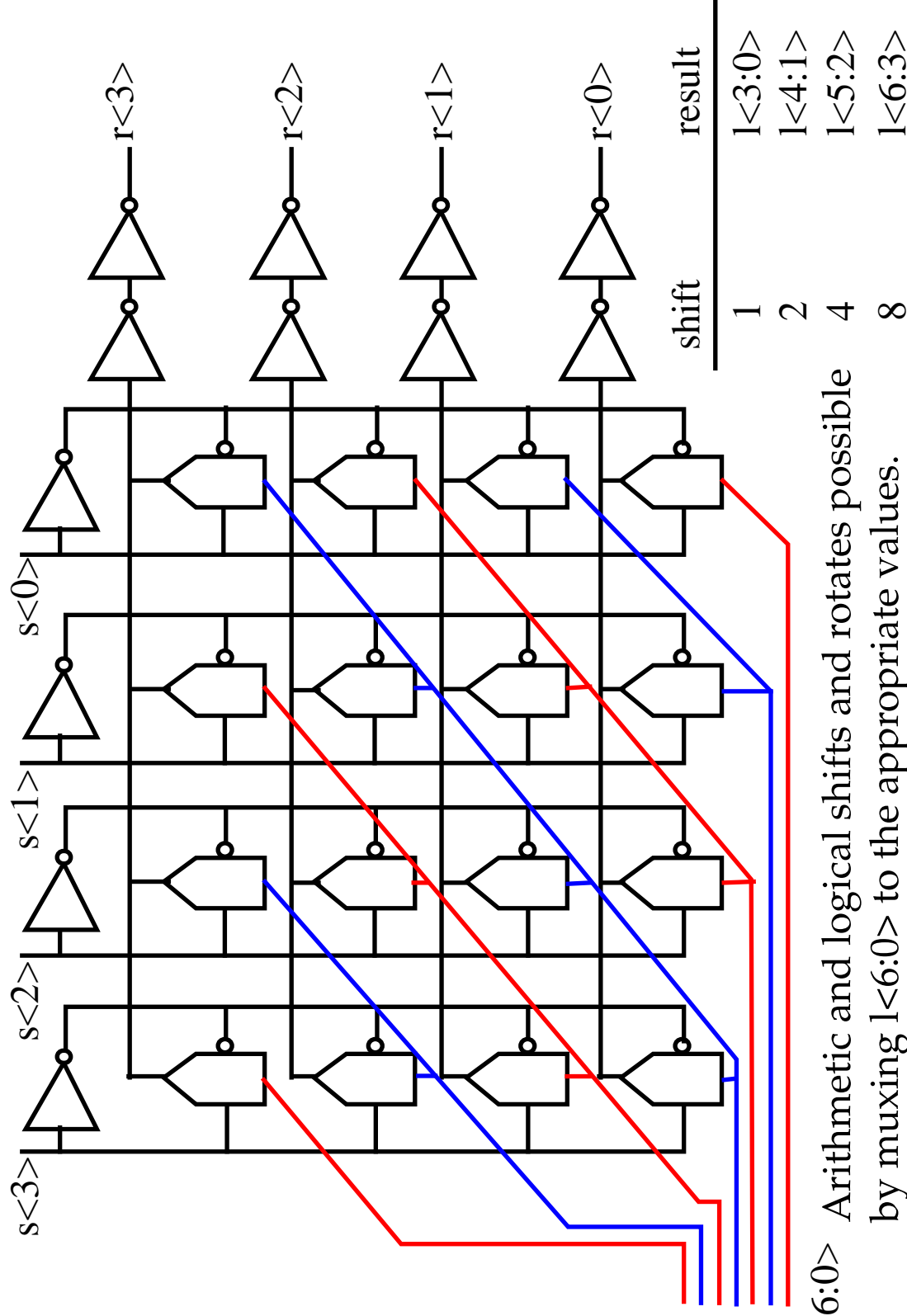

$l\langle 6:0 \rangle$  Arithmetic and logical shifts and rotates possible by muxing  $l\langle 6:0 \rangle$  to the appropriate values.

