


## Smaller Static Flip-Flops

Positive feedback is not the only means to implement a memory function.

A **capacitor** can act as a memory element as well.

In this case, a *periodic refresh* is required (in the millisecond range) due to leakage (hence the word **dynamic**).

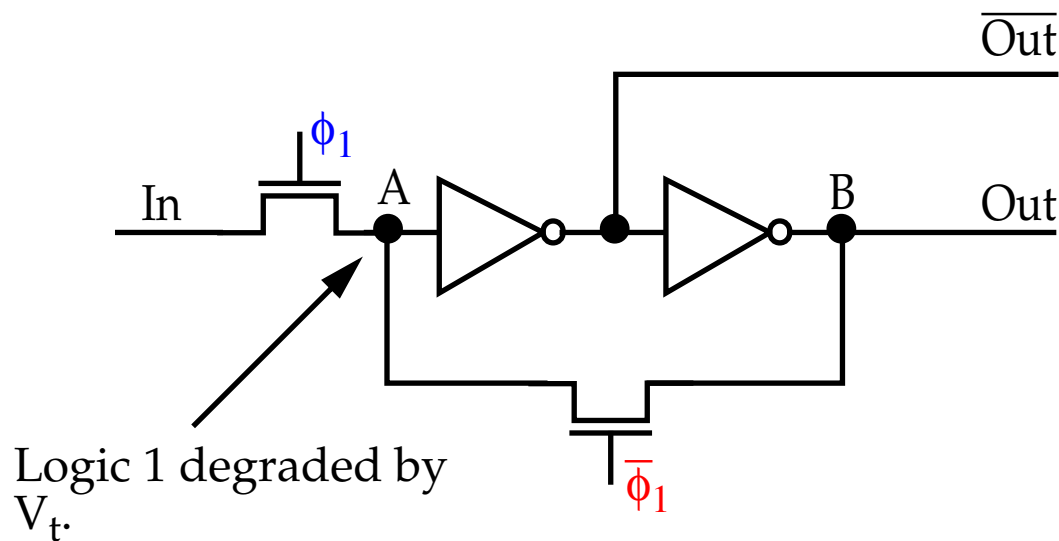Consider the following "cheaper" (1/2 transmission gate) *positive level-sensitive* static latch as a step toward deriving a dynamic FF:




Static as long as  $\phi_1$  is kept low.

When  $\phi_1$  is high,  $In$  is sampled and stored on internal capacitors.
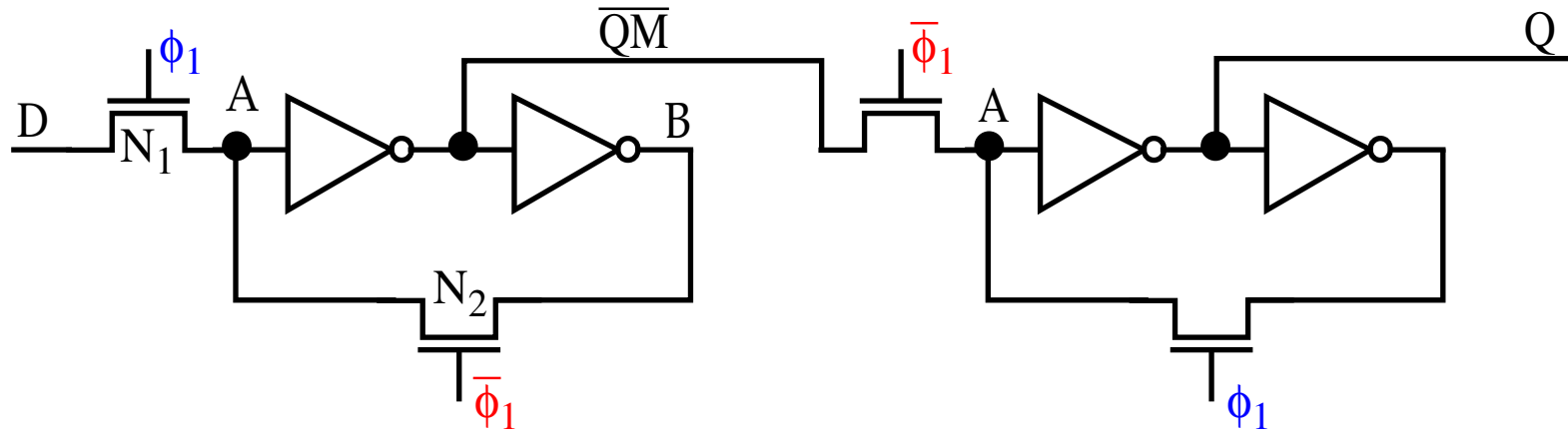
### Smaller Static Flip-Flops

A master-slave FF is created by cascading two of these latches and reversing the clocks.




The problem with this latch is that  $\phi_1$  and  $\bar{\phi}_1$  might overlap, which may cause two types of failures:


- Node A can become undefined as it is driven by both  $D$  and  $B$  when  $\phi_1$  and  $\bar{\phi}_1$  are both high.
- $D$  can propagate through both the master and slave if both  $\phi_1$  and  $\bar{\phi}_1$  are high simultaneously for a long enough period (race condition).
 
### Single Phase Clock Skew/Slew

Clock skew causes conflicts and transparency.



 Clock slew (slow rise and fall times) can also cause transparency:




Clock skew is a dominant problem in current high performance designs.



 
### Pseudo-Static Two-Phase Flip-Flops

The fix is to use two non-overlapping clocks  $\phi_1$  and  $\phi_2$ :



 A large  $t_{\phi-12}$  allows proper operation even in the presence of clock skew.




Note that node  $A$  floats (dynamic) during the time period  $t_{\phi-12}$  but is driven during  $t_{\phi-1}$  and  $t_{\phi-2}$  (static).

Hence, the name *pseudostatic*.

 
## CMOS Dynamic Two-Phase Flip-Flops

This version is simpler (6 trans) and is often used in pipelined datapaths for microprocessors and signal processors.



Degraded '1' values may increase static current if below  $V_{tp}$ .

 Disadv: **2 non-overlapping clocks** required (4 if transmission gates are used).




**p leakers** provide fully restored logic levels.

These implementations **MUST** be simulated at all process corners (under worst-case conditions).

**Two-Phase Clocking**

Clock skew/slew:

Nonoverlapping clocks:


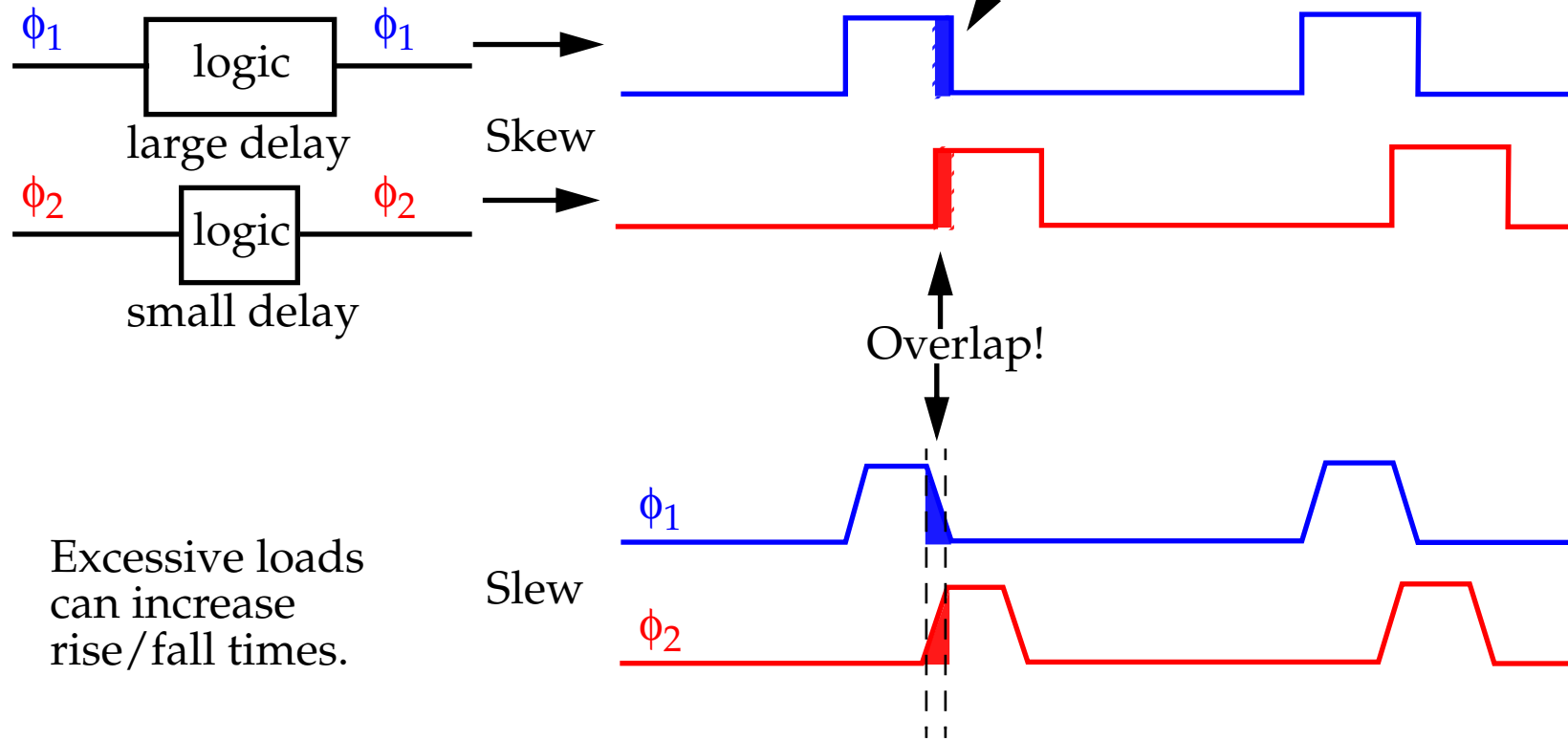


Excessive loads can increase rise/fall times.


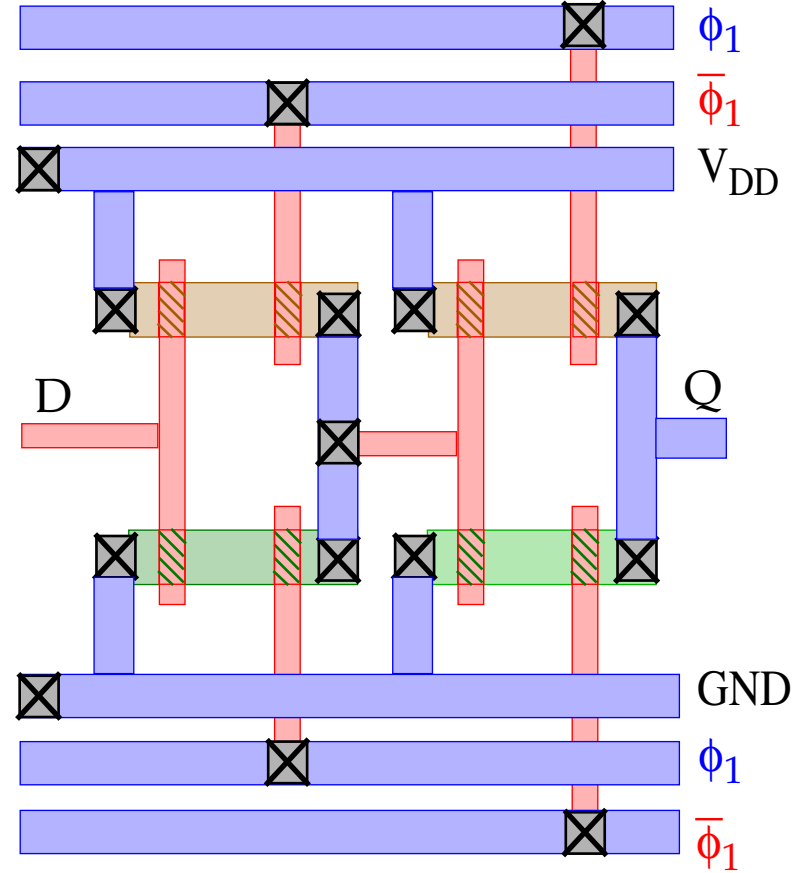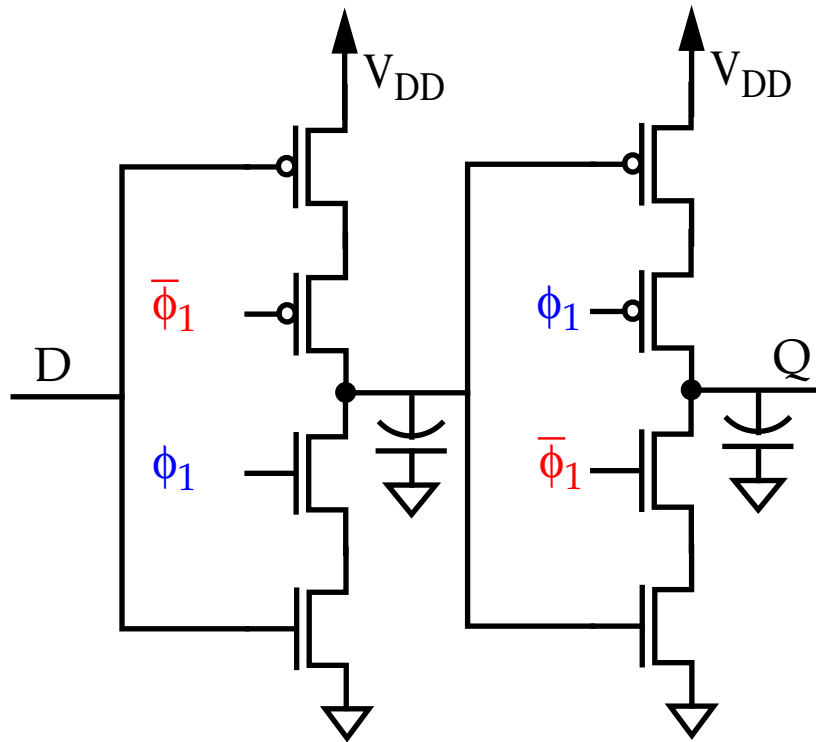
### C<sup>2</sup>MOS Register

C<sup>2</sup>MOS: A clever method which is *insensitive* to clock skew:




Note: Dual phase version is identical except  $\phi_2$  and  $\bar{\phi}_2$  are used to drive the n/p-trans in the right inverter.
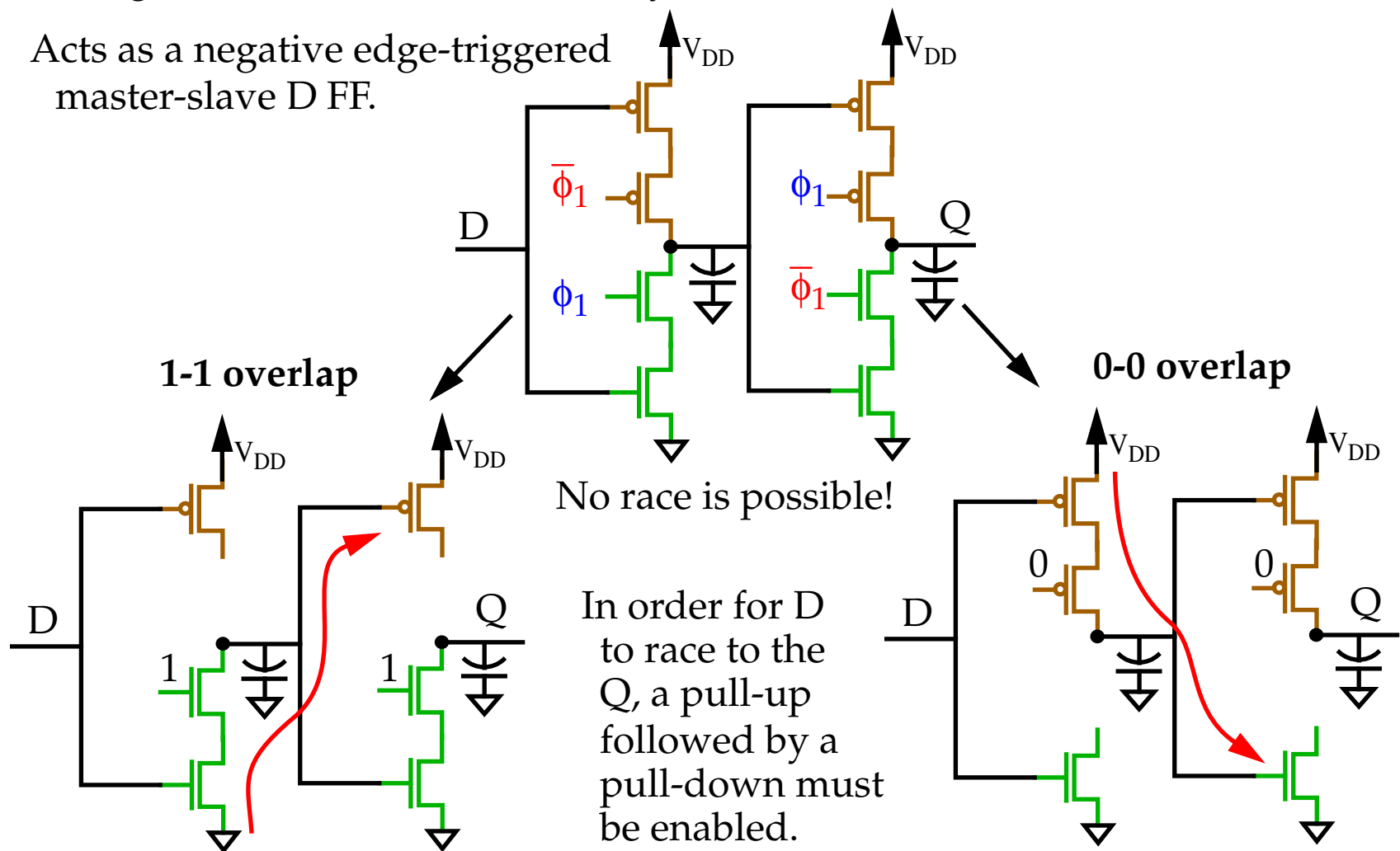
### C<sup>2</sup>MOS Register

C<sup>2</sup>MOS is *insensitive* to overlap as long as the rise and fall times of the clk edges (clock slew) are sufficiently small:

Acts as a negative edge-triggered master-slave D FF.





## C<sup>2</sup>MOS Register

**Races** are just not possible since the overlaps activate either the pull-up or the pull-down networks but never both simultaneously.


The inverters force 0-1 and 1-0 propagation modes only.

However, if the rise and fall times of the clock are slow, there exists a time slot in which *both* n- and p-transistors are conducting simultaneously.

Correct operation requires the clock rise/fall times be smaller than about **5 times** the propagation delay through the FF.

This is not hard to meet in practical designs, making C<sup>2</sup>MOS especially attractive in high speed designs where avoiding clock overlap is hard.


**Pipelining**

 

The minimum allowed clock for the pipelined system is:

$$T_{min} = t_q + \max(t_{d,add}, t_{d,abs}, t_{d,log}) + t_s$$

 
Implementation using pass-transistor based D latches



As indicated, races can occur when  $\phi$  and  $\bar{\phi}$  overlap.
 
## Pipelining



$C^2$ MOS latches can be used instead, but ONLY if the logic functions,  $F$ , implemented between the latches are **non-inverting**.



If  $F$  is inverting, and  $\phi$  and  $\bar{\phi}$  overlap (1-1), then  $C_2$  is discharged as shown above.

**NORA-CMOS** (NO-Race) targets the implementation of fast pipelined datapaths by combining  $C^2$ MOS with  $np$ -CMOS dynamic function blocks.

### Pipelining with NORA-CMOS

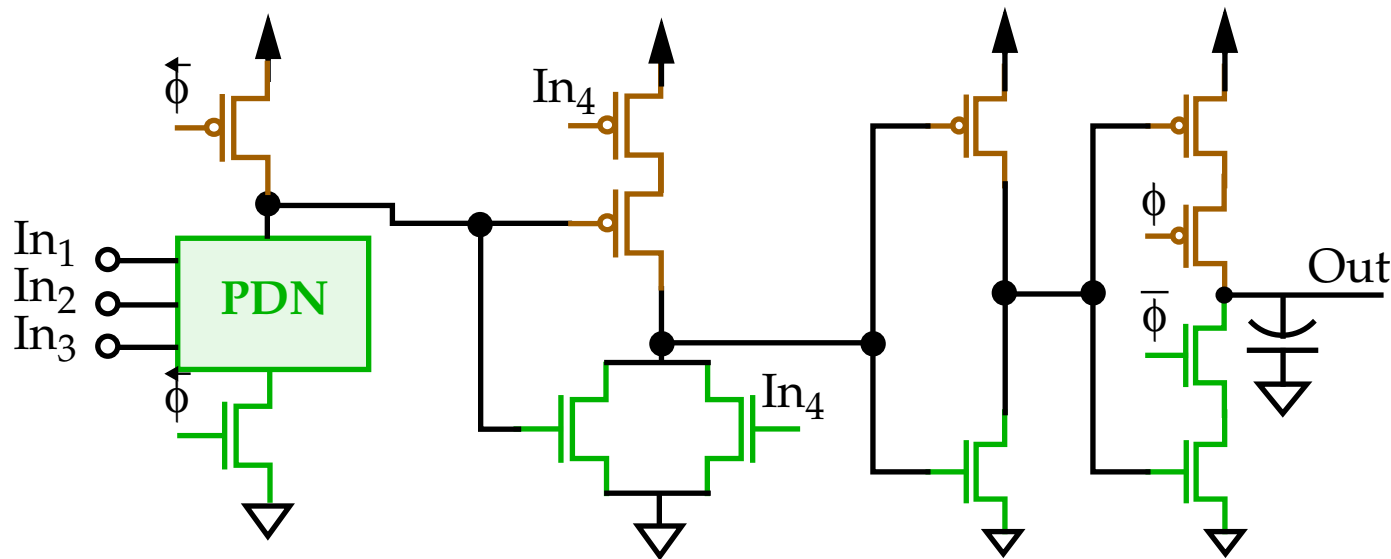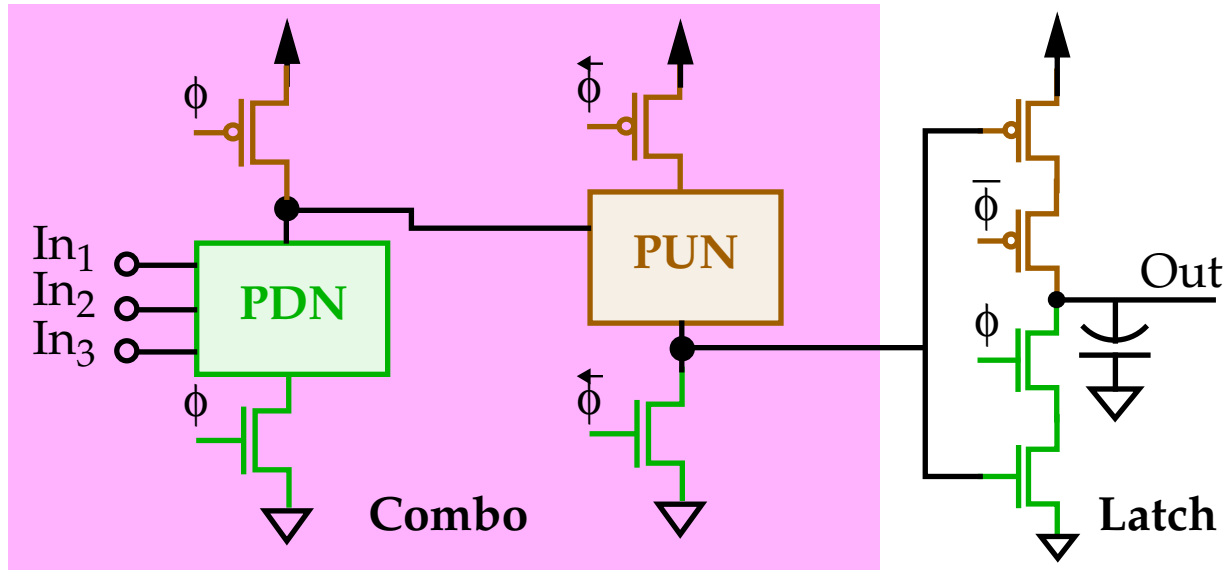


## Pipelining with NORA-CMOS

The NORA datapath consists of a chain of alternating  $\phi$  and  $\bar{\phi}$  modules.

While one class of modules is *precharging* with its output latch in **hold mode**, the other class is *evaluating*.

 Note that dynamic and static logic can be mixed freely.




Rule: # of static inversions between  $C^2$ MOS latches should be **even**. When *dynamic* gates are present, the # of static inverters between a latch and dynamic gate and between the last dynamic gate and latch should be **even**.



 
### True Single-Phase Clocked Logic (TSPCL)

The NORA design style can be simplified so that a **single clock** is sufficient.



Doubled  $n$ - $C^2$ MOS latch

 

Doubled  $p$ - $C^2$ MOS latch

For the doubled  $n$ - $C^2$ MOS latch, when  $\phi = 1$ , the latch is in the **transparent evaluate** mode and corresponds to 2 cascaded inverters (non-inverting).

When  $\phi = 0$ , both inverters are disabled (*hold* mode) -- only the pull-up network is still active.


The dual stage approach **completely eliminates races**.

This style combines the advantages of  $C^2$ MOS and eliminates all constraints.



### True Single-Phase Clocked Logic (TSPCL)

The one disadvantage is that 6 transistors (vs. 4) are needed per latch.

Include logic in the latch

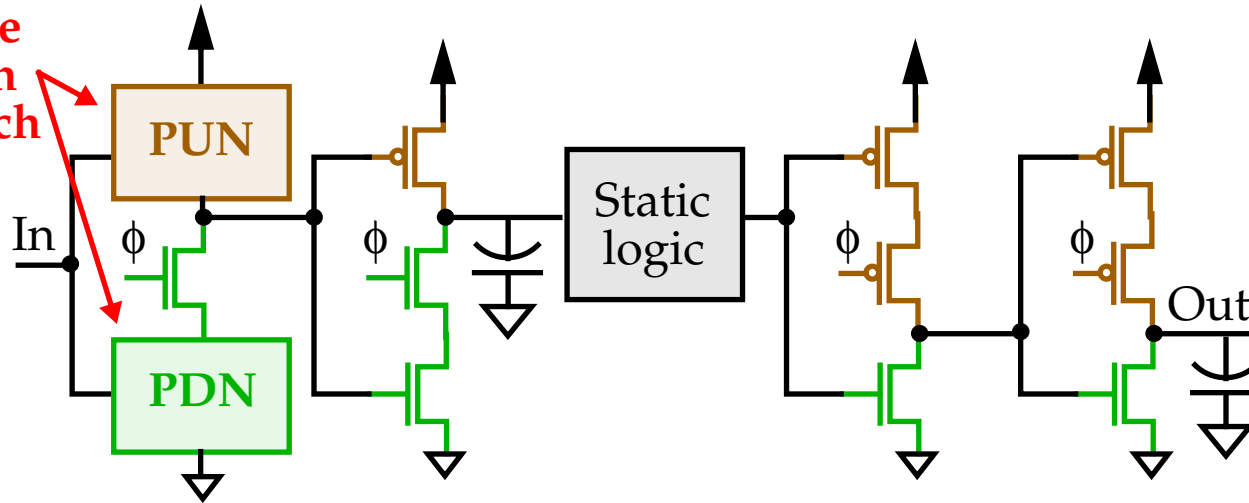

  
A further simplification is to control *only* the first inverter with the clock.



### True Single-Phase Clock Logic (TSPC)

This reduces the number of transistors and the clock load is **reduced in half**.

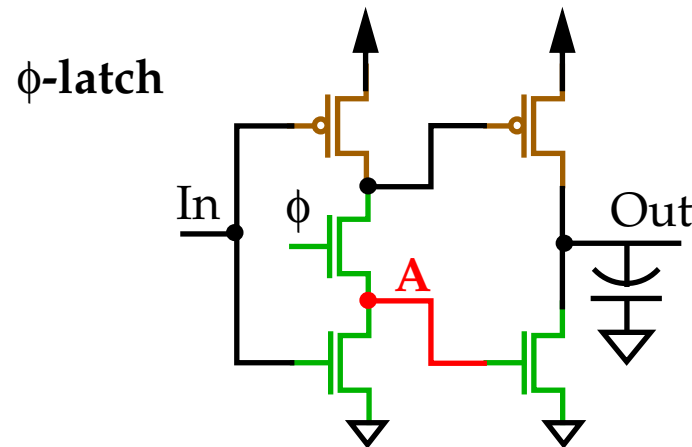Problem: not all node voltages experience the full logic swing.



Node  $A$  (for  $V_{in} = 0V$ ) maximally reaches  $V_{DD} - V_{Tn}$ .

This results in a reduced drive for the output NMOS transistor and a loss in performance.


This design methodology is called **True Single-Phase Clock Logic (TSPC)**.

It allows for the implementation of dynamic sequential circuits with a single clock.



### True Single-Phase Clock Logic (TSPC)

Edge-triggered FFs:

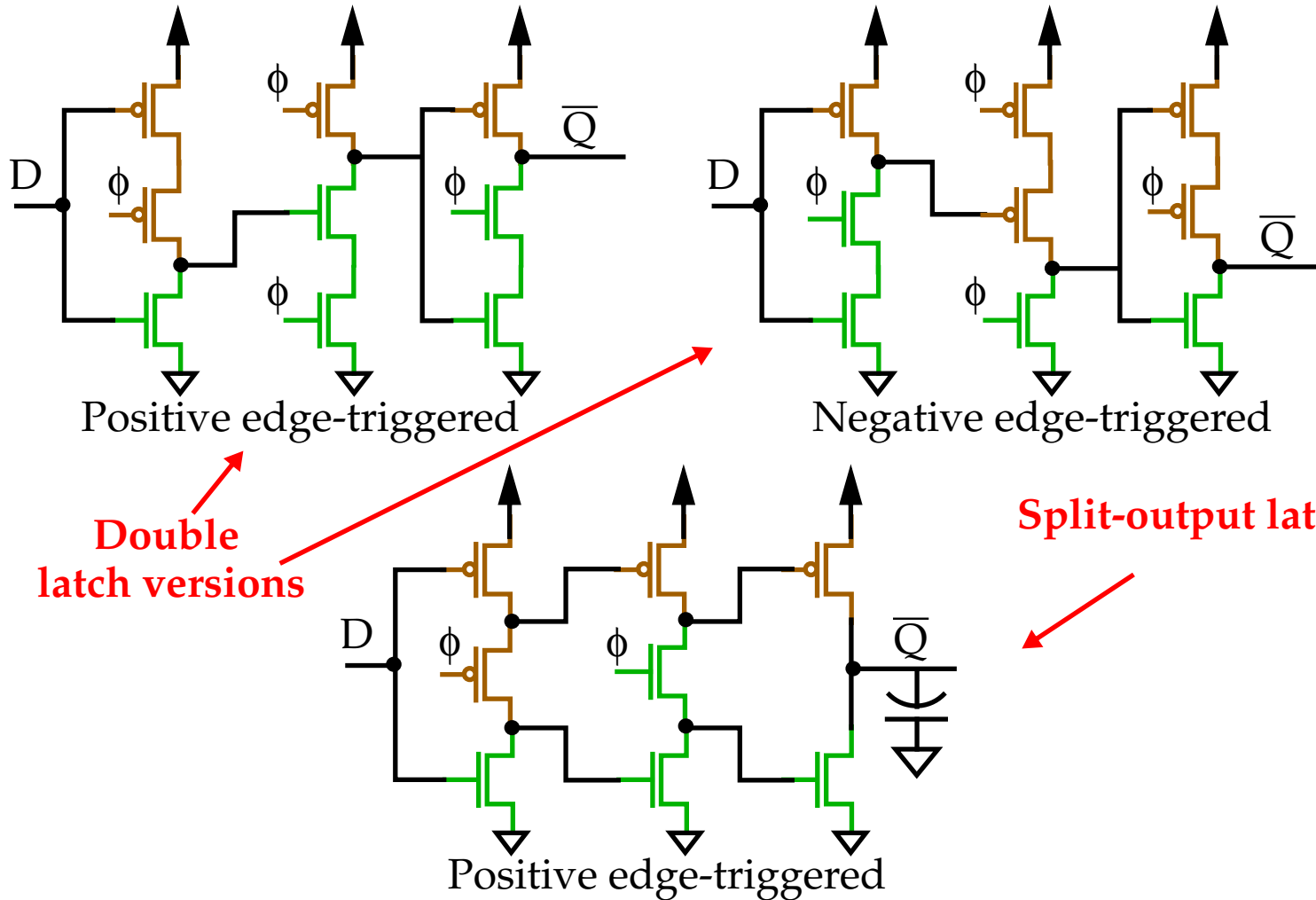

*Split-output* version reduces clock load in half, while performing well.

## Monostable Sequential Circuits


A circuit that generates a pulse of a *predetermined width* every time the circuit is triggered by a pulse or transition event (**one-shot**).

The circuit has **only one stable state** -- the quiescent state.

The trigger causes the circuit to go temporarily into a *quasi-stable* state.

It returns to its quiescent state after a time period determined by the circuit parameters.

 Useful for *address transition detection* (ATD) to generate timing in static memories for subsequent operations.




We've seen this version in edge-triggered FFs.


 
## Monostable Sequential Circuits

A second class uses feedback combined with an  $RC$  timing network to generate a pulse of fixed width.



Initially,  $In$  and  $Out$  are low and therefore  $A$  is high.  $B$  is high via resistor  $R$ .

Pulsing  $In$  high causes  $A$  to go low, pulling node  $B$  with it.

Node  $B$  gets pulled high again with time constant  $RC$ .

$Out$  goes low when  $B$  reaches  $V_M$ , which causes  $A$  to go high again (note  $In$  has already gone low again).

The width ( $t_2 - t_1$ ) is determined by the time-constant  $RC$  and  $V_M$ .

Unfortunately,  $V_M$  is relatively sensitive to process variations.



## Astable Sequential Circuits

A circuit with **no stable states**.

The output oscillates back and forth between two *quasi-stable* states with a period determined by circuit parameters.

The main application of such a circuit is **on-chip clock generation**.

  We already looked at the *ring oscillator* as an example.



Ring oscillator

The period  $T$  of the oscillation is:

$$T = 2 \times t_p \times N \quad \text{where } N \text{ is the \# of inverters in the chain.}$$

where  $t_p$  is the propagation delay of the composing gates.




### Astable Sequential Circuits

By tapping the ring oscillator at different stages, a wide range of clock signals with different duty-cycles and phases can be derived.

It is often desirable to tune the frequency of oscillation.

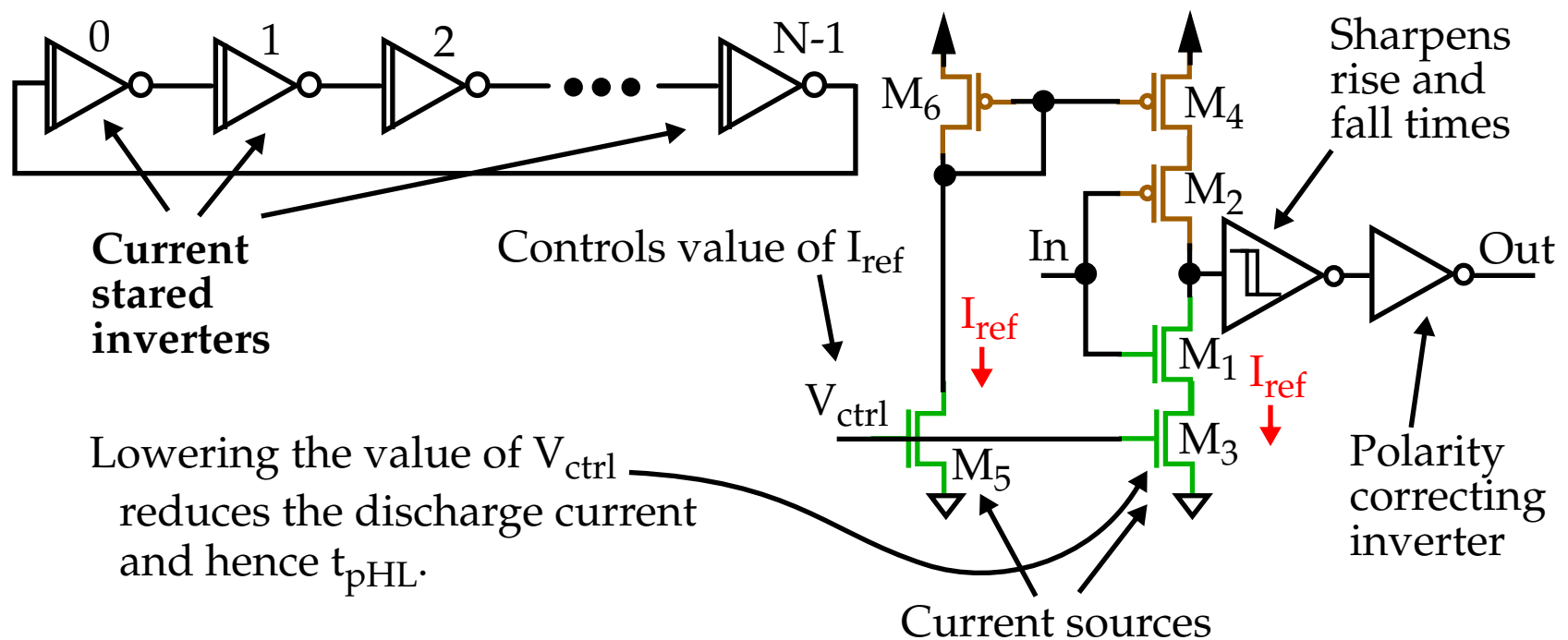An example is a **Voltage-controlled Oscillator (VCO)**, whose frequency is proportional to the value of a control voltage.



### Astable Sequential Circuits

Charging current is controlled via  $M_5$ .

$I_{\text{ref}}$  is translated into a charging current through the **current mirror**  $M_6 - M_4$ .

Here,  $M_6$  acts as a **diode** and sets a bias voltage  $V_{\text{GS6}}$ , that is controlled by  $I_{\text{ref}}$ .

With  $V_{\text{GS4}} = V_{\text{GS6}}$  and both devices operating in *saturation*,  $I_{\text{DS4}} = I_{\text{DS6}} = I_{\text{ref}}$ .

Since both  $M_3$  and  $M_5$  operate in *saturation*, a quadratic relation exists between  $V_{\text{ctrl}}$  and  $I_{\text{ref}}$  (and  $t_p$ ).

This allows the frequency of the VCO to be controlled over a large range.

A Schmitt trigger is used to **sharpen** the weakened rise and fall times of the *current-stared inverter*.

Note that transistors  $M_5$  and  $M_6$  can be shared over all inverters in the chain.