


## Algorithms for Fault Simulation

Purposes of fault simulation during design cycle:

- Guiding the TPG process.
- Measuring the effectiveness of the test patterns.
- Generating fault dictionaries.


Fault simulator needs in addition to the circuit model, stimuli and expected responses (that are needed for true-value simulation):

- Fault model
- Fault list

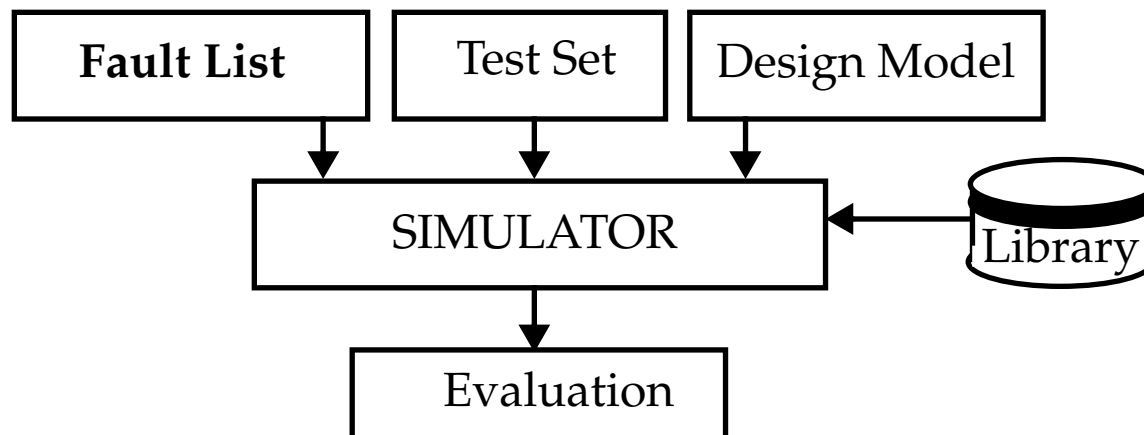
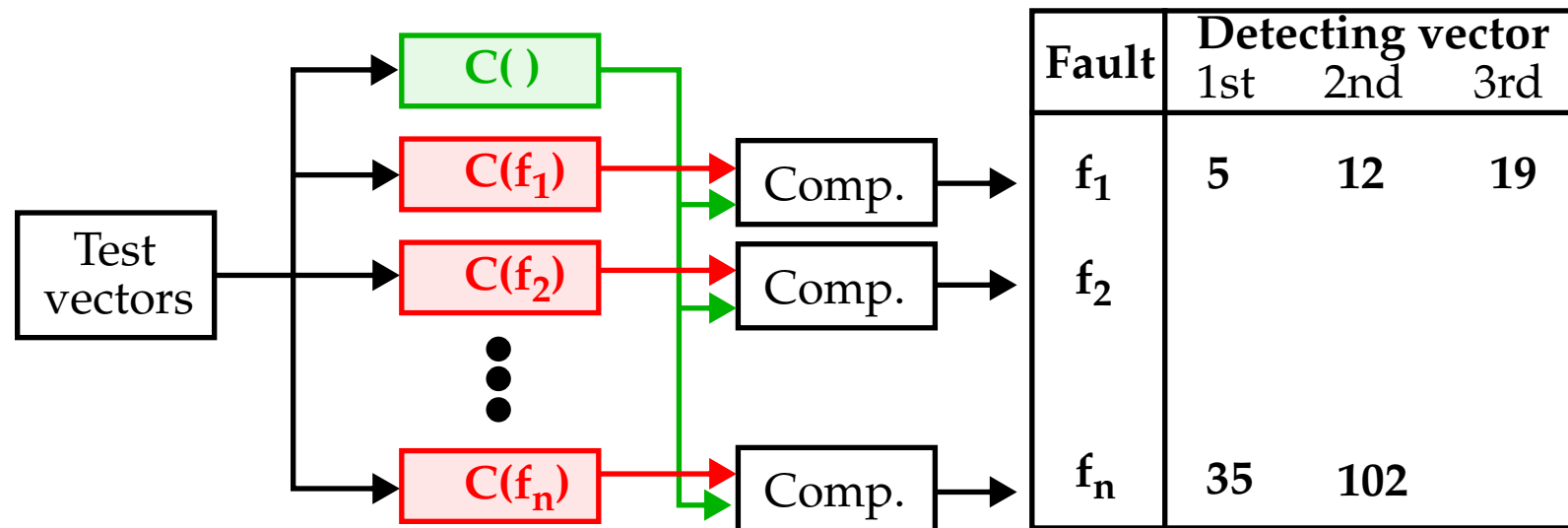
## Algorithms for Fault Simulation

The fault simulator must classify the given target faults as *detected* or *undetected* by the given stimuli.



$C(f_1) \dots C(f_n)$  are copies of the defect-free circuit  $C()$  with fault  $f_x$  permanently inserted.

Here, each time the fault is detected, the simulator records the vector number (and possibly the output(s) in error).

Although useful for **fault diagnosis**, this is compute expensive.

**Fault dropping** causes simulation of  $C(f_n)$  to stop after vector 35.

## Serial Fault Simulation

If fault dropping is not employed, the effort of simulating  $n$  faults is equivalent to either:

- Simulating a circuit  $n$  times larger or
- Repeating the original true-value simulation  $n$  times.

## Serial Fault Simulation

True-value simulation is performed across all vectors and outputs saved. Faulty circuits are simulated one-by-one by modifying circuit and running true-value simulator.

Simulation of faulty circuit stops as soon as fault is detected.

Adv:

Any type of fault can be simulated, e.g., stuck-at, stuck-open, bridges, delay and analog faults.

For  $n$  faults, CPU time can be almost  $n$  times that of a true-value simulator.

Fault dropping significantly improves on this.

## Parallel Fault Simulation

Most effective when:

- Circuit consists of only logic gates.
- Stuck-at faults are modeled.
- Signals assume only binary, 0 or 1, values.
- All gates have the same delay (zero or unit).

Under these conditions, circuits  $C(f_n)$  are almost identical.

Here, the bit-parallelism of logical operations in a computer can be useful. For a 32-bit word, 1 fault-free and 31 faulty circuits can be simultaneously simulated.

This yields a speed up of  $w - 1$ , with  $w$  equal to the word size.


If fault dropping is employed, simulation stops when all  $w - 1$  faults are detected.

Therefore, serial fault simulation has more to gain by fault dropping.


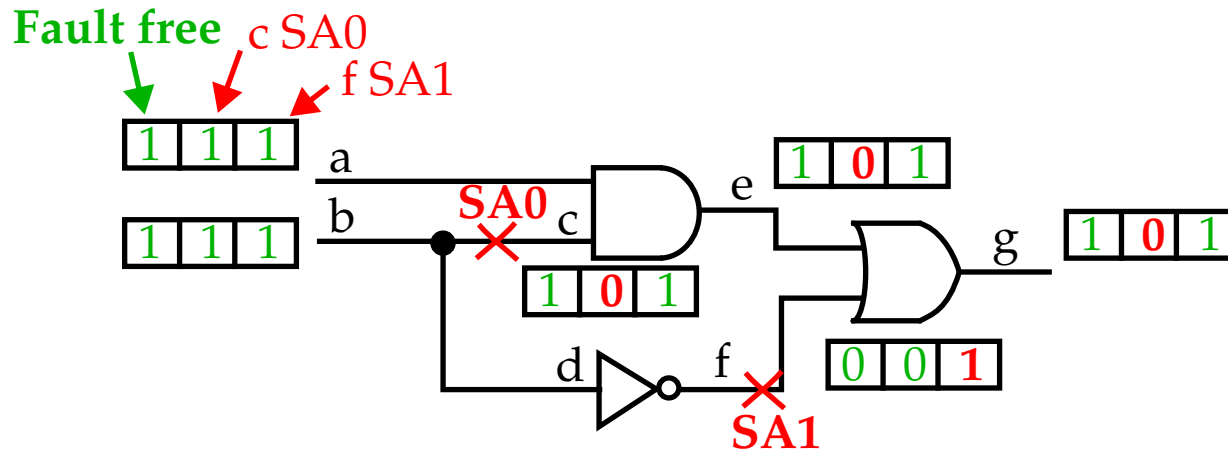
## Parallel Fault Simulation

Parallel fault simulation of two faults,  $c$  SA0 and  $f$  SA1:



Parallel fault simulation cannot accurately model rise and fall delays.

The signal values in all circuits are processed simultaneously.


Zero-delay or unit-delay are used.

Compiled-code or event-driven versions are possible.

Multi-valued logic is possible, e.g., (0, 1, X and Z), by encoding state in more than 1 bit.

A true-value logic simulator can be used as a parallel fault simulator by inserting gates to model faults -- see text.

**Parallel Fault Simulation**

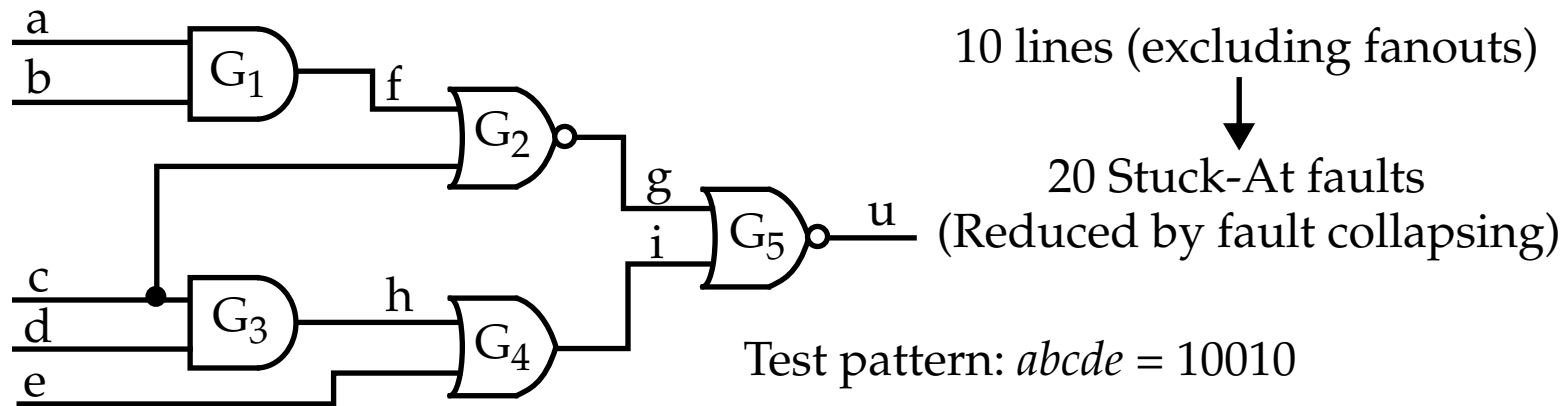

Reduction possible:  $f$  SA1 **eq**  $g$  SA0,  $f$  SA1 **dom**  $b$  SA1 and  $u$  SA0 **dom**  $g$  SA0.

	ff	a/0	b/1	c/1	d/0	e/1	f/0	f/1	g/0	g/1	h/0	h/1	i/0	i/1	u/0	u/1
a=1	1	<b>0</b>	1	1	1	1	1	1	1	1	1	1	1	1	1	1
b=0	0	0	<b>1</b>	0	0	0	0	0	0	0	0	0	0	0	0	0
c=0	0	0	0	<b>1</b>	0	0	0	0	0	0	0	0	0	0	0	0
d=1	1	1	1	1	<b>0</b>	1	1	1	1	1	1	1	1	1	1	1
$f=ab$	0	0	<b>1</b>	0	0	0	0	<b>1</b>	0	0	0	0	0	0	0	0
$g=f+c$	1	1	<b>0</b>	<b>0</b>	1	1	1	<b>0</b>	<b>0</b>	1	1	1	1	1	1	1
$h=cd$	0	0	0	<b>1</b>	0	0	<b>1</b>	0	0	0	0	<b>1</b>	0	0	0	0
e=0	0	0	0	0	0	<b>1</b>	0	0	0	0	0	0	0	0	0	0
$i=e+h$	0	0	0	<b>1</b>	0	<b>1</b>	<b>1</b>	0	0	0	0	<b>1</b>	0	<b>1</b>	0	0
$u=g+i$	<b>1</b>	1	<b>0</b>	1	1	1	1	<b>0</b>	<b>0</b>	1	1	1	1	1	<b>0</b>	1

### Deductive Fault Simulation

Circuit model assumptions are the same as those given for the parallel fault simulator, compiled-code and event-driven versions possible.

Only the fault free circuit,  $C()$ , is simulated.

Faulty circuit values are deduced from the fault-free values.

It processes all faults in a **single pass** of true-value simulation, i.e., it very fast!

Note, however, that major modifications are required (and slow downs) to handle variable rise/fall delays, multiple signal states, etc.

A vector is simulated in true-value mode.


A deductive procedure is then performed on all lines in level-order from inputs to outputs.

Fault lists are generated for each signal using the fault lists on the inputs to the gate generating that signal.


 
### Deductive Fault Simulation

The fault list of a signal contains the *names* of all faults in the circuit that can change the state of that line.






Gate type	Inputs		Output	Output fault list $L_c$
	$a$	$b$	$c$	
AND	0	0	0	$[L_a \text{ intersection } L_b] \text{ union } c_1$
	0	1	0	$[L_a \text{ intersection } \bar{L}_b] \text{ union } c_1$
	1	0	0	$[\bar{L}_a \text{ intersection } L_b] \text{ union } c_1$
	1	1	1	$[L_a \text{ union } L_b] \text{ union } c_0$
OR	0	0	0	$[L_a \text{ union } L_b] \text{ union } c_1$
	0	1	1	$[\bar{L}_a \text{ intersection } L_b] \text{ union } c_0$
	1	0	1	$[L_a \text{ intersection } \bar{L}_b] \text{ union } c_0$
	1	1	1	$[L_a \text{ intersection } L_b] \text{ union } c_0$
NOT	0	-	1	$L_a \text{ union } c_0$
	1	-	0	$L_a \text{ union } c_1$



   
### Deductive Fault Simulation

For example, if both inputs to a 2-input AND are 0, in order for a fault to propagate through, it must be in the lists of both inputs.



Fault-list,  $L_x$ , intersection  $!L_y$  is equivalent to  $L_x \cap !L_y = L_x - (L_x \cap L_y)$

True-value simulation is run first.

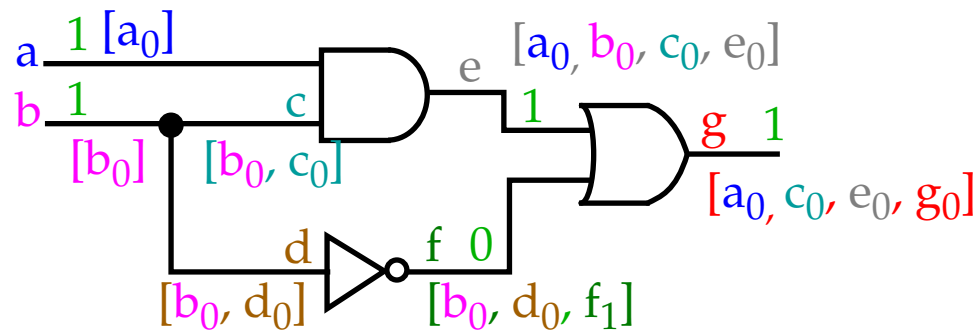


Fault list for  $e$  is composed from the union of the input lists for  $a$  and  $c$ , since the input is  $ab = (11)$ .

Fault list for  $g$  is given by the intersection of  $e$ 's list and  $!f$ 's list.

**Deductive Fault Simulation**

Another example:

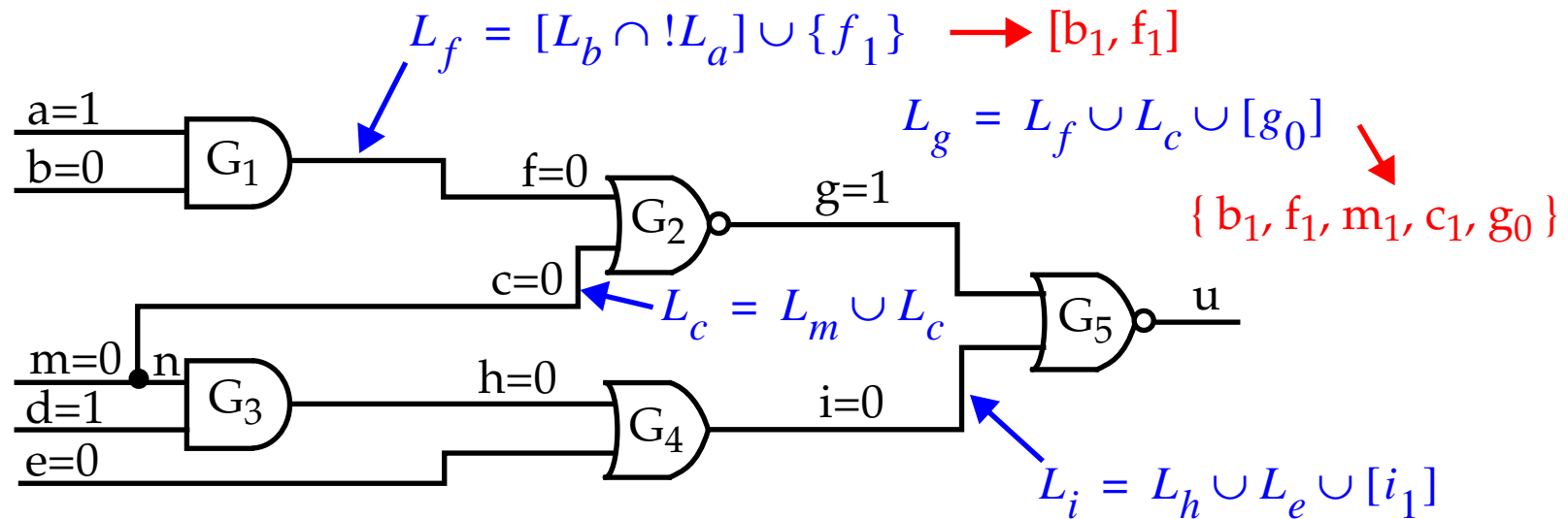

With  $ab = 10$ , only  $L_b$  is sensitizable to  $f$  (faults on  $a$  are masked).

The faults given by  $L_f = [L_b \cap !L_a] \cup [f_1]$  are the faults in  $L_b$  that are not in  $L_a$  union  $[f_1]$ . Therefore,  $L_f = [b_1, f_1]$ .

Had  $b = 1$ ,  $L_a$  would have been sensitized to  $f$ , e.g.,

$$L_f = L_a \cup L_b \cup [f_1]$$

## Concurrent Fault Simulation

It extends the event-driven simulation method to simulation of faults.

It can handle various types of circuit models, faults, signal states and timing models.

Details of the simulator model:

- Events

*Good events*: Occur in the fault-free circuit,  $C()$ , and have three attributes, signal name, type of transition (0-to-1) and time of change.

*Fault-events*: Occur on same lines in faulty circuits,  $C(f_1)...C(f_n)$ , but ONLY if transition is different from  $C()$  transition. Three attributes + fault site and type.

- Circuit

Modeled in the same way as for true-value simulation.

Each *good-gate* has a fault list of *bad-gates* associated with it.

*Bad-gates* are not faulty but rather have an I/O that is affected by some fault.



### Concurrent Fault Simulation


- Faults

Whenever the signal values of a *good-gate* make a fault active, a *bad-gate* is inserted into the fault list on that *good-gate*.

Event-driven simulation is carried out.

Good-events and fault-events make good-gates active for evaluation.

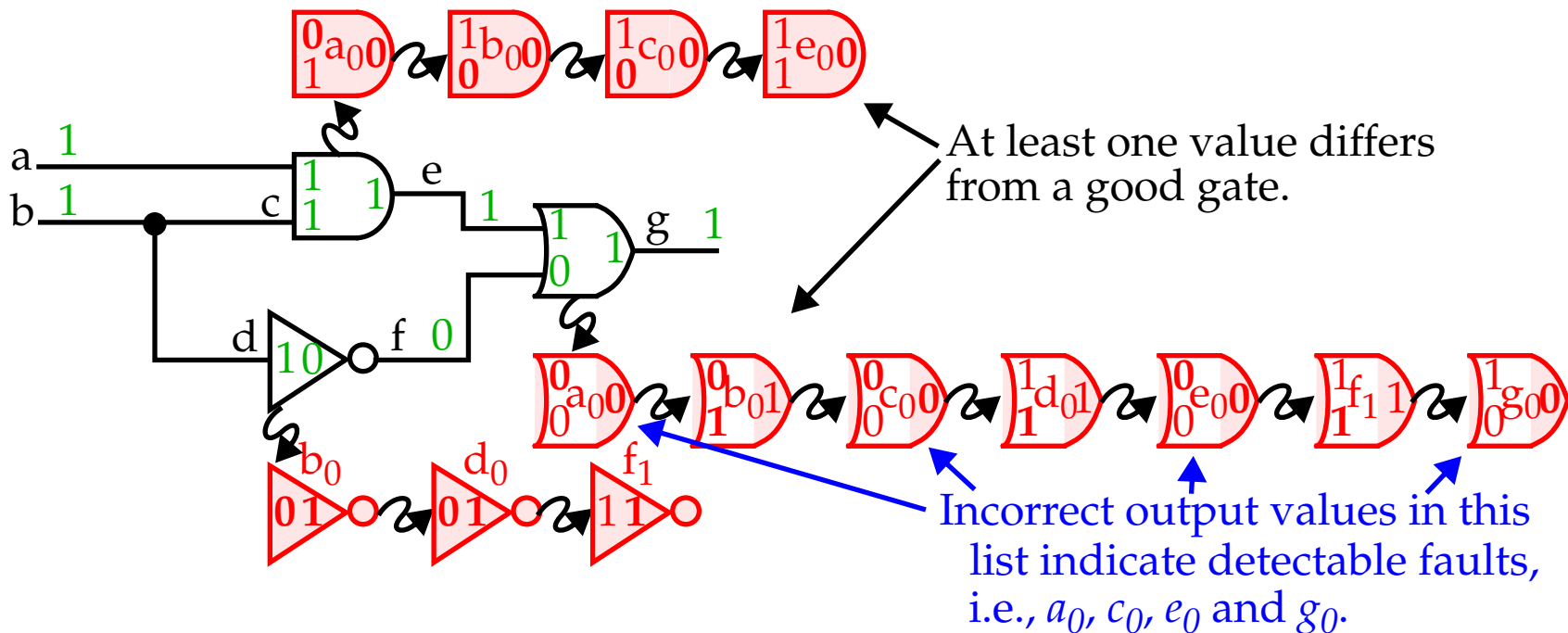Good-events also make bad-gates active for evaluation.




### Concurrent Fault Simulation

This agrees with the deductive fault simulator results.

Note that deductive list is smaller -- fault lists include faults that affect a **signal line**.

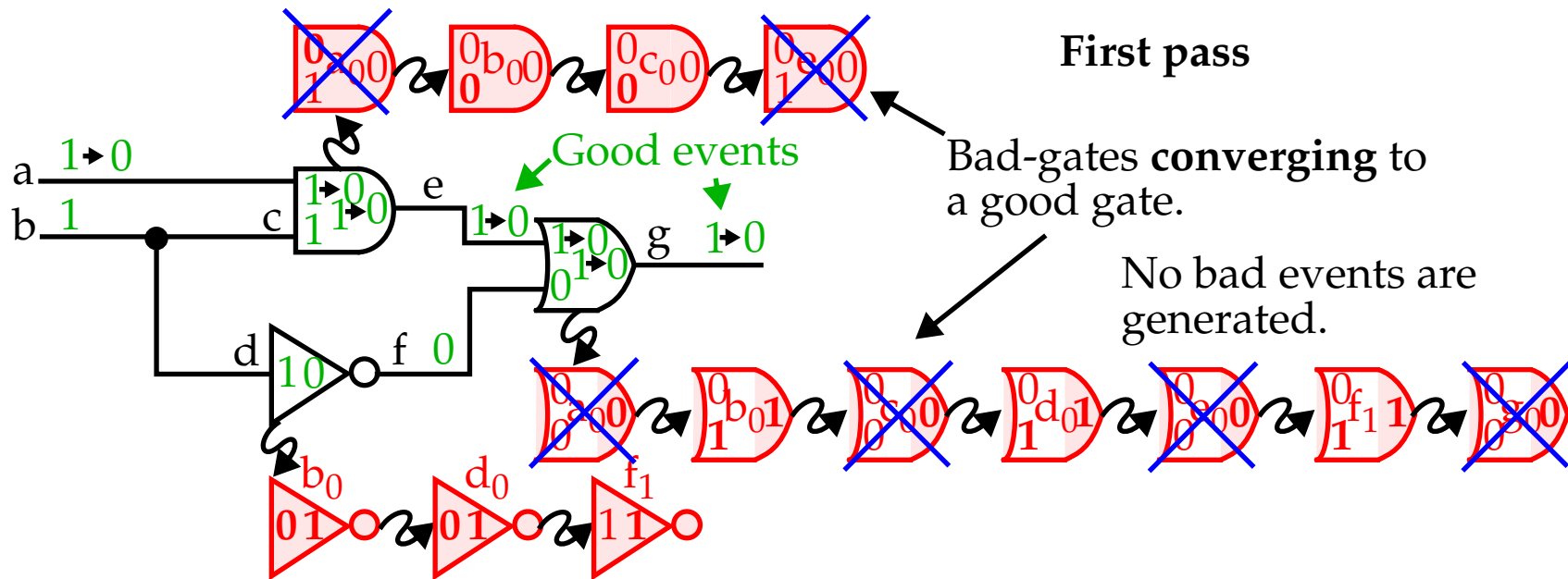
In contrast, concurrent list contains faults that affect the **gate** and includes those that affect its inputs (adv in memory, RTL and behavioral models).



Note that we did not *drop*  $a_0$ ,  $c_0$ ,  $e_0$  and  $g_0$  after the first simulation for illustration only.
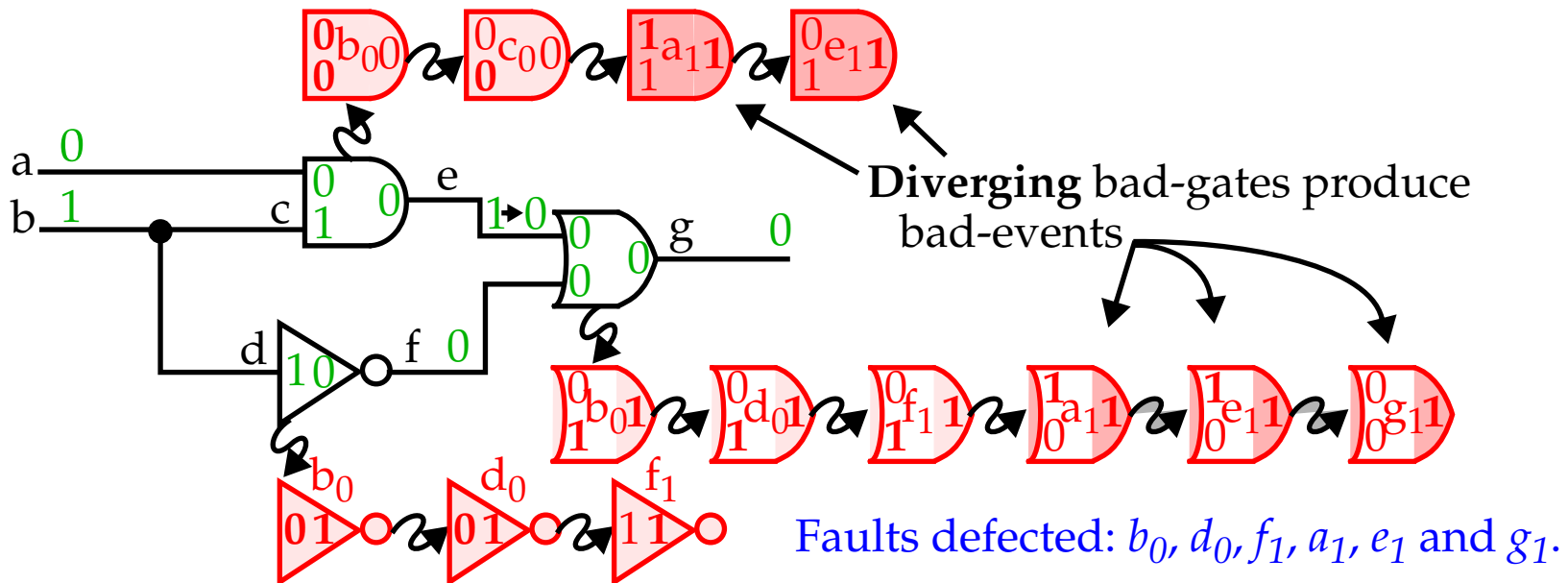
### Concurrent Fault Simulation

Second pass processes the activation of fault  $a_1$  under the good-event transition



The most significant advantages of this algorithm are:

- Efficiency -- redundant computation is eliminated.
- Modeling flexibility -- anything that can be simulated.

MARS, CREATOR, MOZART, MOTIS and FMOSSIM are examples.


### Roth's TEST-DETECT Algorithm

The circuit is simulated for a vector in true-value mode to determine node states (zero delay model is assumed).

Faults are then simulated one at a time to determine which are detected by this vector.

For *two-value* simulation, the signal state given as (*fault-free, faulty*) can take 4 possible assignments.
 
$$0 = (0, 0), 1 = (1, 1), D = (1, 0) \text{ and } \bar{D} = (0, 1)$$



*D*-calculus is used to represent both fault-free and faulty values.

Starting at the fault site, if fault is activated, a *D* or  $\bar{D}$  is placed there.

The symbol is propagated, if it reaches an output, fault is detectable.

## Differential Fault Simulation

Cheng and Yu made 2 improvements on TEST-DETECT.

- Eliminated the use of *D*-calculus.
- Eliminated the explicit restoration to true-value before processing the next fault.

The algorithm, which starts with a vector set and a fault list:

- Simulate a vector in *true-value* mode and store the PO values.
- Activate a fault by creating a transition to the faulty value, e.g., if *true-value* is 0 and it is a SA1, generate a 0 -> 1 transition.
- Simulate the circuit and check for a difference at POs -- drop the fault if detected.
- For next fault, **restore** to true value by placing a restoring transition at previous site. Place a second transition at new fault site and simulate.
- Repeat with the next vector once all faults have been analyzed.

**PROOFS:** a popular, parallel implementation of this *differential fault* simulation algorithm.

Both this and TEST-DETECT can handle synchronous sequential circuits.