



4. Draw a layout diagram of the implementation

5. Implement this circuit on the breadboard. Ask your TA to check your implementation and sign your report.