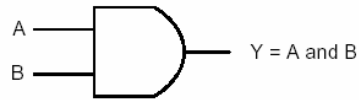


Lecture Notes - Lab 1

Basic logic gates

And Gate



A	B	Y=AB
0	0	0
0	1	0
1	0	0
1	1	1

Or Gate



A	B	Y=A+B
0	0	0
0	1	1
1	0	1
1	1	1


2/8/2006

1

Lecture Notes - Lab 1


Basic logic gates

Inverter

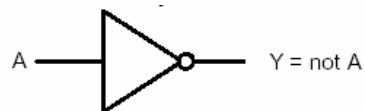

A	Y=notA
0	1
1	0

NAND

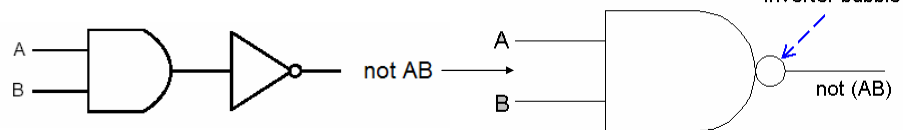

Elementary Theorem - Identity

$$X * 1 = X; X * 0 = 0 \quad X + 1 = 1; X + 0 = X$$


2/8/2006

2

Lecture Notes - Lab 1


Logic gates

Nor Gate

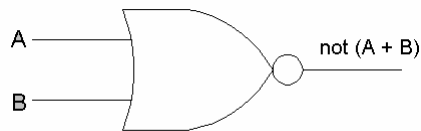

A	B	A+B	Y=not(A+B)
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

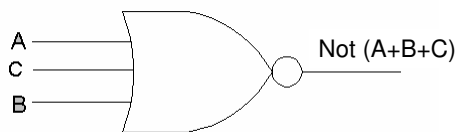Create two-input Nor with three-input Nor



We Want
Not (A+B+C) = Not (A+B)

C = ?

2/8/2006

3

Lecture Notes - Lab 1

Example 1

Design a circuit for the following function:

$$F3 = (Y + Z')X + X'YZ$$

X	Y	Z	X'	Z'	Y + Z'	(Y + Z')X	X'YZ	F3
0	0	0	1	1	1	0	0	0
0	0	1	1	0	0	0	0	0
0	1	0	1	1	1	0	0	0
0	1	1	1	0	1	0	1	1
1	0	0	0	1	1	0	0	1
1	0	1	0	0	0	0	0	0
1	1	0	0	1	1	0	1	1
1	1	1	0	0	1	0	0	1

$$F3 = XY + XZ' + X'YZ$$

F3 equals 1 when XY or XZ' or X'YZ equals 1

2/8/2006

4

Lecture Notes - Lab 1

K-maps

$$F3 = (Y + Z')X + X'YZ$$

X	Y	Z	X'	Z'	Y + Z'	(Y + Z')X	X'YZ	F3
0	0	0	1	1	1	0	0	0
0	0	1	1	0	0	0	0	0
0	1	0	1	1	1	0	0	0
0	1	1	1	0	1	0	1	1
1	0	0	0	1	1	1	0	1
1	0	1	0	0	0	0	0	0
1	1	0	0	1	1	1	0	1
1	1	1	0	0	1	1	0	1

1- Map TT to K-map

		Y Z			
		00	01	11	10
X	0	0	0	1	0
	1	1	0	1	1

2/8/2006

2- Simplify the boolean function

		Y Z			
		00	01	11	10
X	0	0	0	1	0
	1	1	0	1	1

$$F3 = YZ + XZ'$$


5

Lecture Notes - Lab 1

Design an AND/OR circuit


$$F3 = YZ + XZ'$$

Logic diagram

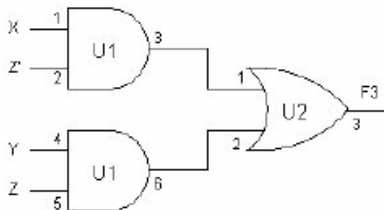

2/8/2006

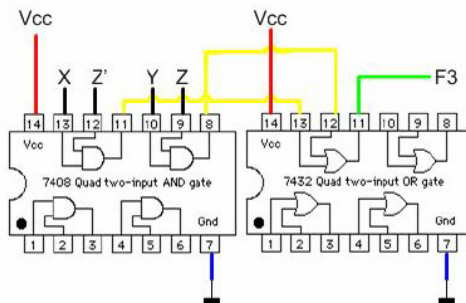Layout diagram - position on the breadboard



6

Lecture Notes - Lab 1

Example 2

Consider the following 4 variable function:

$$F4 = B'CE' + A'B'E' + AC'E' + ABC'E$$

A B C E	A	B'	C'	E'	B'CE'	A'B'E'	AC'E'	ABC'E	F4
0000	1	1	1	1	0	1	0	0	1
0001	1	1	1	0	0	0	0	0	0
0010	1	1	0	1	1	1	0	0	1
0011	1	1	0	0	0	0	0	0	0
0100	1	0	1	1	0	0	0	0	0
0101	1	0	1	0	0	0	0	0	0
0110	1	0	0	1	0	0	0	0	0
0111	1	0	0	0	0	0	0	0	0
1000	0	1	1	1	0	0	1	0	1
1001	0	1	1	0	0	0	0	0	0
1010	0	1	0	1	1	0	0	0	1
1011	0	1	0	0	0	0	0	0	0
1100	0	0	1	1	0	0	1	0	1
1101	0	0	1	0	0	0	0	1	1
1110	0	0	0	1	0	0	0	0	0
1111	0	0	0	0	0	0	0	0	0

2/8/2006

7

Lecture Notes - Lab 1

1- Maps the TT to K-map

		C E			
		00	01	11	10
A B	00	1	0	0	1
	01	0	0	0	0
	11	1	1	0	0
	10	1	0	0	1

2- Simplify the boolean function

		C E			
		00	01	11	10
A B	00	1	0	0	1
	01	0	0	0	0
	11	1	1	0	0
	10	1	0	0	1

$$F4 = B'E' + ABC'$$

2/8/2006

8

Lecture Notes - Lab 1


Design a NAND circuit: $F4 = B'E' + ABC'$

$$F4 = F4'' = ((B'E' + ABC')')$$


$$F4 = ((B'E')'(ABC')')$$

By using Demorgan's identity

Logic diagram

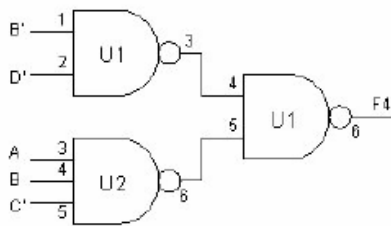

2/8/2006

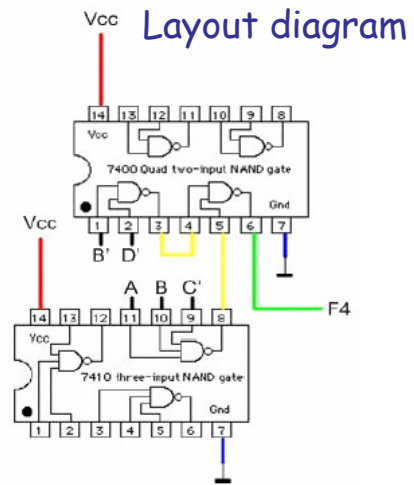

9