

Name _____
Date _____
Section _____

Lab 7 Worksheet

Design Analysis

Draw a block diagram of what would be an 8-bit wide ripple carry adder.

Creating, synthetizing and simulating a Half Adder (HA)

Step 1

- Turn in a copy of your completed *half_adder.vhd* code.

Creating, synthetizing and simulating a Full Adder (FA)

Step 2

- Turn in a copy of your completed *full_adder.vhd* code.

Creating, synthetizing and simulating a 4-bit Full Adder (FA)

Step 3

- Turn in a copy of your completed *four_bit_full_adder_tb.vhd* file.

Creating, synthetizing and simulating an Accumulator

Step 4

- Turn in a copy of your completed *accumulator.vhd* code.

Name _____
Date _____
Section _____

Implementing the Accumulator

Step 5

Have your TA verify that your accumulator works. Signature _____

Resources Analysis

Step 6

How many CLBs is using your system?

Final Task

Step 7

Demonstrate the system to the T.A
T.A signature:

Bonus Activity

Step 8

Demonstrate the system to the T.A
T.A signature:

1. How many CLBs is using your system? Is it more or less than the original design? Why?
2. Print down your code for the accumulator and attach it to your final report.

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.