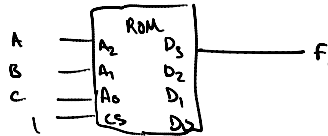


$F_1(A, B, C) = ABC$ using 8×4 Rom

Program Rom using $A_2 = A, A_1 = B, A_0 = C$
 $D_3 = F_1$ as shown



| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |


$F_1(A, B) = AB, F_2(A, B) = A+B$ Use 8×4 Rom

| A | B | F_1 | F_2 |
|---|---|-------|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Use $A_2 = 0, A_1 = A, A_0 = B, D_3 = F_1, D_2 = F_2$

| A_2 | A_1 | A_0 | D_3 | D_2 | D_1/D_0 |
|-------|-------|-------|-------|-------|-----------|
| 0 | 0 | 0 | 0 | 0 | - |
| 0 | 0 | 1 | 0 | 1 | - |
| 0 | 1 | 0 | 0 | 1 | - |
| 0 | 1 | 1 | 1 | 1 | - |


All others

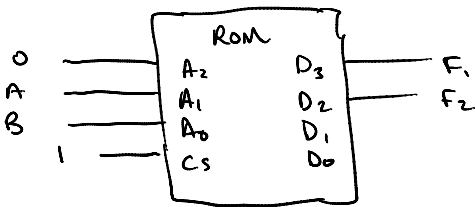

$F(A, B, C, D) = AB + BC + ABCD$ use 8×4 Rom plus any additional needed logic

$$F(A, B, C, D) = F_{A=0}(B, C, D)\bar{A} + F_{A=1}(B, C, D)A$$

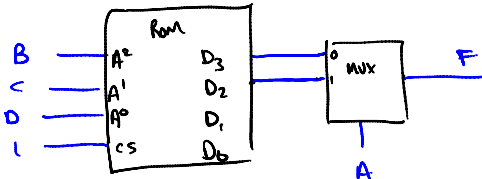Set $\begin{cases} A_2 = B \\ A_1 = C \\ A_0 = D \end{cases}$ $F_{A=0}$ in D_3
 $F_{A=1}$ in D_2



| B | C | D | D_3 | D_2 |
|-------|-------|-------|-------|-------|
| A_2 | A_1 | A_0 | | |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

$$F_{A=0}(B, C, D) = F(0, B, C, D) = BC = D_3$$

$$F_{A=1}(B, C, D) = F(1, B, C, D) = B + BC + BCD = B = D_2$$

Sketch of a 5-variable problem $F(A,B,C,D,E)$

Use 4-to-1 Mux, uses 2 inputs

