

ECE 238 Exam 2

Problem 1 20 /20

Problem 2 25 /25

Problem 3 30 /30

Problem 4 25 /25

Total 100

Name: Solutions

Good Luck!

Problem 1 (20 points total)

We would like to build a Moore circuit that outputs the sequence:


1, 0, 0, 0, 1, and the sequence repeats.

1(a)(4 points) Give the state diagram that realizes this sequence. *Hint:* You will need 5 states.

1(b)(8 points) Derive the state table for implementing the circuit using D flip-flops.



1(c)(5 points) Use K-maps to compute optimal expressions for the inputs to the D flip-flops.

1(d)(3 points) Show the final circuit.


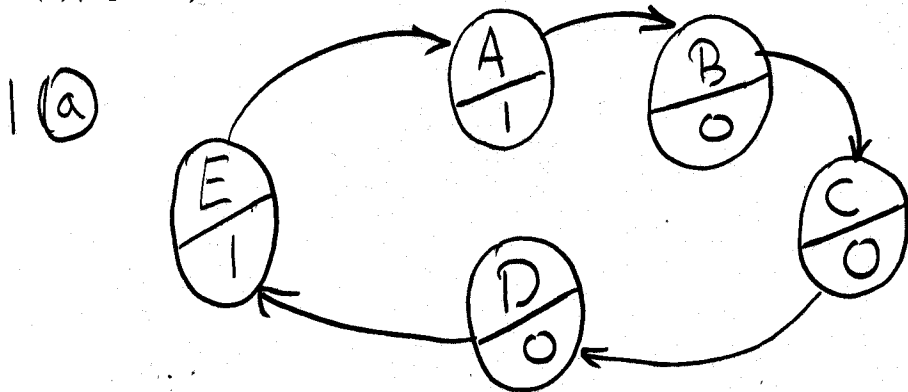


1(b) Q_2, Q_1, Q_0 Present State D_2, D_1, D_0 inputs, Next State Output

A: 000	B: 001	1	} For the rest of the states: 111, 100, 101, next states and output are set to x.
B: 001	C: 011	0	
C: 011	D: 110	0	
D: 110	E: 010	0	
E: 010	A: 000	1	

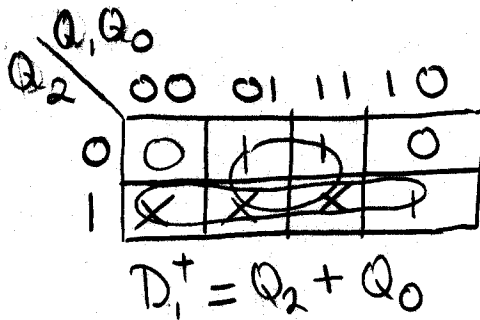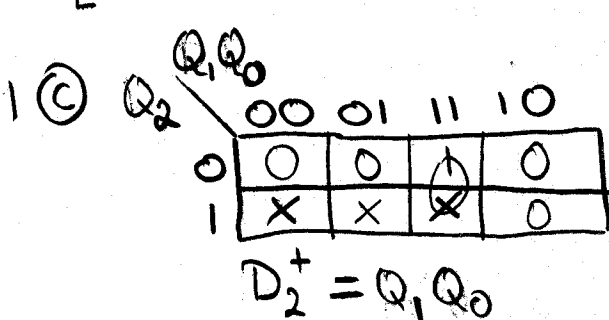


$Z = \overline{Q_2} \overline{Q_0}$

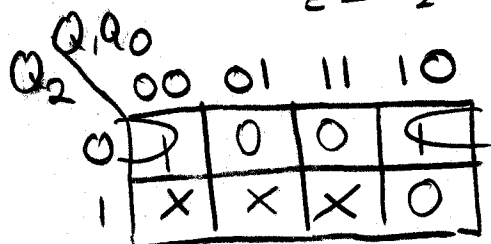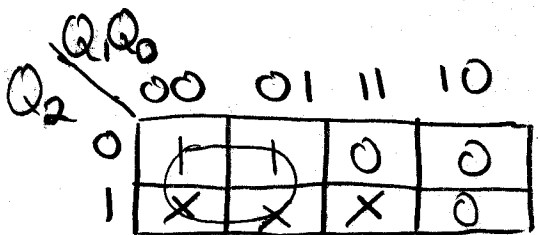

10

1-2
2

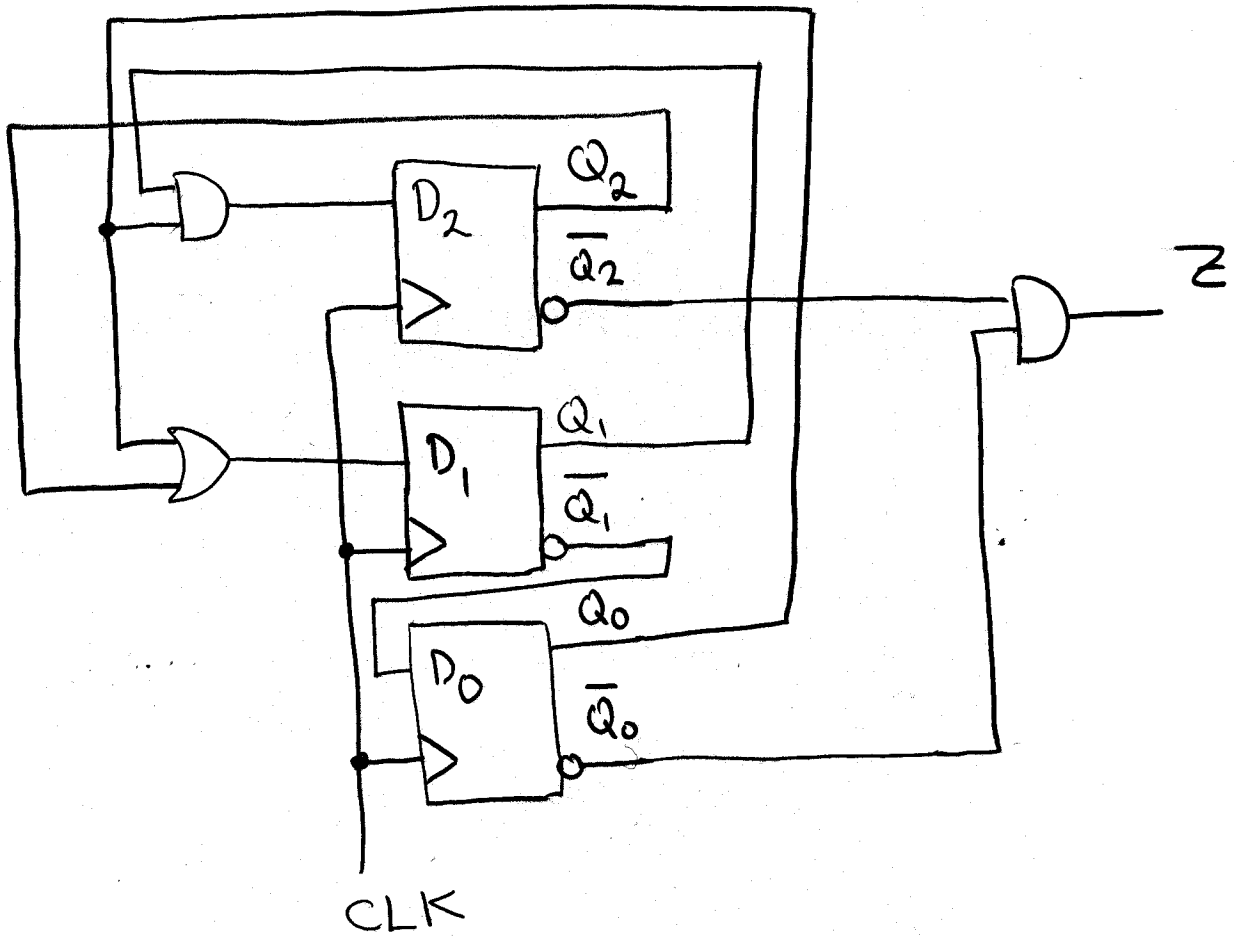

Problem 2 (25 points total)


We want to build a Moore circuit that outputs a 1 if the number of 1s received can be expressed as $4k + 1$ where $k = 0, 1, \dots$ is an integer.

As an example, consider the following input/output sequence:

Input: 001111100
Output: 0001000100

Note that in this Moore circuit, after the first 1 is received, the output becomes 1 in the next clock cycle. Then the output becomes 1 after four more 1s have been received.

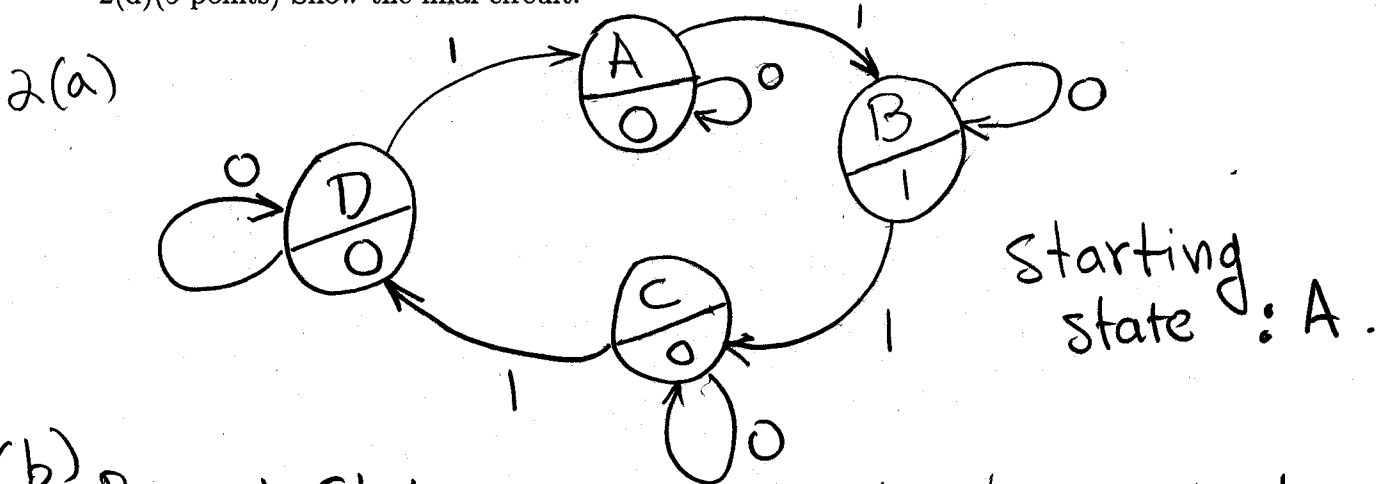- 2(a)(5 points) Give the Moore state diagram for this problem.
- 2(b)(10 points) Derive the state table for implementing the circuit using D flip-flops.
- 2(c)(5 points) Use K-maps to compute optimal expressions for the inputs to the D flip-flops.
- 2(d)(5 points) Show the final circuit.



2(b)

Present State Q_1, Q_0	Next State		Output
	$X=0$	$X=1$	
A: 00	00	01	0
B: 01	01	11	1
C: 11	11	10	0
D: 10	10	00	0

Next state and D-Flip-flop input equations are the same.

2(c)

Q_1, Q_0	x	0	1
00		0	0
01		0	*
11		*	*
10		*	0

$$D_1 = Q_0x + Q_1\bar{x}$$


Q_1, Q_0	x	0	1
00		0	*
01		*	*
11		*	0
10		0	0

$$D_0 = \bar{Q}_1x + Q_0\bar{x}$$

Q_1	Q_0	0	1
0		0	0
1		0	0

$$z = \bar{Q}_1Q_0$$

2(d)

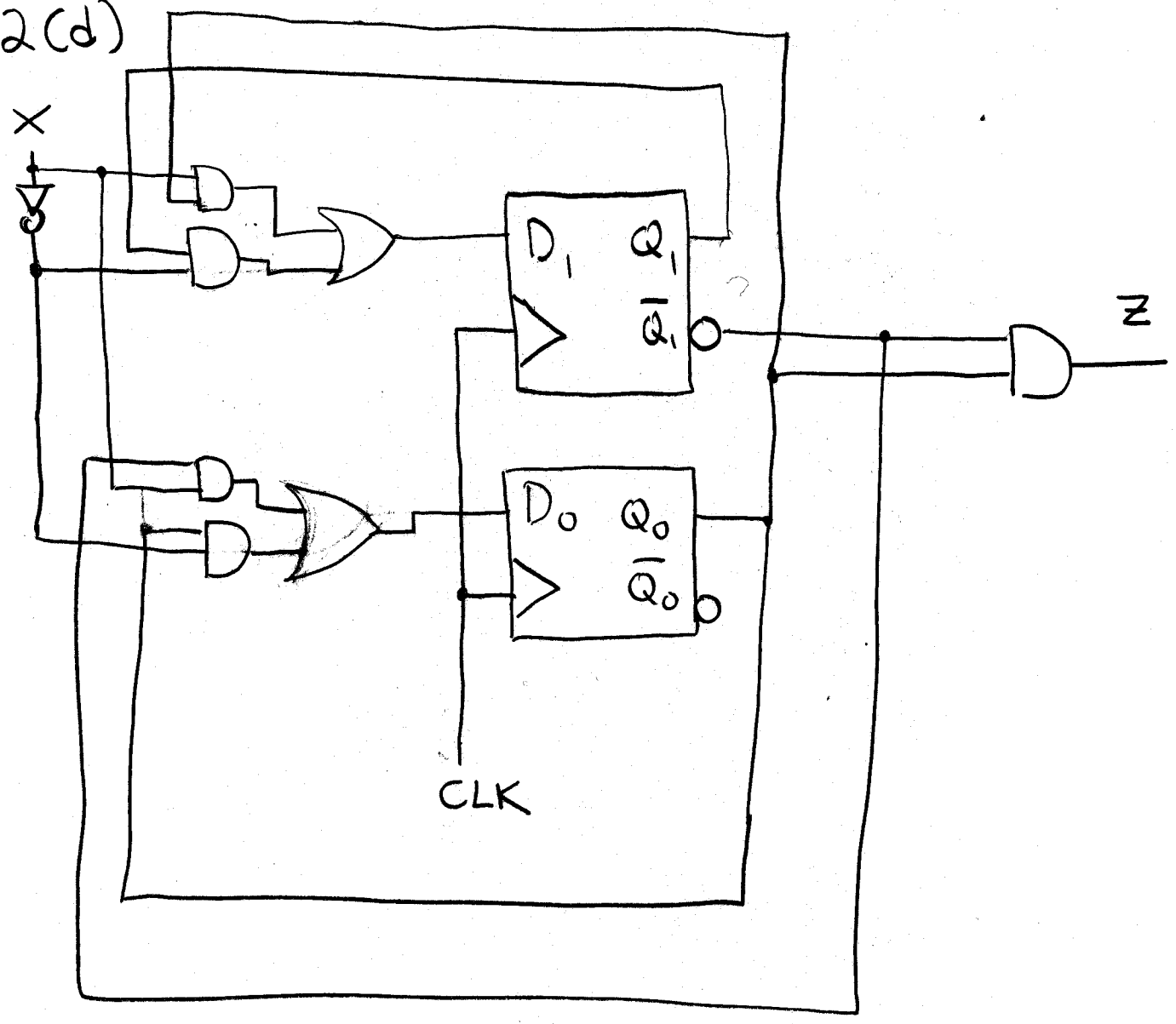

Problem 3 (30 points total)


We would like to use the serial adder circuit below to add: $2 - 1$. We also want to modify the circuit as described below.

3(a)(5 points) Indicate how to initialize the registers and the carry to zero.

3(b)(10 points) Indicate how to use the inputs to compute $2 - 1$.

For full credit, you will need to show:

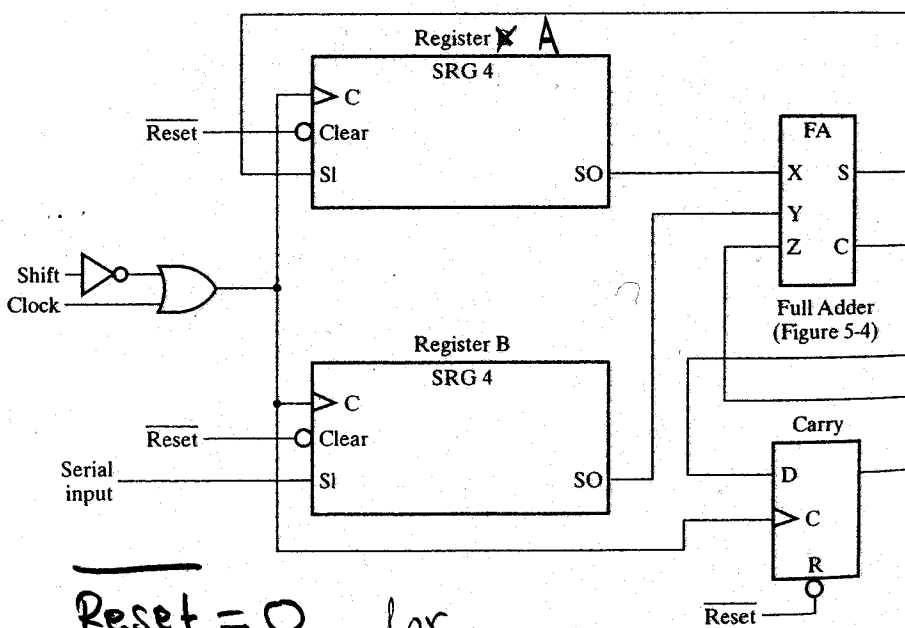- values of all inputs
- the states of registers A, B and the Carry, with respect to the rise of the clock
- if the states of the registers or the Carry cannot be determined, simply mark them with X.



3(a) Set $\text{Reset} = 0$ for Carry, Registers A & B.

3(b)

	SI	Reg B	Reg A	Carry
2	0	0000	0000	0
	1	0000	0000	0
	0	1000	0000	0
	0	0100	0000	0
-1	1	0010	0000	0
	1	1001	0000	0
	1	1100	1000	0
	1	1110	0100	0

* Changes occur after next ↑


* Shift = 1 for all clock periods. (Shift = 0 at end)

We need four more ↑s:

SI	Reg B	Reg A	Carry
0	1111	0010	0
0	0111	1001	0
0	0011	0100	1
0	0001	0010	1
0	0000	0001	1

shift=0

3ce)

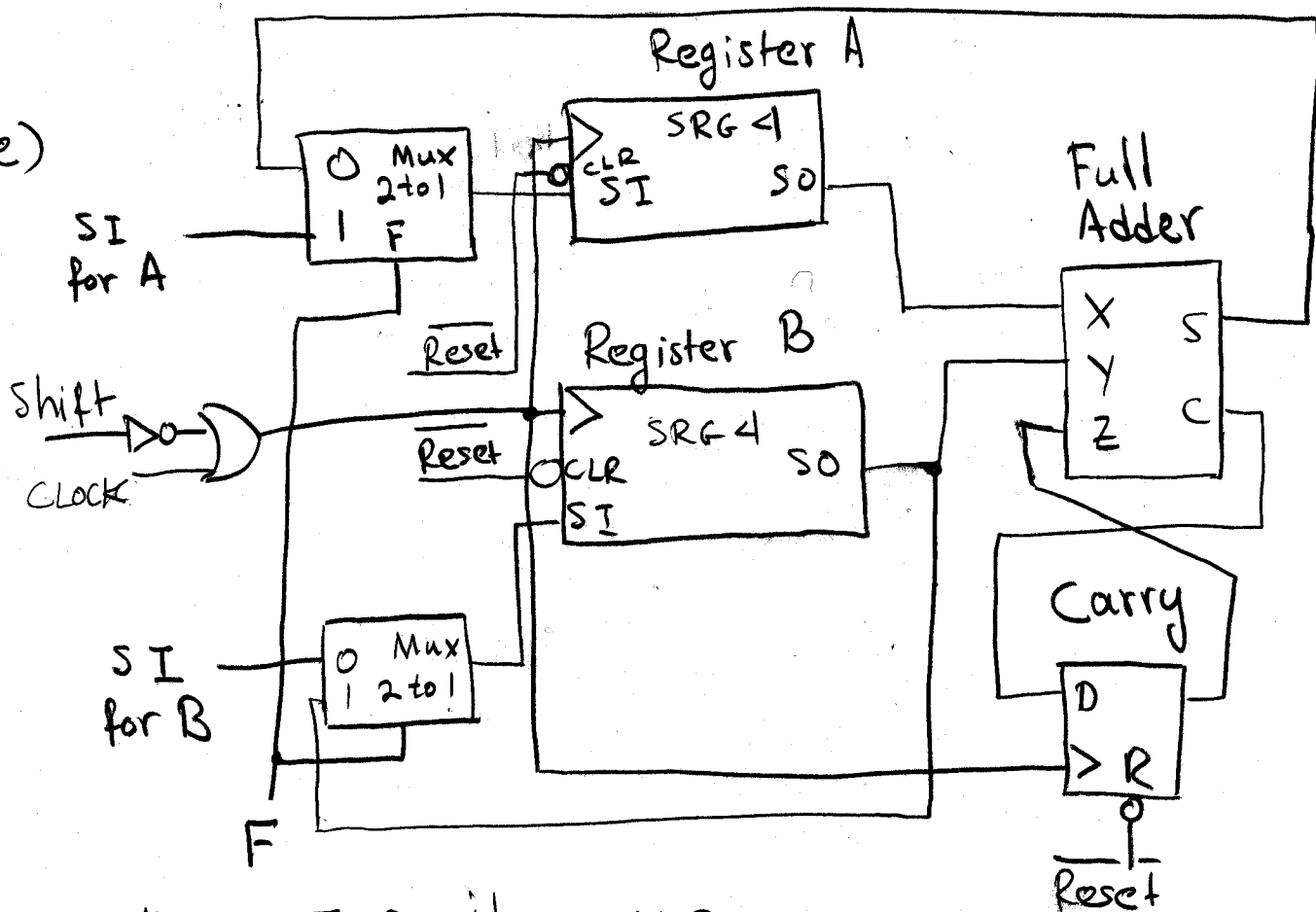

* When $F=0$, it works as before.

* When $F=1$, A gets SI and B gets its value shifted back in.

3(c)(2 points) Please indicate when we need to reset the Carry bit to zero.


3(d)(5 points) Suppose that we want to modify the circuit for performing subtractions. That is assume that we want to compute $A - N_1 - N_2 - \dots$. Indicate how you will have to modify the circuit to do this.

3(e)(8 points) Suppose that we want to modify the circuit so that A can either: (i) store the result of the addition, as it is setup right now, or (ii) load in a new value into A, while leaving B unchanged. Indicate how this can be accomplished in 4 cycles.

Hint: Use two 2-to-1 multiplexers and any additional logic (if needed) to accomplish the task.

3(c) The carry should be reset to zero every four cycles (after each addition).

3(d)

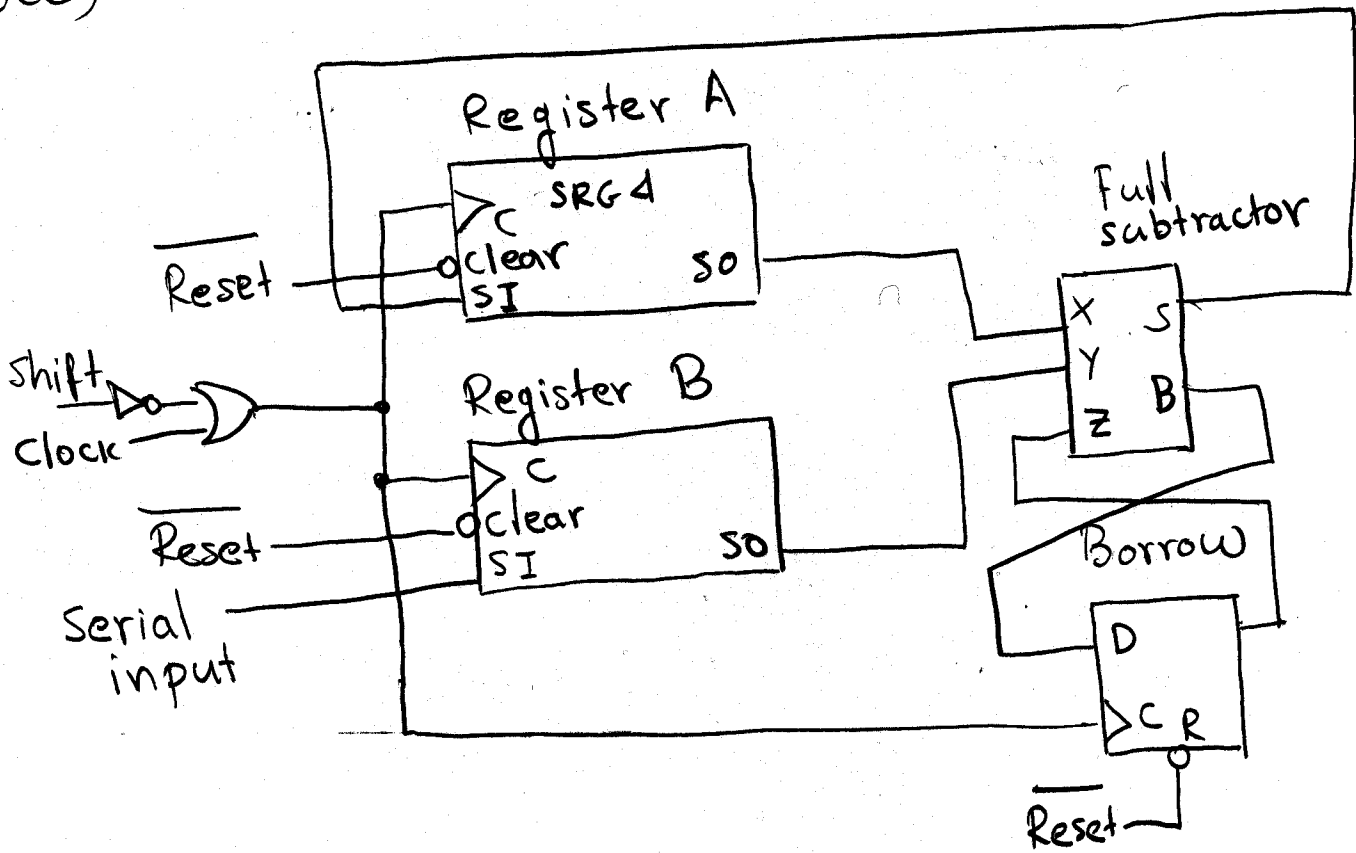

3(e) See page 3-2.

Problem 4 (25 points total) Design a binary counter that counts from 0 to 7:

0, 1, 2, 3, 4, 5, 6, 7 and then the counting repeats.


4(a)(5 points) Draw the state transition diagram.

4(b)(10 points) Derive the state table for implementing the counter using D Flip-Flops.

4(c)(5 points) Use K-maps to minimize the inputs to the D Flip-Flops.

4(d)(5 points) Show the final circuit.

4(a)

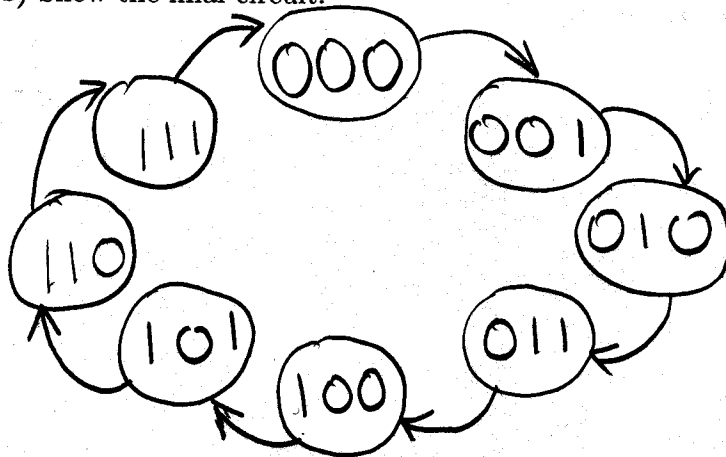

4(b)

Present state $Q_2 Q_1 Q_0$	Next State / Flip-Flop Inputs $Q_2^+ Q_1^+ Q_0^+ / D_2 D_1 D_0$
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
0 1 1	1 0 0
1 0 0	1 0 1
1 0 1	1 1 0
1 1 0	1 1 1
1 1 1	0 0 0

4(c)

Q_2	$a_1 a_0$	00	01	11	10
0		0	0	0	0
1		0	0	0	0

Q_2	$Q_1 a_0$	00	01	11	10
0		0	0	0	0
1		0	0	0	0

$$D_2 = \bar{Q}_2 a_1 a_0 + Q_2 \bar{Q}_0 + Q_2 \bar{Q}_1$$

$$D_1 = \bar{Q}_1 a_0 + Q_1 \bar{Q}_0$$

Q_2	$a_1 a_0$	00	01	11	10
0		0	0	0	0
1		0	0	0	0

$$D_0 = \bar{Q}_0$$

