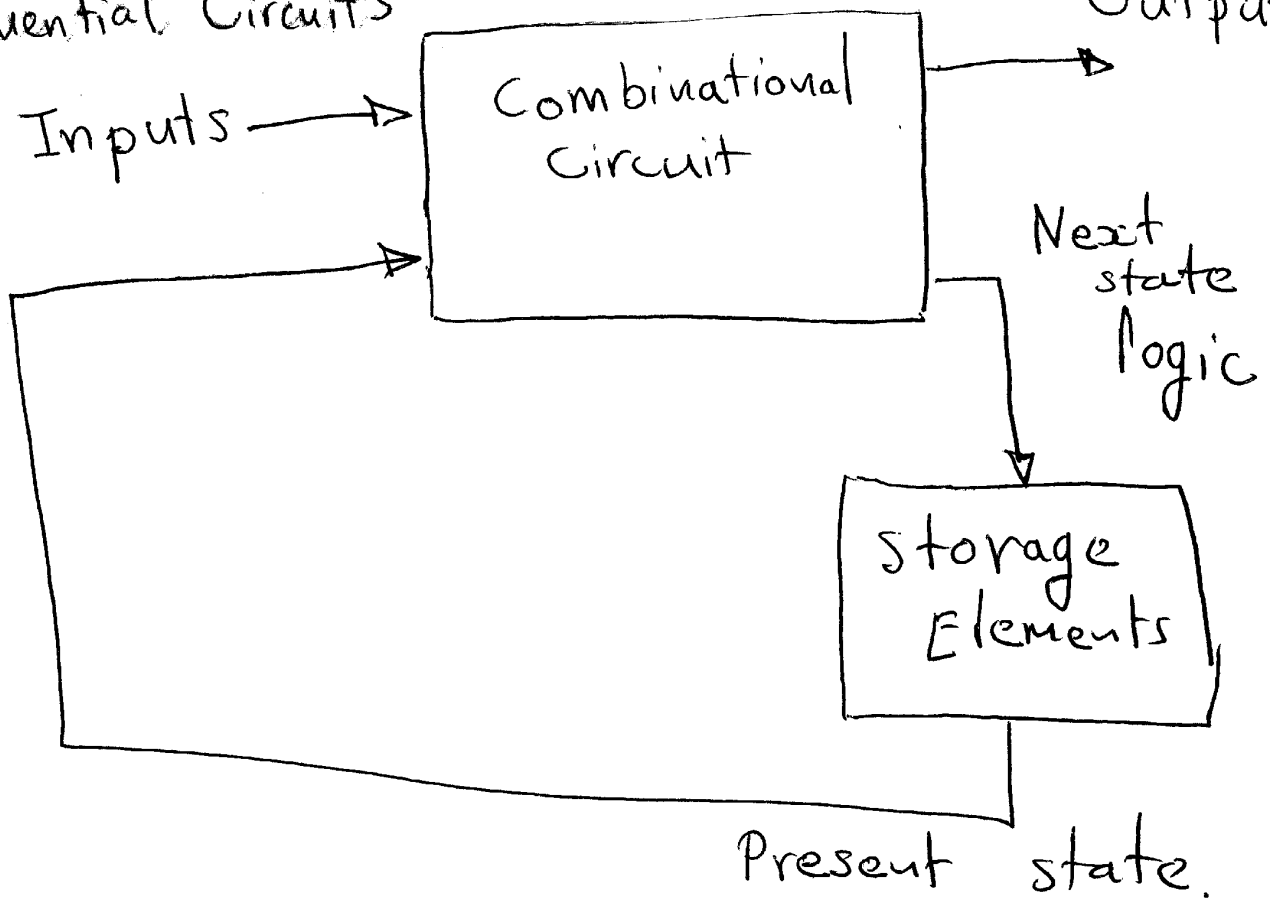



Chapter 4 (sec. 4.1-4.3) p. 1/16
Sequential Circuits




eg: drink dispenser machine.
It remembers the money we put in.



synchronous sequential circuits:

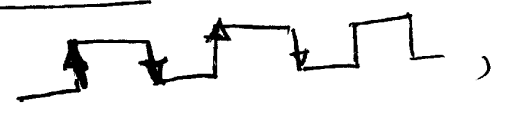We have a clock:



and we only allow changes when we have: (i) a rising edge  or

a falling edge  of the clock. (edge-trigger)

or (ii) when clock is at $c=0$  or $c=1$ . (pulse-trigger)


Asynchronous sequential circuits

2/16

- Like combinational circuits, changes occur when the inputs change.

For asynchronous circuits, to avoid oscillations, inputs cannot change indefinitely.


Eg:

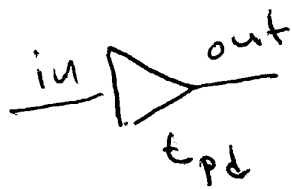

, reproduces its


A buffer:

input after t_{pd} :

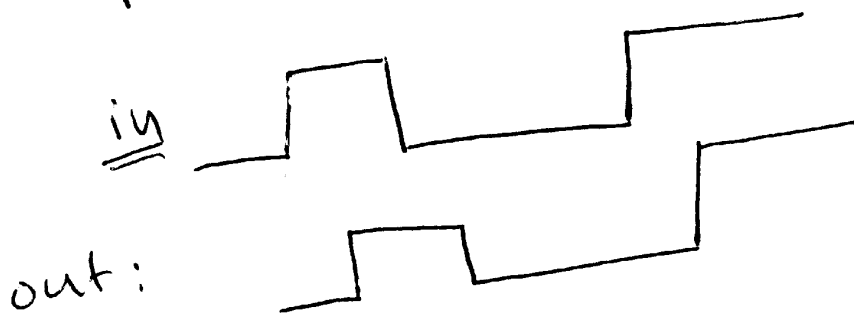


delayed input by t_{pd}


will converge with feedback:

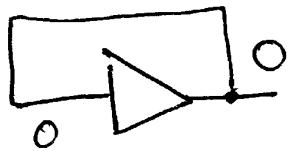


or

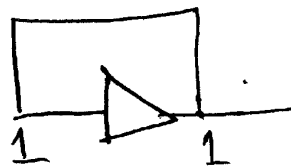


A single inverter will oscillate:

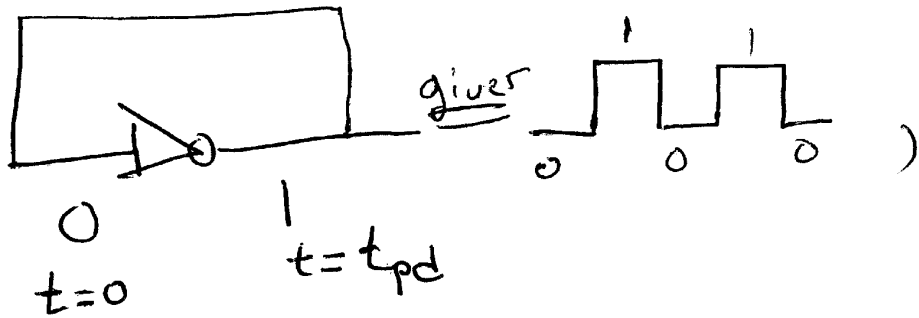

but 2 inverters will work:

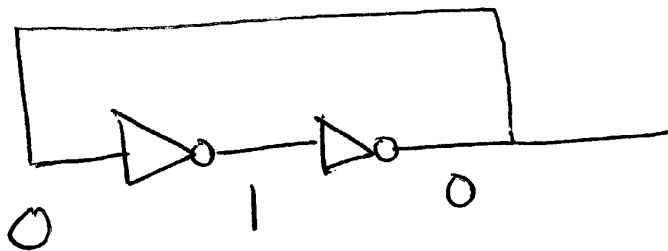

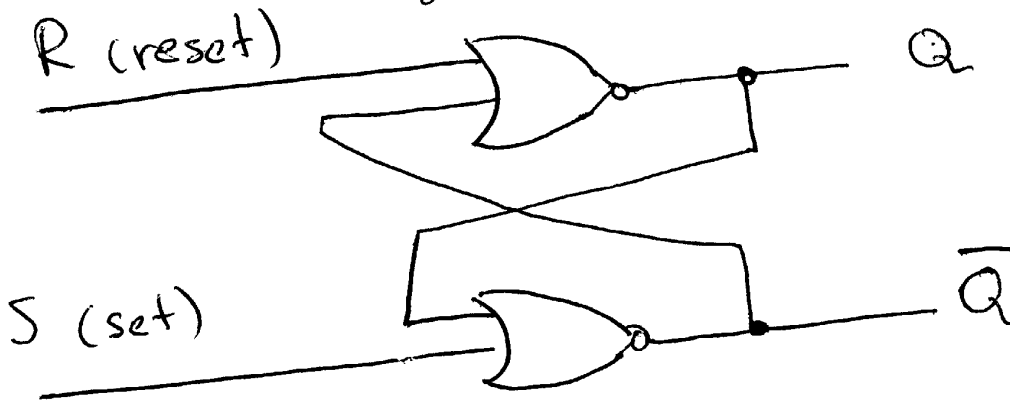SR Latch: P187 Latches are the most basic storage elements, from which flip-flops are usually constructed.




Function table

S	R	Q	\bar{Q}	
1	0	1	0	Set State
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined


SR Latch with NOR gates.

Let $S=1, R=0,$ $t = t_{pd}$

$R(\text{reset})=0$

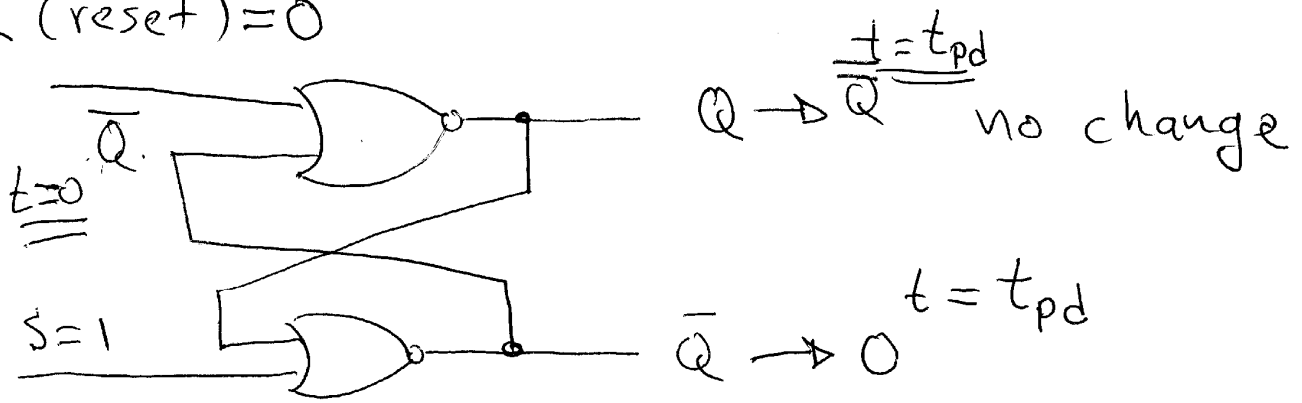


$t = 2t_{pd}$

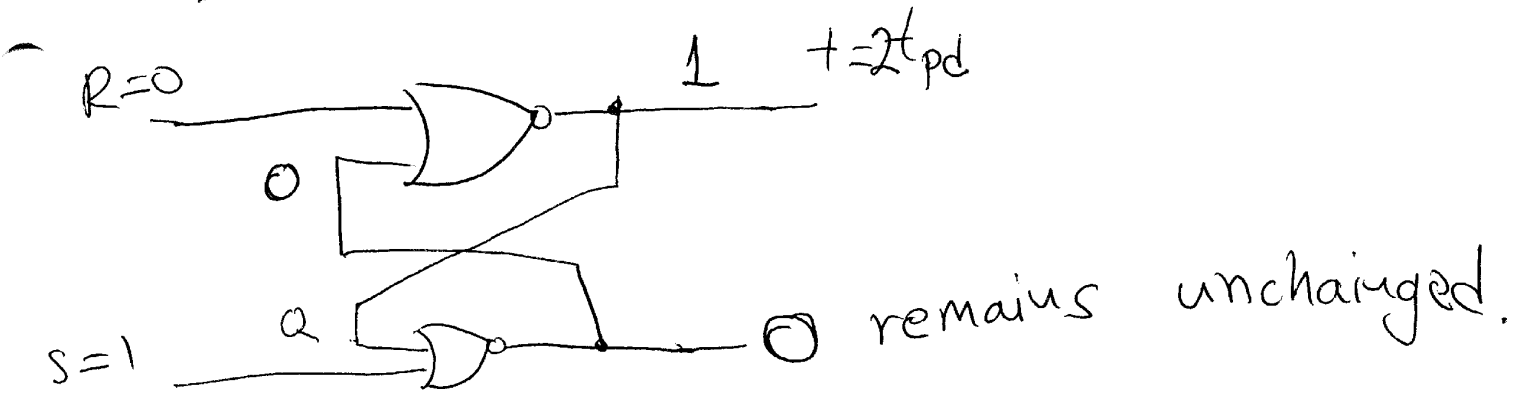


$t = 3t_{pd} \dots$ nothing changes.

Let $S=0, R=1.$ $t = t_{pd}$

5/16

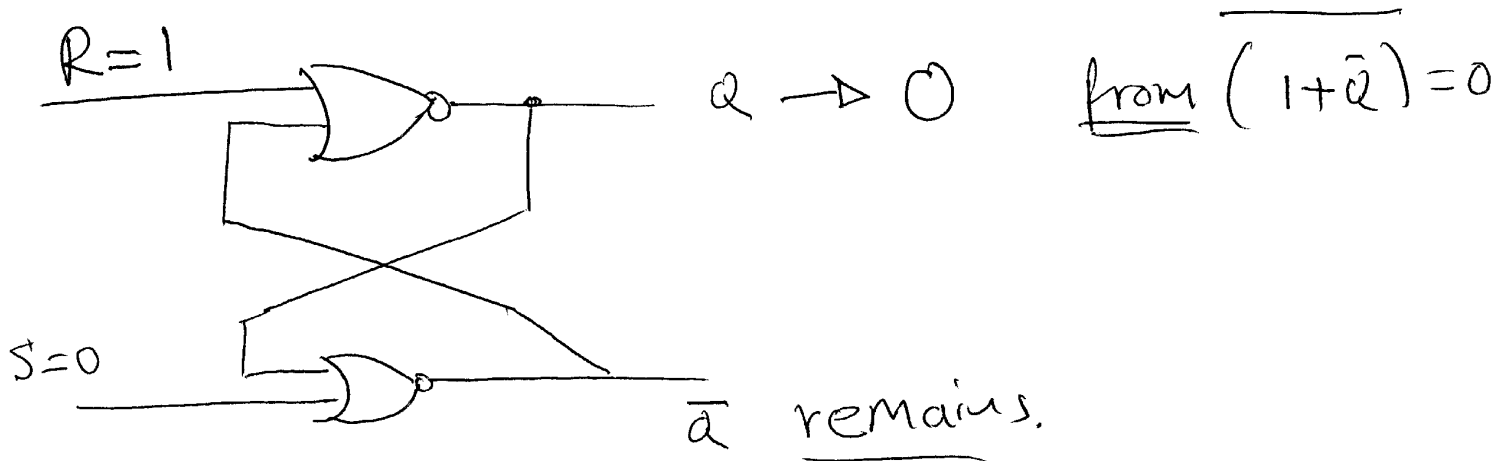


$t = 2 t_{pd}$

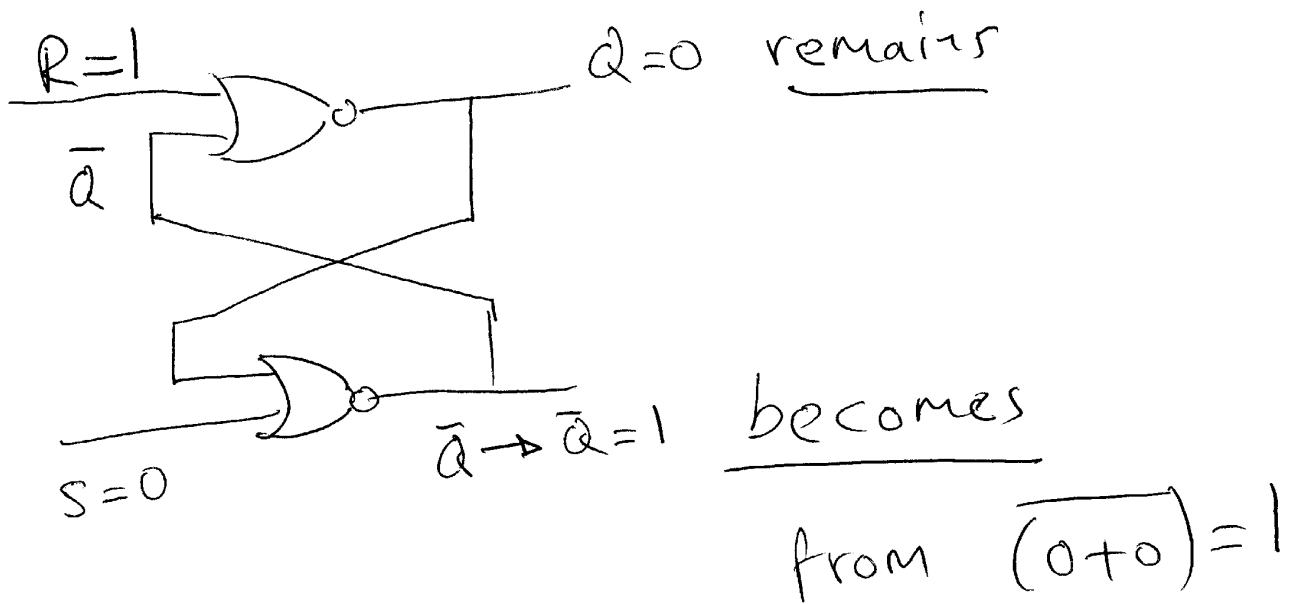

After this, nothing changes.

- $S=1, R=1, t=t_{pd}$

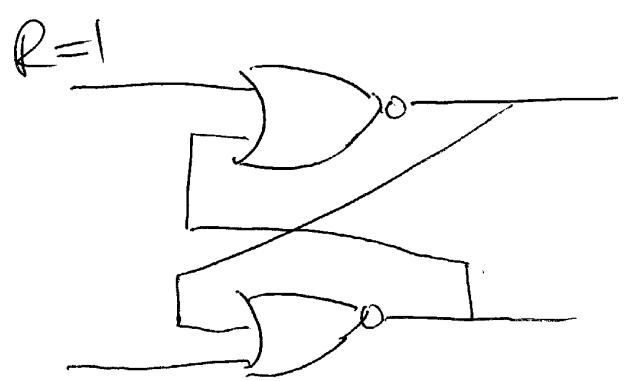

$Q \rightarrow \overline{(Q+1)} = 0$

$\bar{Q} \rightarrow \overline{(\bar{Q}+1)} = 0$

$S=1$

$t=2t_{pd}, \dots$ outputs remain.


- But this state is invalid since:

$Q=0, \bar{Q}=0, (\bar{Q} \text{ should be the complement of } Q).$

If this state is followed by $S=R=0$ at $t=5t_{pd}$, then...

$$t = 6 t_{pd}$$

7
16

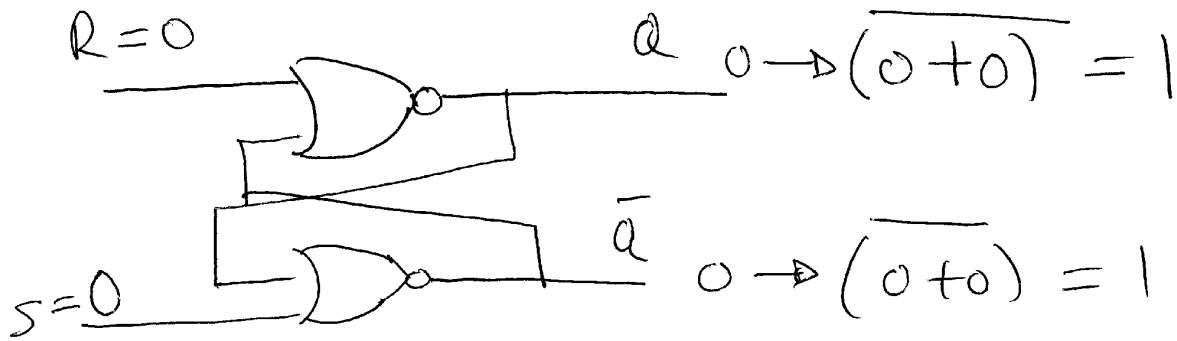

$$t = 7 t_{pd}$$

$$q \rightarrow \overline{(1+0)} = 0$$

$$\bar{q} \rightarrow \overline{(1+0)} = 0$$


$$t = 8 t_{pd}$$

$$q \rightarrow \overline{(0+0)} = 1$$

$$\bar{q} \rightarrow \overline{(0+0)} = 1$$


and it keeps oscillating
from $(q=0, \bar{q}=0)$ to $(q=1, \bar{q}=1)$
to $(q=0, \bar{q}=0)$ to $(q=1, \bar{q}=1)$,
... (see Fig. 4-5)

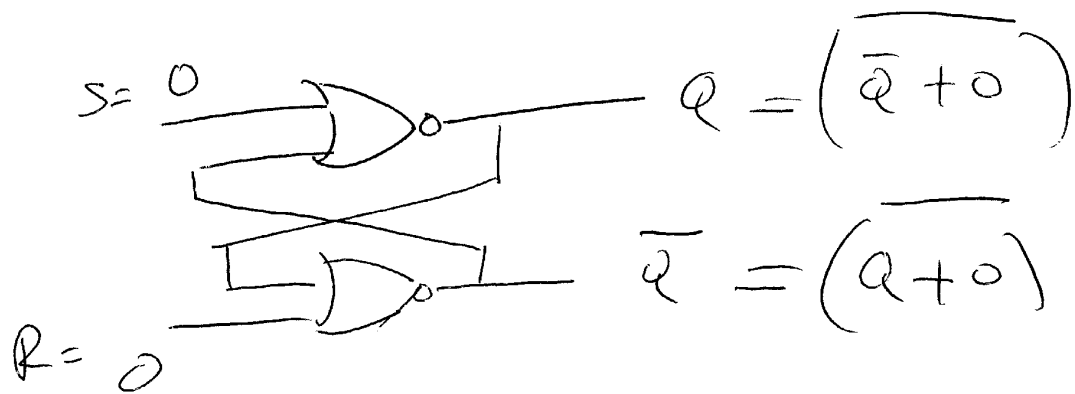Normally, $s=r=0$ has no effect: $\infty/16$



Hence, we can introduce a control input C , for controlling changes:

SR Latch with Control input

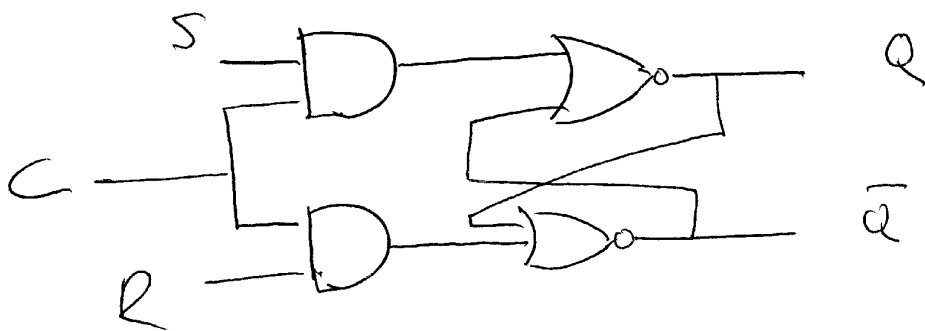


when $C=0$, no change.

when $C=1$, we have regular operation.

In summary, we use:

9/16

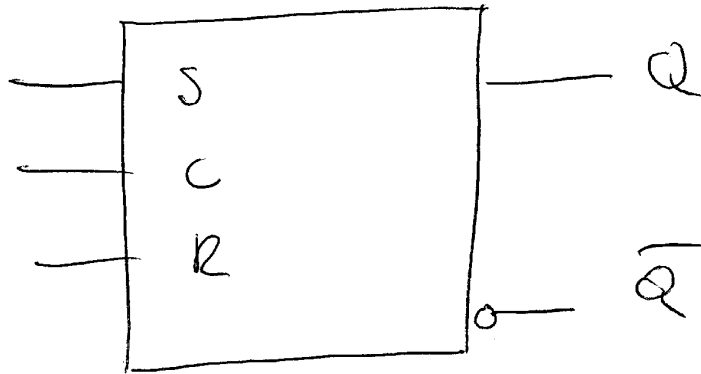


C	S	R	Next state of Q
0	x	x	No change
1	0	0	No change
1	0	1	Q=0; Reset state
1	1	0	Q=1; Set state
1	1	1	Undefined

Master-Slave Flip-Flop p192

10
16

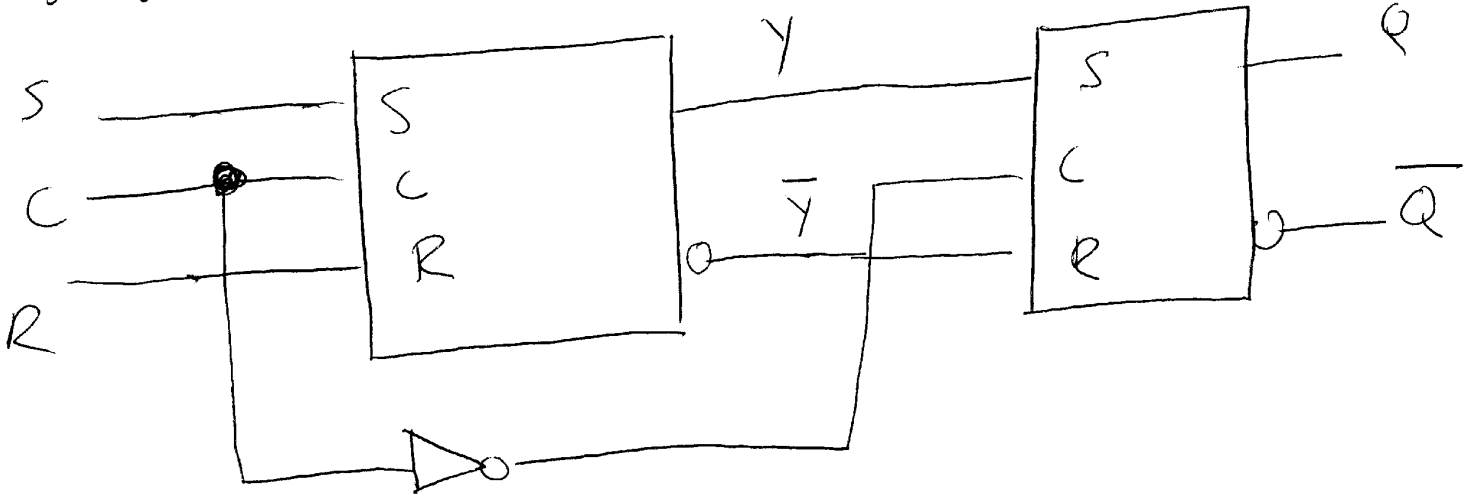The state of a latch in a flip-flop is allowed to switch by a momentary change in value on the control input. This change is called a trigger, and it enables or triggers the flip-flop.




Note that only one of the 2 FFs is active at any time. (they have complemented controls)

This allows the master FF to settle to an output Y, \bar{Y} ($\bar{C}=1$) while the slave is inactive ($\bar{C}=0$), maintaining its previous outputs.

- Then, when $c=0$, the master is ^{"16} not affected by anything, and it holds Y, \bar{Y} steady for the slave to copy into Q, \bar{Q} .

Problem:

Suppose that: (i) we allow $S \& R$ to change during $c=1$ .

(ii) We want to change to $s=0=R$, but we allow $S \& R$ to go from: either:

- (S, R, Q, \bar{Q})
- A. ~~S~~ $S=1, R=0$ to $S=0, R=0$, OR
 - B. ~~R~~ $S=0, R=1$ to $S=0, R=0$ when $c=1$.

I. B/c we first have: $S=1, R=0$ we will set the master FF to $\bar{Y}=1$, despite our intention to leave it as is.

⇒ II. B/c we first have: $S=0, R=1$, we will set $\bar{Y}=0$, instead of unchanged.

∴ We cannot change $S \& R$ for $c=1$.

B/c the FF can change incorrectly 12/14


For $C=1$, we call it pulse-triggered, and ^(+ve edge, or -ve edge) ^{we show} make sure that ~~you~~ we prepare & hold its inputs before

the pulse 

P193, fig. 4-11

Master On Slave On Master On Slave On


13

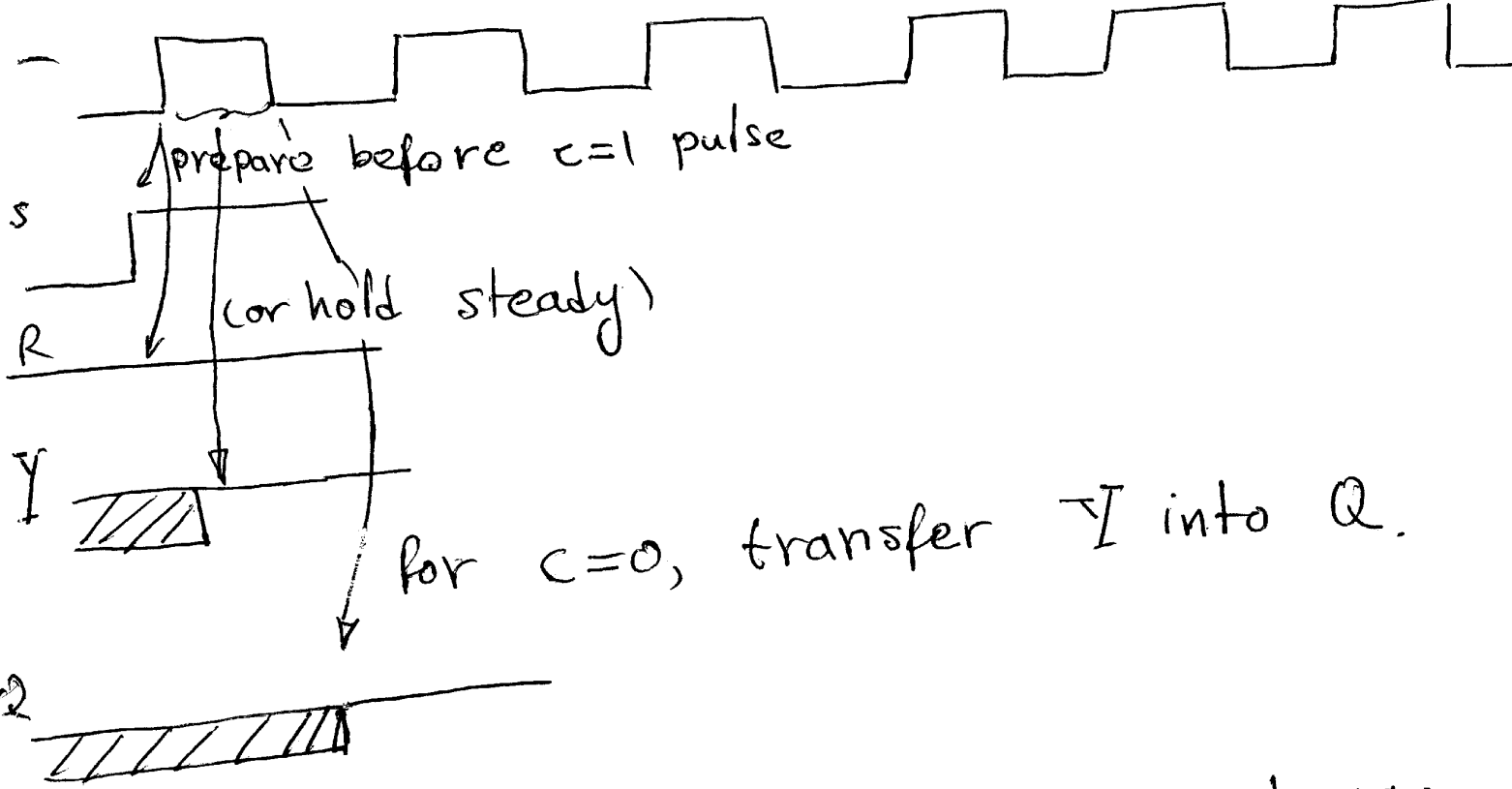

similarly, during $c=0$, we can change s & R to new inputs, and then:
(i) wait for the pulse $c=1$ to change Y , and (ii) change Q to Y when c goes to zero again.

JK FF. (fig 4-12, P194)

14/16

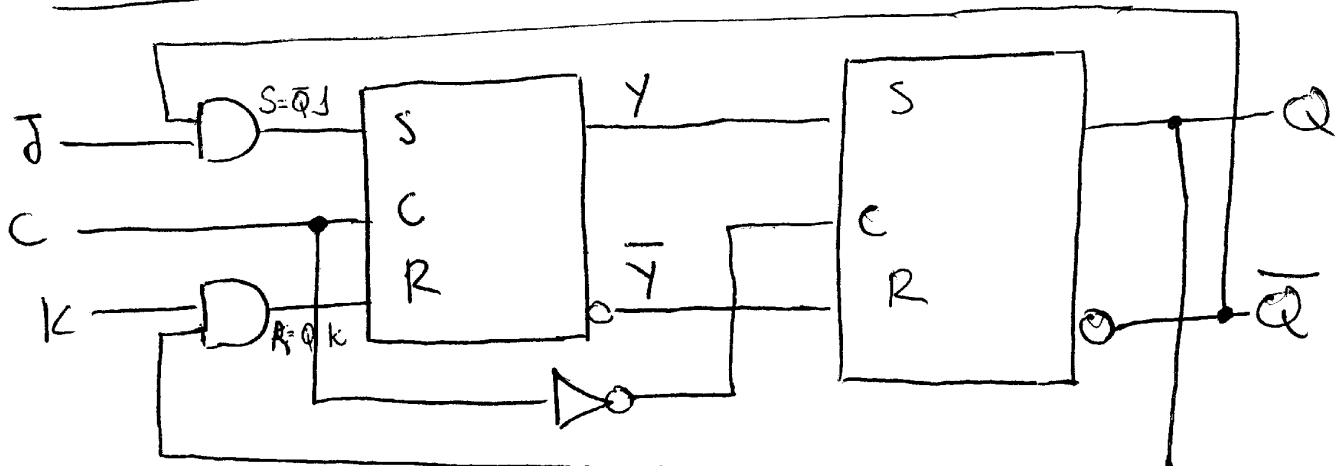

Master-Slave JK Flip-Flop.


J	K	Next-State $Q(t+1)$
0	0	$S=R=0, \underline{Q}$ (unchanged)
0	1	$S=0, R=\underline{KQ}$, taking/keeping Q to <u>0</u>
1	0	$S=\underline{\bar{Q}}, R=0$, taking/keeping Q to <u>1</u>
1	1	$S=\underline{\bar{Q}}, R=Q$, taking Q to <u>\bar{Q}</u>

Edge-triggered FF.

15/15

A D-latch (p 190) simply follows its input:

C	D	Next state
0	x	No change
1	0	0
1	1	1

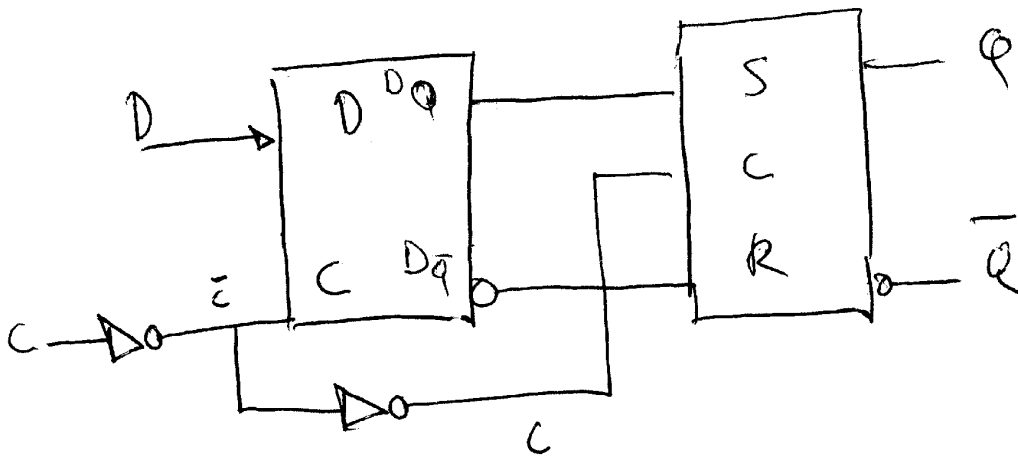


As before, but now a samples (copies)

D at the rising edge of C.


- (i) For the clock input equal to 0, the master latch is enabled and transparent and follows the D input value.
- (ii) The slave latch is disabled and holds the state of the flip-flop fixed.

p198


symbols.

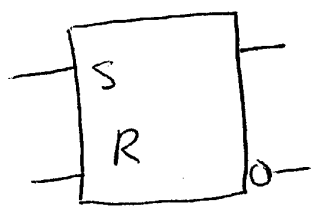


SR Latch

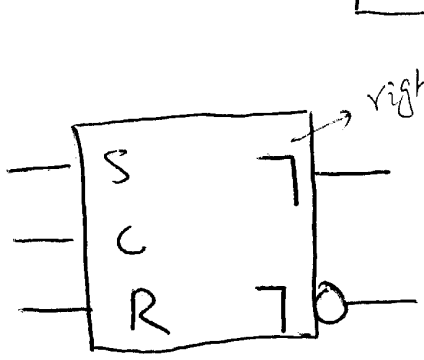


right-angle symbol
↑ Pulse

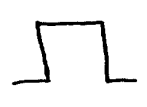

Trigger SR FF.

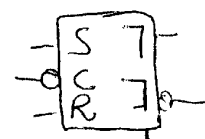


Triggered SR

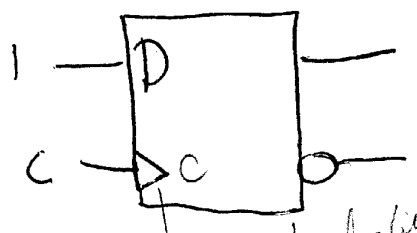

arrowhead-like symbol

edge


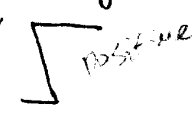


edge-triggered
Triggered D FF.



bubble

negative edge-triggered

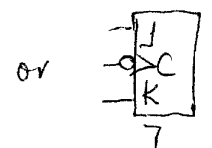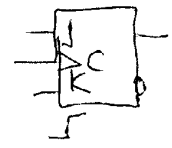

characteristic table for T FF:

T	Q(t+1)
0	Q(t) No change
1	$\bar{Q}(t)$ Complement.

In this class, it is assumed that all flip-flops are of the positive-edge-triggered type, unless otherwise indicated.

Characteristic Tables

They define the next state as a function of the inputs and present state. $Q(t)$ refers to the present state prior to the application of a clock pulse. $Q(t+1)$ is the state one clock period later, which is referred to

Memorize me! p219, table 4-10.

Flip-Flop Excitation Tables

JK FF.

$Q(t) \rightarrow Q(t+1)$	J K
0 \rightarrow 0	0 X
0 \rightarrow 1	1 X
1 \rightarrow 0	X 1
1 \rightarrow 1	X 0

characteristic tables
Flip-flop characteristic tables

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

SR FF

$Q(t) \rightarrow Q(t+1)$	S R
0 \rightarrow 0	0 X
0 \rightarrow 1	1 0
1 \rightarrow 0	0 1
1 \rightarrow 1	X 0

S	R	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	Not Undefined

D FF

$Q(t) \rightarrow Q(t+1)$	D
0 \rightarrow 0	0
0 \rightarrow 1	1
1 \rightarrow 0	0
1 \rightarrow 1	1

Q	D	$Q(t+1)$
0	X	No change
0	0	0
1	1	1

T FF

$Q(t) \rightarrow Q(t+1)$	T
0 \rightarrow 0	0
0 \rightarrow 1	1
1 \rightarrow 0	1
1 \rightarrow 1	0

T	$Q(t+1)$
0	$Q(t)$ No change
1	$\bar{Q}(t)$ complement