

Definitions

XOR: $X \oplus Y = X\bar{Y} + \bar{X}Y$

Truth Table:

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

Notice that: $(X \oplus Y) \oplus Y = X$ from: ~~Encryption~~ Encryption.

X	$X \oplus Y$	Y	$(X \oplus Y) \oplus Y$
0	0	0	0
0	1	1	0
1	0	0	1
1	1	1	0

some.

If: X represents a background pixel,
 Y represents a foreground pixel.

$X \oplus Y$ "places" Y on X,
 $(X \oplus Y) \oplus Y$ removes Y and restores X

Its complement:

$$\begin{aligned} \overline{X \oplus Y} &= (\overline{X \bar{Y} + \bar{X} Y})' \\ &= (X' + Y)(X + Y') \\ &= \cancel{X'X} + X'Y' + YX + \cancel{YY'} \\ &= X'Y' + YX \end{aligned}$$

which is only true if X is the same as Y :

	X	Y	
		0	1
0	1	0	
1	0	1	

$$\overline{X \oplus Y}$$

Note diagonal pattern

- \oplus is commutative: $A \oplus B = B \oplus A$
 \oplus is associative: $(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$

\oplus K-maps occupy alternating tiles:

	X	YZ			
		00	01	11	10
0			1		1
1	1			1	

$$X \oplus Y \oplus Z$$

Identities:

$$X \oplus 0 = X$$

$$X \oplus X = 0$$

$$X \oplus \bar{Y} = \overline{X \oplus Y}$$

$$X \oplus 1 = \bar{X}$$

$$X \oplus \bar{X} = 1$$

$$\bar{X} \oplus Y = \overline{X \oplus Y}$$

← 1 when the number of 1s in XYZ is odd.

- 4-variable map obeys the same principle: It has 1s when the number of 1s in ABCD is odd.

		CD			
		00	01	11	10
AB	00		1		1
	01	1		1	
	11		1		1
	10	1		1	

$A \oplus B \oplus C \oplus D$

This property makes XOR ideal for parity generation and parity checking.

Parity Generation: For a given number of bits, attach a new bit of 0 or 1 to ensure that the total number of 1s is either even or odd.

- Ex: odd parity bit generation.

101 has 2 1s.

- (a) Attach 1 at the end to get:
1011 which has 3 1s and odd-parity
- (b) Attach 0 at the end to get:
1010 which has 2 1s and even-parity

- The logical function f which returns 1, ^{making} ^{total} the number of 1s in its argument even is called the odd-function. It can be realized

using XOR:

$$f(A, B) = A \oplus B$$

$$f(A, B, C) = A \oplus B \oplus C$$

$$f(A, B, C, D) = A \oplus B \oplus C \oplus D$$

$$f(x_1, \dots, x_n) = x_1 \oplus x_2 \oplus \dots \oplus x_n$$

To generate ~~even~~ parity bit for 5/5

7-bits: $f(x_1, \dots, x_7) = x_1 \oplus \dots \oplus x_7$.


For ~~even~~ ^{odd} parity, simply complement:

$$f'(x_1, \dots, x_7) = \overline{(x_1 \oplus \dots \oplus x_7)}$$


or implement using exclusive-NOR gates

gates

XOR GATES

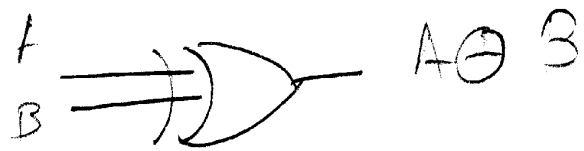

X-NOR GATES

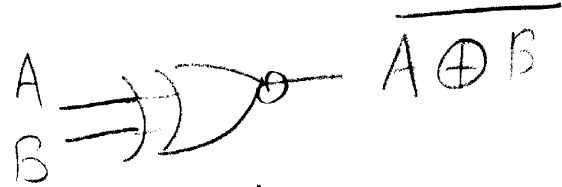


Sender

Even parity

generation & checking (use odd functions)




Receiver

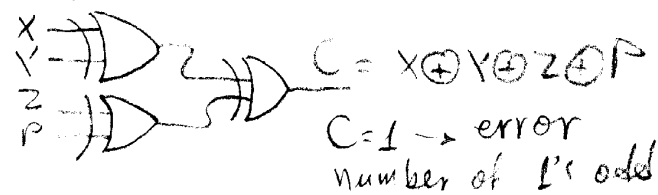


Odd parity generation & checking (use even functions)

Sender

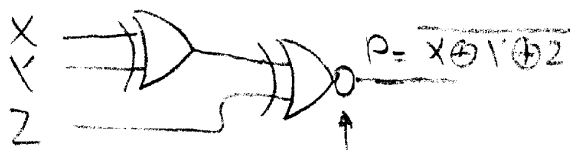

Receiver

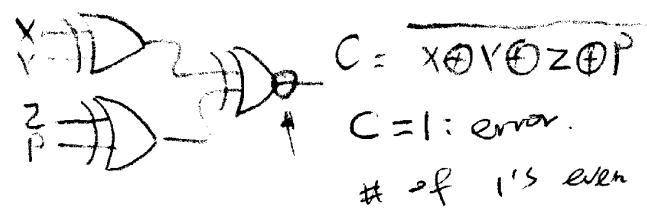

Plotting XOR K-maps

Ignore

AB \ CD	00	01	11	10
00				
01	1	1	1	1
11				
10	1	1	1	1

$A \oplus B = 1$
when $\begin{cases} A=1, B=0 \\ A=0, B=1 \end{cases}$

$A' \oplus B = 1$

when $\begin{cases} A'=0, B=1 \\ A'=1, B=0 \end{cases}$

AB \ CD	00	01	11	10
00	1	1	1	1
01				
11	1	1	1	1
10				

or $\begin{cases} A=1, B=1 \\ A=0, B=0 \end{cases}$

$A \oplus B = 1$

$A' \oplus B \oplus C = 1$

when we have odd # of 1s:

AB \ CD	00	01	11	10
00	1	1		
01			1	1
11	1	1		
10			1	1

$A'=1, B=0, C=0, (A=0)$
 $A'=1, B=1, C=1, (A=0)$
 $A'=0, B=1, C=0, (A=1)$
 $A'=0, B=0, C=1, (A=1)$