

Programming Languages (PL) vs. Hardware Description Languages (HDL)

Programming languages such as C or Java **cannot** serve as HDLs (unless modified significantly).

Programming languages are modeled after a sequential process, where operations are performed in a sequential order (order matters).

This is amenable to the human thinking process, in which an algorithm is unfolded into a *recipe* or step-by-step process

HDLs such as VHDL (**VHSIC** (Very High Speed Integrated Circuit) **HDL**) and Verilog were developed to support the underlying characteristics of hardware

- Connections of parts
- Concurrent operations
- Concept of propagation delay and timing

These characteristics cannot be captured by traditional PLs

Hardware Description Languages (HDL)

HDLs serve several roles in the design process

- Formal documentation
- Input to a simulator
- Input to a synthesizer

The fundamental characteristics of a digital circuit are captured using the concepts:

- *Entity*: a self-contained, basic building block of a real circuit
- *Connectivity*: models the connecting wires among the circuit components
- *Concurrency*: models parallel operations carried out by interconnected components
- *Timing*: models starting and ending of each operation and defines an order

HDLs can be used to describe a design at the **gate level** and **RT level**, in either a **structural** or **behavioral** view.

Other highlights of a modern HDL include:

- Sequential execution constructs (similar to PLs) for modeling behavior
- A set of mathematical, Boolean and other special purpose operations, e.g., shifting
- Constructs to support hierarchical design process

Hardware Description Languages (HDL)

VHDL and **Verilog** are the industry standards

- Syntax and “appearance” of the two languages are very different
- Capabilities and scopes are quite similar
- Both are supported by most software tools

VHDL initially sponsored by DoD as a hardware documentation standard, early 80s

Transferred to IEEE and ratified it as IEEE standard 1176 in 1987 (known as VHDL-87)


Major modification in '93 (known as VHDL-93), but revisions continue

IEEE Extensions

- IEEE standard 1076.1 Analog and Mixed Signal Extensions (VHDL-AMS)
- IEEE standard 1076.2 VHDL Mathematical Packages
- IEEE standard 1076.3 Synthesis Packages
- IEEE standard 1076.4 VHDL Initiative Towards ASIC Libraries (VITAL)
- IEEE standard 1076.6 VHDL Register Transfer Level (RTL) Synthesis
- IEEE standard 1164 Multivalued Logic System for VHDL Model Interoperability
- IEEE standard 1029 VHDL Waveform and Vector Exchange (WAVES)

VHDL Introduction

 VHDL introduction through an example: *Even parity* detection circuit



Input:
a(2), a(1), a(0)

Output:
even

a(2)	a(1)	a(0)	even
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

SOP expr: $even = a(2)' \cdot a(1)' \cdot a(0)' + a(2)' \cdot a(1) \cdot a(0) + a(2) \cdot a(1)' \cdot a(0) + a(2) \cdot a(1) \cdot a(0)'$

```

library ieee;
use ieee.std_logic_1164.all;
-- entity declaration
entity even_detector is
  port (
    a: in std_logic_vector(2 downto 0);
    even: out std_logic
  );
end even_detector;

```

VHDL Introduction

```
-- architecture body
architecture sop_arch of even_detector is
  signal p1, p2, p3, p4 : std_logic;
  begin
    even <= (p1 or p2) or (p3 or p4);
    p1 <= (not a(2)) and (not a(1)) and (not a(0));
    p2 <= (not a(2)) and a(1) and a(0);
    p3 <= a(2) and (not a(1)) and a(0);
    p4 <= a(2) and a(1) and (not a(0));
  end sop_arch;
```

Entity declaration

- Specifies I/O ports

One input port, an array *a* of three components and one output port, *even*.


Architecture body specifies internal operation of the circuit

- Signal declaration: defines a set of 'wires' *p1* through *p4*

VHDL Introduction

- The concurrent (signal assignment) statements
Are the circuit components
- Architecture body can be thought as a "collection of five circuit parts"
Signal name on both right and left indicates a wire connecting these components
Component order does NOT matter!


Conceptual Interpretation:

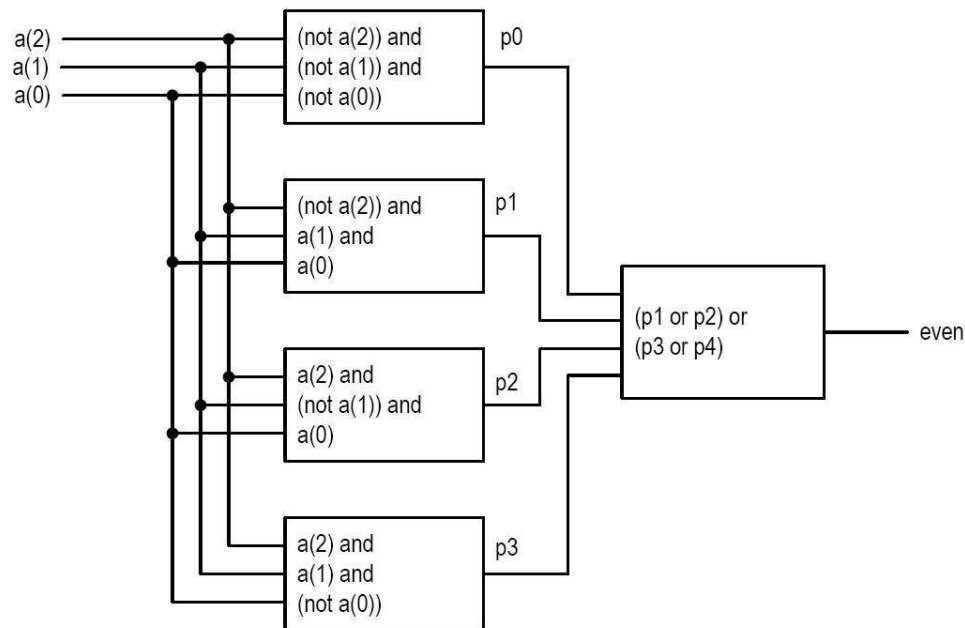

VHDL Introduction

More efficient architecture which uses *xor* operator (entity declaration is the same):
 
```
architecture xor_arch of even_detector is  
  signal odd: std_logic;  
  begin  
    even <= not odd;  
    odd <= a(2) xor a(1) xor a(0);  
end xor_arch;
```



Structural Description

In structural view, a circuit is constructed of smaller components

A structural description specifies the types of parts and connections

Essentially a textual description of a schematic


Structural Description

A structural description can also be done using the concept of 'component'

- First declared (make known)
- Then instantiated (used)

Consider the *even-parity* detector again

 Assume there is a *library* of predesigned parts, **xor2** and **not1**:



Structural Description

```
architecture str_arch of even_detector is
  component xor2 -- declaration for xor gate
    port (
      i1, i2: in std_logic;
      o1: out std_logic
    );
  end component;

  component not1 -- declaration for inverter
    port (
      i1: in std_logic;
      o1: out std_logic
    );
  end component;

  signal sig1,sig2: std_logic;
```

Structural Description

begin

```
-- instantiation of the 1st xor instance
unit1: xor2
    port map (i1=>a(0), i2=>a(1), o1=>sig1);
-- instantiation of the 2nd xor instance
unit2: xor2
    port map (i1=>a(2), i2=>sig1, o1=>sig2);
-- instantiation of inverter
unit3: not1
    port map (i1=>sig2, o1=>even);
end str_arch;
```

Architecture body consists of three statements

Each statement consists of three parts:

The *unit1* label serves as a unique id for this part

The *xor2* identifies the instantiated component

The *port map* specifies the mapping between the **formal** and **actual** signals

Structural Description

The mapping indicates that *formal* signals *i1*, *i2* and *o1* are connected to *actual* signals *a(0)*, *a(1)* and *sig1*

Component instantiation is one type of *concurrent* statement, and can be mixed with other types

When the architecture body consists of only component instantiations (as above), it is just a textual description of a **schematic**

A schematic is a more natural representation but this textual description enables schematics to be embedded with other VHDL coding styles

The definition of the actual components are 'decoupled' and 'hidden' from the architecture and can be defined (and later changed) in a library

```
library ieee;  
use ieee.std_logic_1164.all  
entity xor2 is  
  port (  
    i1, i2: in std_logic;
```

Structural Description

```
        o1: out std_logic
    );
end xor2;

architecture beh_arch of xor2 is
    begin
        o1 <= i1 xor i2;
    end beh_arch;

library ieee;
use ieee.std_logic_1164.all
entity not1 is
    port (
        i1: in std_logic;
        o1: out std_logic
    );
end not1;
```

Structural Description

```
architecture beh_arch of not1 is  
  begin  
    i1 <= not o1;  
  end beh_arch;
```

The use of components facilitates

- **Hierarchical** design (divide a system into smaller components, each designed individually)
- **IP** incorporation (use of complex, third party, predesigned circuits that can be black boxes)

Behavioral Description

Human reasoning and algorithms resemble a sequential process

VHDL provides language constructs that resemble sequential semantics

The **process**: a language construct to encapsulate 'sequential semantics'

The entire **process** stmt is a **concurrent** statement

Behavioral Description

Syntax:

```
process (sensitivity_list)
  variable declaration;
  begin
    sequential statements;
end process;
```

The *process* has a **sensitivity list**, which is a set of signals

When a signal in the sensitivity list changes, the process is "activated"

Inside the process, the semantics are similar to that of a PL, e.g., variables can be used and execution of the statements is sequential

Consider the *even-parity* detector:

```
architecture beh1_arch of even_detector is
  signal odd: std_logic;
  begin
```

Behavioral Description


```
-- inverter
  even <= not odd;
-- xor network for odd parity
process (a)
  variable tmp: std_logic;
begin
  tmp := '0';
  for i in 2 downto 0 loop
    tmp := tmp xor a(i);
  end loop;
  odd <= tmp;
end process;
end beh1_arch;
```

The *xor* network is described by a process that utilizes a **variable** and a **for loop**

Unlike signal assignment in a concurrent statement, the *variable* and *loop* constructs do NOT have a direct hardware counterpart

Behavioral Description

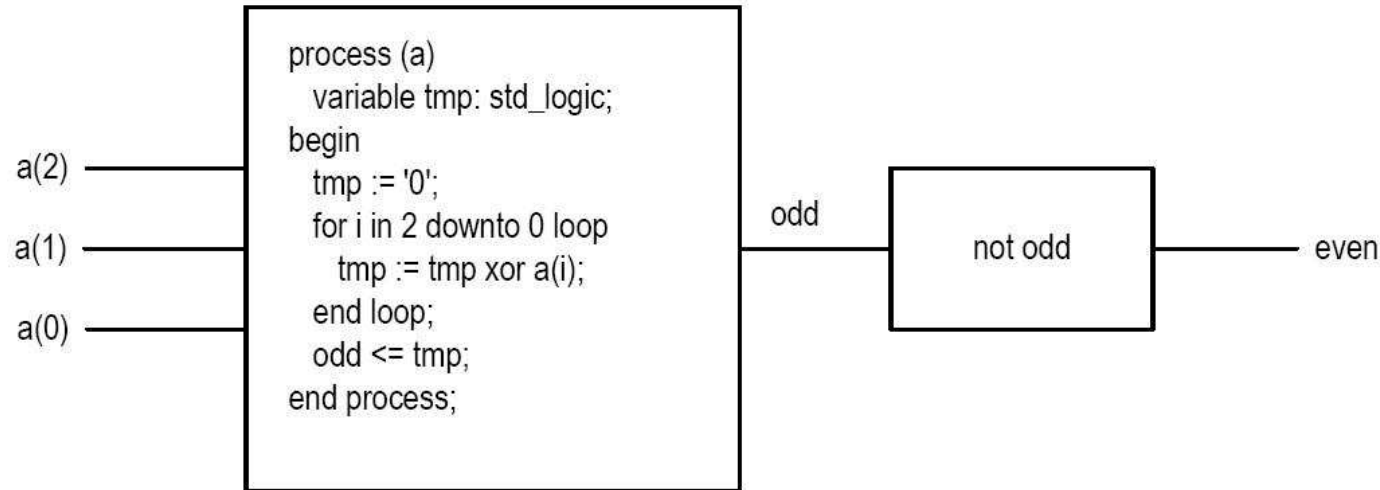The process should be treated as one *indivisible* part, whose behavior is specified by sequential statements



A second example:

```
architecture beh2_arch of even_detector is
  begin
    process (a)
      variable sum, r: integer;
      begin
```


Behavioral Description


```
sum := 0;
for i in 2 downto 0 loop
    if a(i)='1' then
        sum := sum + 1;
    end if;
end loop ;
r := sum mod 2;
if (r=0) then
    even <= '1';
else
    even <= '0';
end if;
end process;
end beh2_arch;
```

Note that this is easy to understand, but there is no clue about the underlying structure and how this will be actually implemented

The code describes the **behavior** of the component, not the structure.

Behavioral Description

Conceptual diagram

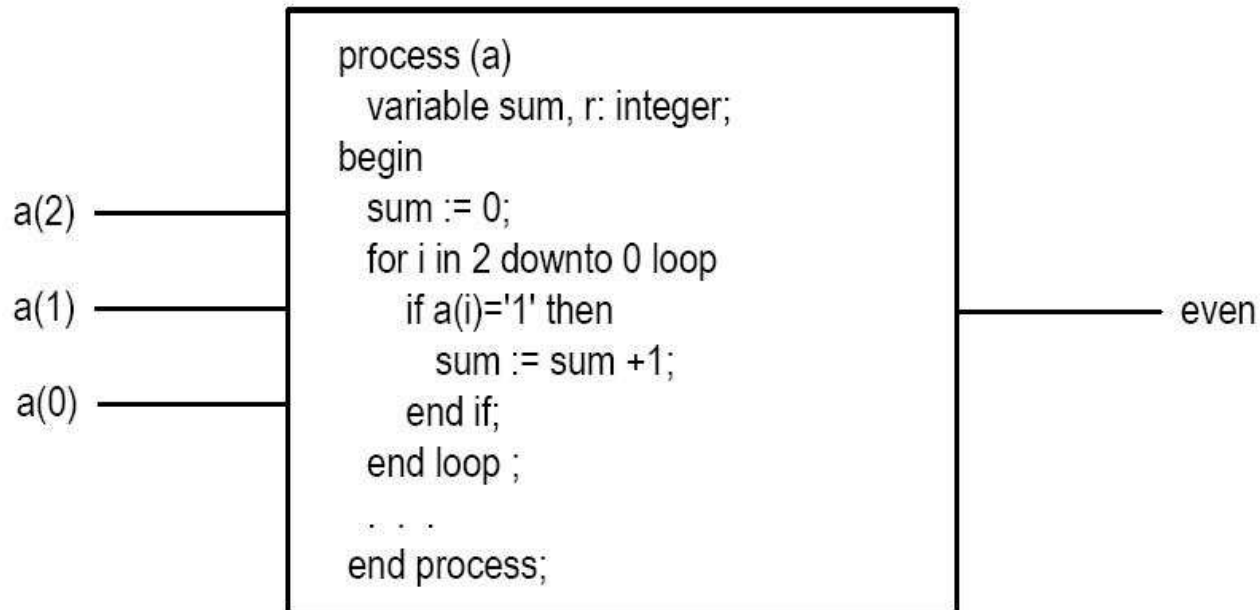

Testbench

A 'virtual' experiment setup, consisting of

- The circuit to be tested
- The input stimuli (e.g., pattern generator)
- An output monitor (e.g., logic analyzer)

Testbench

Testbench for *even-parity* detector

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity even_detector_testbench is  
end even_detector_testbench;  
  
architecture tb_arch of even_detector_testbench is  
-- declaration of component to be tested  
  component even_detector  
    port (  
      a: in std_logic_vector(2 downto 0);  
      even: out std_logic  
    );  
  end component;  
  
  signal test_in: std_logic_vector(2 downto 0);  
  signal test_out: std_logic;
```

Testbench

```
begin
-- instantiate the circuit under test
  uut: even_detector
    port map(a=>test_in, even=>test_out);

-- test vector generator
process
  begin
    test_in <= "000";
    wait for 200 ns;
    test_in <= "001";
    wait for 200 ns;
    test_in <= "010";
    wait for 200 ns;
    test_in <= "011";
    wait for 200 ns;
    test_in <= "100";
    wait for 200 ns;
```

Testbench

```
    test_in <= "101";
    wait for 200 ns;
    test_in <= "110";
    wait for 200 ns;
    test_in <= "111";
    wait for 200 ns;
end process;

--verifier
process
    variable error_status: boolean;
begin
    wait on test_in;
    wait for 100 ns;
    if ((test_in="000" and test_out = '1') or
        (test_in="001" and test_out = '0') or
        (test_in="010" and test_out = '0') or
        (test_in="011" and test_out = '1') or
```

Testbench

```
(test_in="100" and test_out = '0') or
(test_in="101" and test_out = '1') or
(test_in="110" and test_out = '1') or
(test_in="111" and test_out = '0'))

then
    error_status := false;
else
    error_status := true;
end if;

-- error reporting
    assert not error_status
        report "test failed."
        severity note;
end process;
end tb_arch;
```


Testbench

Two concurrent process statements are given, and both processes run simultaneously

Note the use of *non-synthesizable* statements such as **wait for** and **assert not**

Since testbenches are NOT synthesized to logic (only used in simulations), this is not a problem

Conceptually:

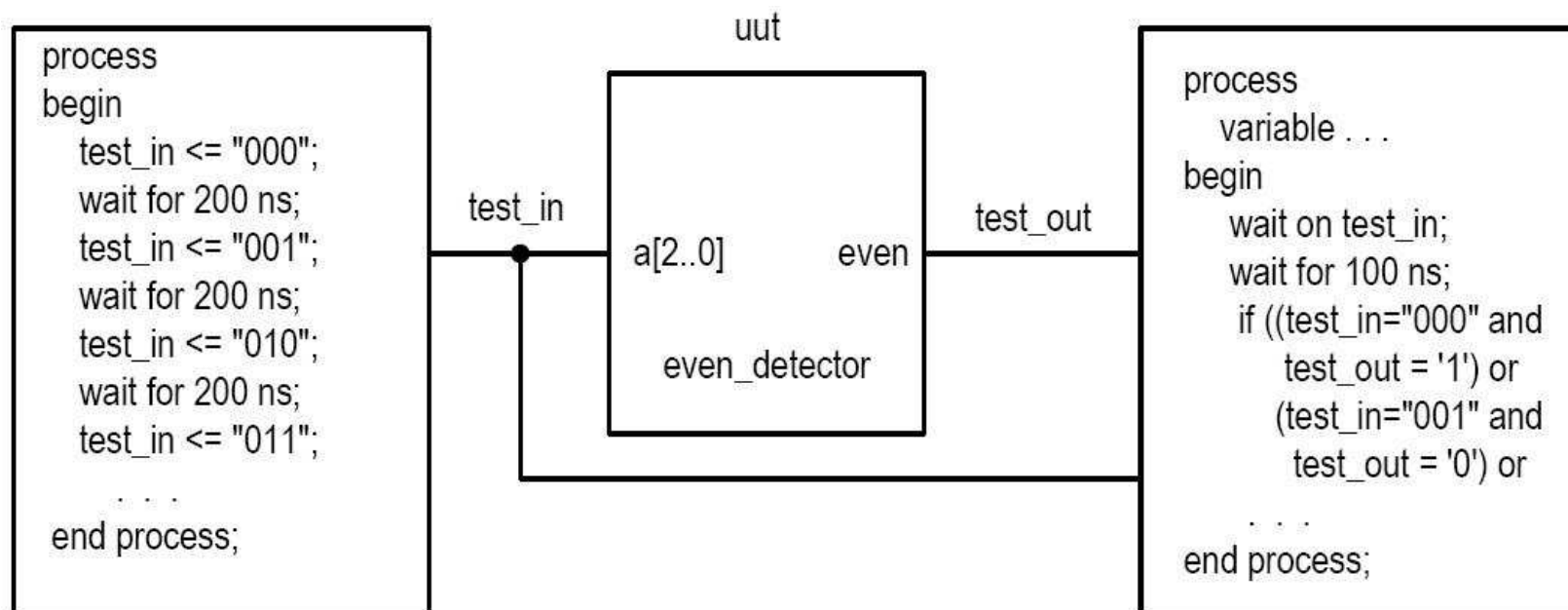

VHDL in Development Flow

Behavioral description written first, simulated


Synthesis-oriented code developed

It is also simulated, many times using the same testbench to confirm it meets specification

Once synthesized, the result is a gate-level netlist represented by a **structural** VHDL description

It is also simulated, and and timing analyzed

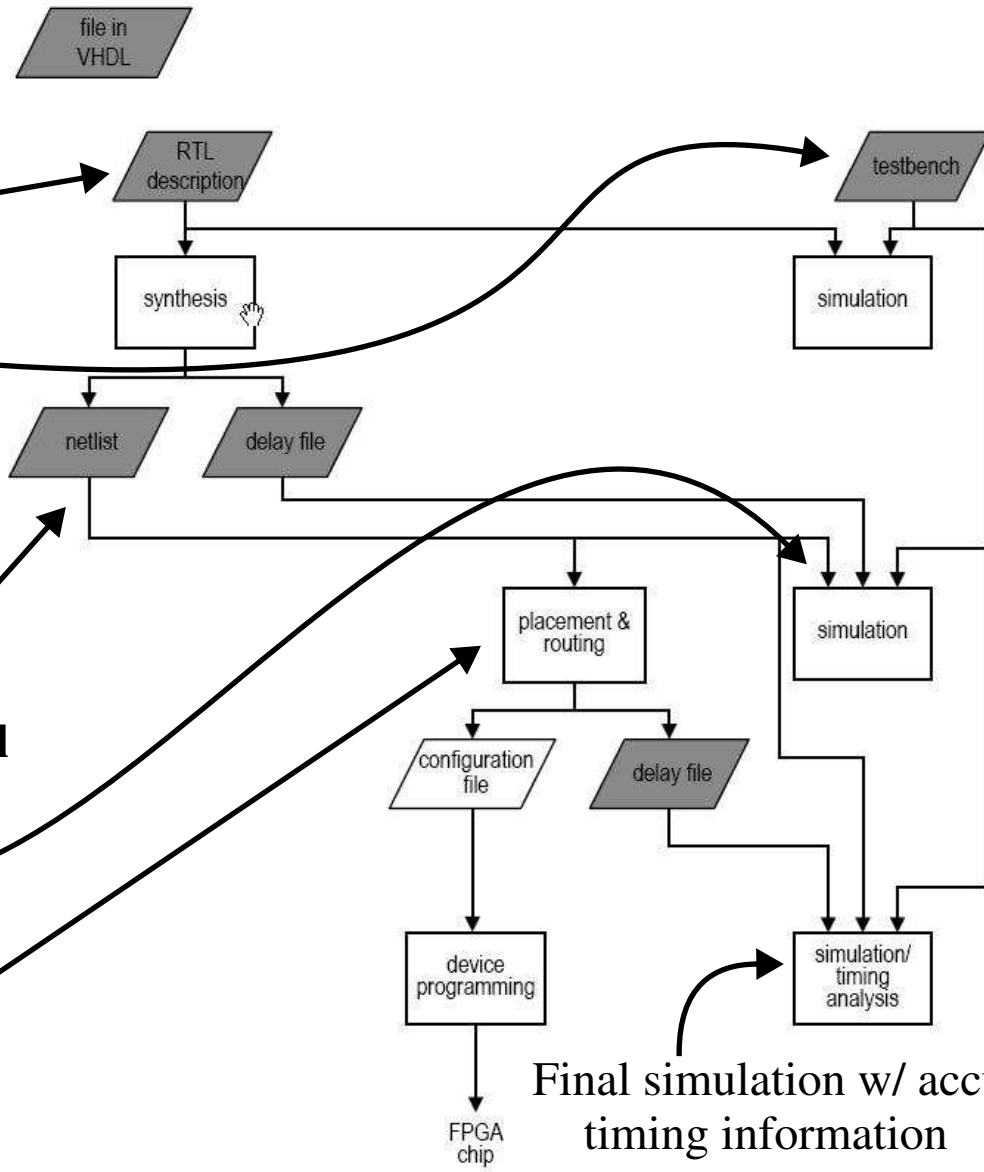Place and route produces a GDS for ASICs or a bitstream for FPGAs



Coding for Synthesis

Execution of VHDL code

- For Simulation:

Design is 'realized' in a virtual environment, the simulation software

All language constructs can be 'realized' here

- For Synthesis

Design is 'realized' by hardware components

- Many VHDL constructs can NOT be synthesized, e.g, file operation, floating-point data type, division

- Also realize that although any VHDL code is 'easy' to simulate, it may be difficult to synthesize

VHDL code that contains 10 additions needs to be mapped to 10 adders

(unless resources are shared), a fairly complex set of hardware components